

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)
Examination for Direct Second Year Students Commencing from 10th April 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2019

Examination: SE Semester III (For DSE Students)


Course Code: ELC304 and Course Name: Electrical Network Analysis and Synthesis


Time: 2 hour


Max. Marks: 80



Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	-----between coils is defined as fraction of magnetic flux produced by the current in one coil that links the other
Option A:	Coefficient of Coupling
Option B:	Self Inductance
Option C:	Mutual Inductance
Option D:	Self Coupling
2.	The combined inductance of two coils connected in series is 0.6 H or 0.1 H depending on relative directions of currents in the two coils. If one of the coils has a self-inductance of 0.2 H, find (a) mutual inductance, and (b) coefficient of coupling.
Option A:	(a)M=0.105H , (b) K= 0.62
Option B:	(a)M=0.125H , (b) K= 0.72
Option C:	(a)M=0.115H , (b) K= 0.72
Option D:	(a)M=0.125H , (b) K= 0.62
3.	Which notation of instant implies that the unchanged condition of network is about to change?
Option A:	$t(0)^+$
Option B:	$t(0)^-$
Option C:	t^*
Option D:	\hat{t}
4.	What does 'σ' indicate in the equation of complex frequency variable $s = \sigma + j\omega$ while defining the Laplace transform?
Option A:	Attenuation constant
Option B:	Damping factor





Option C:	Propagation constant
Option D:	Phase constant
5.	Consider a function $f(t)$ that satisfies the differential equation given below. What equation will be generated by taking Laplace transform and replacing the terms $f(0^-)$ & $f'(0^-)$ by zero? $[d^2 f(t) / dt^2] + 5 [df(t) / dt] + 6 f(t) = 10$
Option A:	$[S^2 F(s) + 5s F(s) + 6 F(s)] = 10/s$
Option B:	$[S^2 F(s) + 5s F(s) - 6 F(s)] = 10/s$
Option C:	$[S^2 F(s) - 5s F(s) + 6 F(s)] = 10/s$
Option D:	$[S^2 F(s) - 5s F(s) - 6 F(s)] = 10/s$
6.	What is an ideal value of network function at poles?
Option A:	Zero
Option B:	Nonzero
Option C:	Infinity
Option D:	Unity
7.	The realization of driving point immittance functions of networks can be done by any of the forms which are not used from following
Option A:	Foster I
Option B:	Foster II
Option C:	Cauer I
Option D:	Cauer II
8.	Which among the following represents the precise condition of reciprocity for transmission parameters?
Option A:	$AD-BC=0$
Option B:	$AC-BD=1$
Option C:	$AD-BC=1$
Option D:	$BC-AD=1$
9.	The relation between Z_{OT} , Z_{oc} , Z_{sc} is?
Option A:	$Z_{OT} = \sqrt{Z_{oc} Z_{sc}}$
Option B:	$Z_{oc} = \sqrt{(Z_{OT} Z_{sc})}$
Option C:	$Z_{sc} = \sqrt{(Z_{OT} Z_{oc})}$
Option D:	$Z_{oc} = \sqrt{(Z_{OT} Z_{oc})}$
10.	In determining Hybrid parameters, among V_1 , V_2 , I_1 , I_2 , which of the following

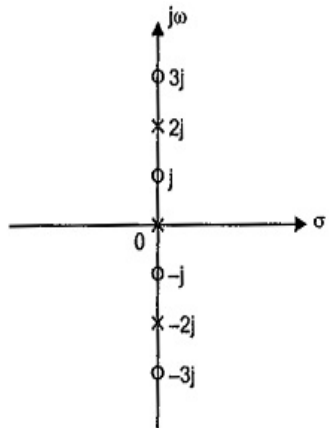
	are dependent variables?
Option A:	V_1 and V_2
Option B:	I_1 and I_2
Option C:	V_1 and I_2
Option D:	I_1 and V_2
11.	The Laplace transform of a unit-ramp function starting at $t = a$ is
Option A:	$\frac{1}{(s+a)^2}$
Option B:	$\frac{e^{-as}}{(s+a)^2}$
Option C:	$\frac{e^{-as}}{s^2}$
Option D:	$\frac{a}{s^2}$
12.	 <p style="text-align: center;">Fig. 7.4</p> <p>Above pole zero diagram indicates which function</p>
Option A:	RC
Option B:	LC
Option C:	RL
Option D:	RLC
13.	A system is represented by the transfer function $10 / (S+2)(s+1)$, The dc gain of this system is
Option A:	1
Option B:	5
Option C:	10
Option D:	2
14.	The transfer function of a low-pass RC network is

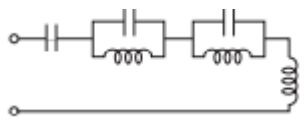Option A:	$(RCs) (1 + RCs)$
Option B:	$\frac{RCs}{1 + RCs}$
Option C:	$\frac{1}{1 + RCs}$
Option D:	$\frac{s}{1 + RCs}$
15.	The input ports of two networks are connected in series and the output ports are connected in parallel ,then resultant h-parameter matrix is the ----- of h-parameter matrices of each individual two-port network
Option A:	Substraction
Option B:	Division
Option C:	Multiplication
Option D:	Sum
16.	For a two-port network to be reciprocal
Option A:	$z_{11} = z_{22}$
Option B:	$y_{21} = y_{12}$
Option C:	$h_{21} = h_{12}$
Option D:	$AD - BC = 0$
17.	The number of roots of $s^3 + 5s^2 + 7s + 3 = 0$ in the right half of s-plane is
Option A:	Zero
Option B:	One
Option C:	Two
Option D:	Three
18.	The circuit shown in Fig. is 
Option A:	Cauer I form
Option B:	Cauer II form
Option C:	Foster I form
Option D:	Foster II form
19.	From below functions which is positive real function
Option A:	$F(s) = \frac{s^3 + 5s}{s^4 + 2s^2 + 1}$
Option B:	$F(s) = \frac{s^2 + s + 6}{s^2 + s + 1}$

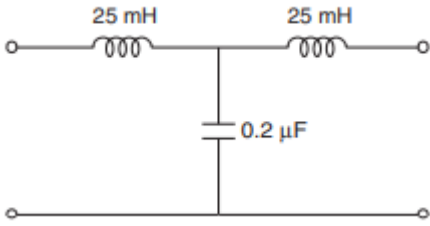Option C:	$F(s) = \frac{s^2 + 4}{s^3 + 3s^2 + 3s + 1}$
Option D:	$F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$
20.	Find the nominal impedance, cut-off frequency for the network shown in fig. 
Option A:	nominal impedance=500, cut-off frequency=3.18Khz
Option B:	nominal impedance=600, cut-off frequency=3.18Khz
Option C:	nominal impedance=500, cut-off frequency=2.16Khz
Option D:	nominal impedance=600, cut-off frequency=2.16Khz

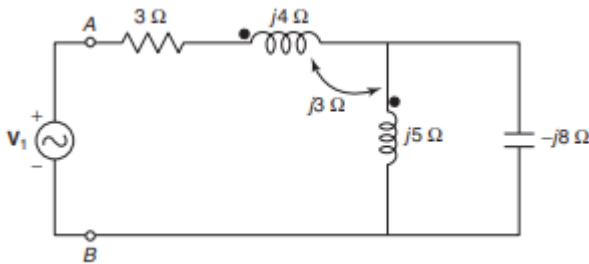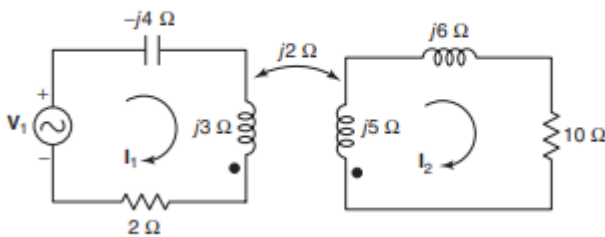Q2 (20 Marks)	Solve any Four out of Six (5 marks each)
A	For the coupled circuit shown in Figure, find input impedance at terminals A and B. 
B	Find the conductively coupled equivalent circuit for the network shown in Fig. 
C	In the network shown in Figure, the switch is changed from the position 1 to the position 2 at $t = 0$, steady condition having reached before switching. Find the values of I , di/dt , d^2i/dt^2 at $t=0^+$

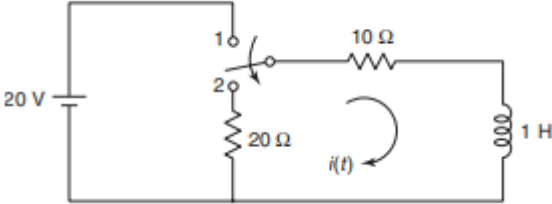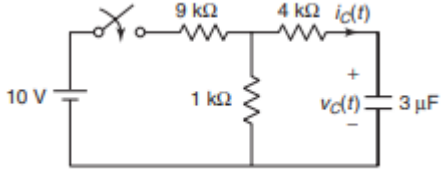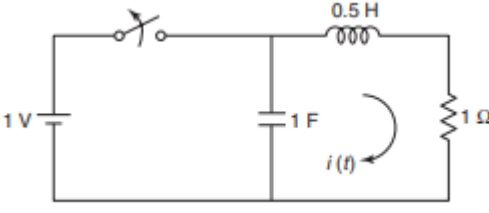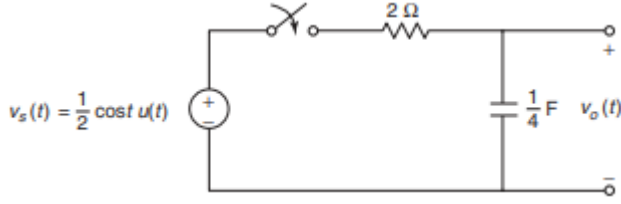	
D	<p>In the network shown in Figure, the switch closes at $t = 0$. The capacitor is initially uncharged. Find $v_c(t)$ and $i_c(t)$</p> 
E	<p>In the network shown in Figure, the switch is opened at $t = 0$. Steady-state condition is achieved before $t = 0$. Find $i(t)$</p> 
F	<p>For the network shown in Figure, find the response $v_o(t)$.</p> 

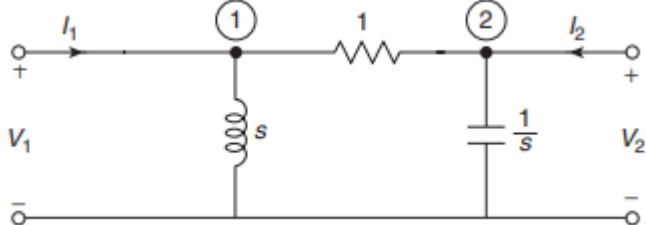Q3 (20 Marks)	
Q.3 A	Solve any Two (5 marks each)
i.	Write short note on Different types of filter
ii.	Determine the transmission parameters for the network shown in Fig.
	
iii.	Write derivation for Condition for Reciprocity
Q.3 B	Solve any One (10 marks each)
i.	a) Prove that polynomial $P(s) = s^4 + s^3 + 2s^2 + 3s + 2$ is not Hurwitz.

	b) Test whether the polynomial $P(s) = s^8 + 5s^6 + 2s^4 + 3s^2 + 1$ is Hurwitz by Routh array
ii.	Realise Foster I & Cauer I forms of the following RC impedance function $Z(s) = \frac{s+4}{(s+2)(s+6)}$

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)

Examination for Direct Second Year Students Commencing from 10th April 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2019

Examination: SE Semester III (For DSE Students)

Course Code: ELC304 and Course Name: Electrical Network Analysis and Synthesis

Time: 2 hour

Max. Marks: 80

Q1:

Question Number	Correct Option (Enter either 'A' or 'B' or 'C' or 'D')
Q1.	A
Q2.	B
Q3.	B
Q4.	A
Q5.	A
Q6.	C
Q7.	D
Q8.	C
Q9.	A
Q10.	C
Q11.	C
Q12.	B
Q13.	B
Q14.	C
Q15.	D
Q16.	B
Q17.	A
Q18.	C
Q19.	D
Q20.	A

Important steps and final answer for the questions involving numerical example

Q2(A):

Solution The equivalent circuit in terms of dependent sources is shown in Fig. 4.52.

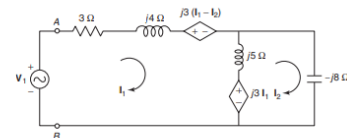


Fig. 4.52

Applying KVL to Mesh 1,

$$V_1 - 3I_1 - j4I_1 - j3(I_1 - I_2) - j5(I_1 - I_2) - j3I_1 = 0$$

$$(3 + j15)I_1 - j8I_2 = V_1 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$j3I_1 - j5(I_2 - I_1) + j8I_2 = 0$$

$$j8I_1 + j3I_2 = 0$$

$$I_2 = -\frac{j8}{j3}I_1 = -2.67I_1 \quad \dots(ii)$$

Substituting Eq (ii) in Eq (i),

$$(3 + j15)I_1 - j8(-2.67I_1) = V_1$$

$$(3 + j36.36)I_1 = V_1$$

$$Z_i = \frac{V_1}{I_1} = (3 + j36.36)\Omega = 36.48 \angle 85.28^\circ \Omega$$

Q2(B):

Solution The current I_1 leaves from the dotted end and I_2 enters from the dotted end. Hence, mutual inductance M is negative.


In the conductively coupled equivalent circuit,

$$Z_1 = j\omega(L_1 - M) = j\omega L_1 - j\omega M = j3 - j2 = j1\Omega$$

$$Z_2 = j\omega(L_2 - M) = j\omega L_2 - j\omega M = j5 - j2 = j3\Omega$$

$$Z_3 = j\omega M = j2\Omega$$

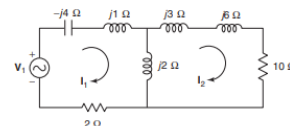The conductively coupled equivalent circuit is shown in Fig. 4.76.



Q2(C):

Solution At $t = 0^-$, the network attains steady-state condition. Hence, the capacitor acts as an open circuit.

$$v_C(0^-) = 30 \text{ V}$$

$$i(0^-) = 0$$

At $t = 0^+$, the network is shown in Fig. 6.27.

At $t = 0^+$, the capacitor acts as a voltage source of 30 V.

$$v_C(0^+) = 30 \text{ V}$$

$$i(0^+) = -\frac{30}{30} = -1 \text{ A}$$

For $t > 0$, the network is shown in Fig. 6.28.

Writing the KVL equation for $t > 0$,

$$-10i - 20i - \frac{1}{1 \times 10^{-6}} \int_0^t i \, dt - 30 = 0 \quad \dots(i)$$

Differentiating Eq. (i),

$$-30 \frac{di}{dt} - 10^6 i = 0 \quad \dots(ii)$$

$$\text{At } t = 0^+, \quad -30 \frac{di}{dt}(0^+) - 10^6 i(0^+) = 0$$

$$\frac{di}{dt}(0^+) = \frac{10^6(-1)}{30} = 0.33 \times 10^5 \text{ A/s}$$

At $t = 0^+$,

$$-30 \frac{d^2i}{dt^2}(0^+) - \frac{d^2i}{dt^2}(0^+) = 0$$

$$\frac{d^2i}{dt^2}(0^+) = 1800 \text{ A/s}^2$$

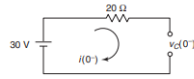


Fig. 6.26

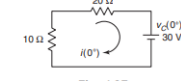


Fig. 6.27

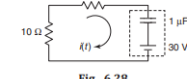


Fig. 6.28

Q2(E)

Solution At $t = 0^-$, the network is shown in Fig. 7.54. At $t = 0^-$, the switch is closed and steady-state condition is achieved. Hence, the capacitor acts as an open circuit and the inductor acts as a short circuit.

$$v_C(0^-) = 1 \text{ V}$$

$$i(0^-) = 1 \text{ A}$$

Since current through the inductor and voltage across the capacitor cannot change instantaneously,

$$v_C(0^+) = 1 \text{ V}$$

$$i(0^+) = 1 \text{ A}$$

For $t > 0$, the transformed network is shown in Fig. 7.55.

Applying KVL to the mesh for $t > 0$,

$$\frac{1}{s} - \frac{1}{s} I(s) - 0.5s I(s) + 0.5 - I(s) = 0$$

$$0.5 + \frac{1}{s} = \frac{1}{s} I(s) + 0.5s I(s) + I(s)$$

$$I(s) \left[1 + \frac{1}{s} + 0.5s \right] = 0.5 + \frac{1}{s}$$

$$I(s) = \frac{s+2}{s^2+2s+2} = \frac{(s+1)+1}{(s+1)^2+1} = \frac{s+1}{(s+1)^2+1} + \frac{1}{(s+1)^2+1}$$

Taking the inverse Laplace transform,

$$i(t) = e^{-t} \cos t + e^{-t} \sin t \quad \text{for } t > 0$$

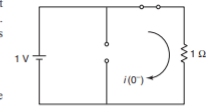


Fig. 7.54

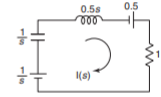


Fig. 7.55

Q2(D):

Solution At $t = 0^-$, the capacitor is uncharged. Hence, it acts as a short circuit.

$$v_C(0^-) = 0$$

$$i_C(0^-) = 0$$

At $t = 0^+$, the network is shown in Fig. 6.130.

Since voltage across the capacitor cannot change instantaneously,

$$v_C(0^+) = 0$$

$$\text{At } t = 0^+, \quad i_T(0^+) = \left[\frac{10}{9 \text{ k} + (4 \text{ k} \parallel 1 \text{ k})} \right] = \frac{10}{9.8 \text{ k}} = 1.02 \text{ mA}$$

$$i_C(0^+) = 1.02 \text{ mA} \times \frac{1 \text{ k}}{1 \text{ k} + 4 \text{ k}} = 0.204 \text{ mA}$$

For $t > 0$, the network is shown in Fig. 6.131.

For $t > 0$, representing the network to the left of the capacitor by Thevenin's equivalent network,

$$V_{\text{eq}} = 10 \times \frac{1 \text{ k}}{9 \text{ k} + 1 \text{ k}} = 1 \text{ V}$$

$$R_{\text{eq}} = (9 \text{ k} \parallel 1 \text{ k}) + 4 \text{ k} = 4.9 \text{ k}\Omega$$

For $t > 0$, Thevenin's equivalent network is shown in Fig. 6.132.

Writing the KCL equation for $t > 0$,

$$3 \times 10^{-6} \frac{dv_C}{dt} + \frac{v_C - 1}{4.9 \times 10^3} = 0$$

$$\frac{dv_C}{dt} + 68.02 v_C = 68.02$$

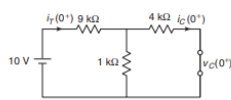


Fig. 6.130

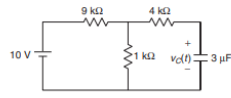


Fig. 6.131

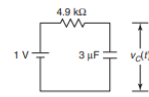


Fig. 6.132

$$\text{Comparing with the differential equation } \frac{dv}{dt} + Pv = Q,$$

$$P = 68.02, \quad Q = 68.02$$

The solution of this differential equation is given by,

$$v_C(t) = e^{-Pt} \int Q e^{Pt} dt + k e^{-Pt}$$

$$= e^{-68.02t} \int 68.02 e^{68.02t} dt + k e^{-68.02t}$$

$$= 1 + k e^{-68.02t}$$

At $t = 0, v_C(0) = 0$

$$0 = 1 + k$$

$$k = -1$$

$$v_C(t) = 1 - e^{-68.02t} \quad \text{for } t > 0$$

$$i_C(t) = C \frac{dv_C}{dt}$$

$$= 3 \times 10^{-6} \frac{d}{dt} (1 - e^{-68.02t})$$

$$= 3 \times 10^{-6} \times 68.02 e^{-68.02t}$$

$$= 204.06 \times 10^{-6} e^{-68.02t} \quad \text{for } t > 0$$

Q2(F)

Solution For $t > 0$, the transformed network is shown in Fig. 7.83.

$$V_C(s) = \frac{1}{s} - \frac{s}{2s^2+1}$$

By voltage-division rule,

$$V_C(s) = V_2(s) \times \frac{4}{2 + \frac{4}{s}} = \frac{2V_2(s)}{s+2} = \frac{s}{(s^2+2s+2)}$$

By partial-fraction expansion,

$$V_C(s) = \frac{As+B}{s^2+1} + \frac{C}{s+2}$$

$$s = (As+B)(s^2+1) + C(s^2+1)$$

$$s = (A+C)s^2 + (2A+B)s + (2B+C)$$

Comparing coefficient of s^2, s and s^0 ,

$$A+C=0$$

$$2A+B=1$$

$$2B+C=0$$

Solving the equations,

$$A = 0.4, \quad B = 0.2, \quad C = -0.4$$

$$V_C(s) = \frac{0.4s+0.2}{s^2+1} - \frac{0.4}{s+2} = \frac{0.4s}{s^2+1} + \frac{0.2}{s^2+1} - \frac{0.4}{s+2}$$

Taking the inverse Laplace transform,

$$i(t) = 0.4 \cos t + 0.2 \sin t - 0.4e^{-2t} \quad \text{for } t > 0$$

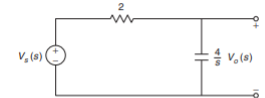


Fig. 7.83

Q3(A1):Types of filter with explanation.

Q3(A2):

Solution

Applying KCL at Node 1,

$$I_1 = \frac{V_1}{s} + (V_1 - V_2)$$

$$= \frac{s+1}{s} V_1 - V_2$$

...(i)

Applying KCL at Node 2,

$$I_2 = \frac{V_2}{s} + (V_2 - V_1)$$

$$= \frac{V_2}{s} - (s+1)V_2 + V_1$$

$$V_1 = (s+1)V_2 - I_2$$

...(ii)

Substituting Eq. (ii) in Eq. (i),

$$I_1 = \frac{s+1}{s} [(s+1)V_2 - I_2] - V_2$$

$$= \left[\frac{(s+1)^2}{s} - 1 \right] V_2 - \frac{s+1}{s} I_2$$

$$= \left(\frac{s^2+s+1}{s} \right) V_2 - \left(\frac{s+1}{s} \right) I_2 \quad \dots(\text{iii})$$

Comparing Eqs (ii) and (iii) with ABCD parameter equations,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{s+1}{s} & 1 \\ \frac{s^2+s+1}{s} & \frac{s+1}{s} \end{bmatrix}$$

Q3(A3):

9.5.1 Condition for Reciprocity

(a) As shown in Fig. 9.37, voltage V_1 is applied at the input port and the output port is short-circuited.

i.e.,

$$V_1 = V_2$$

$$V_2 = 0$$

$$I_2' = -I_2$$

From the h -parameter equations,

$$V_1 = h_{11} I_1$$

$$-I_2' = h_{21} I_1$$

$$\frac{V_1}{I_2'} = -\frac{h_{11}}{h_{21}}$$

Fig. 9.37 Network for deriving condition for reciprocity



(b) As shown in Fig. 9.38, voltage V_1 is applied at the output port with the input port short-circuited.

i.e.,

$$V_1 = 0$$

$$V_2 = V_1'$$

$$I_1 = -I_1'$$

From the h -parameter equations,

$$0 = h_{11} I_1 + h_{12} V_1'$$

$$h_{12} V_1' = -h_{11} I_1 = h_{11} I_1'$$

$$\frac{V_1'}{I_1'} = \frac{h_{11}}{h_{12}}$$

Hence, for the network to be reciprocal,

$$\frac{V_2}{I_2'} = \frac{V_1'}{I_1'}$$

$$h_{21} = -h_{12}$$

i.e.,

Fig. 9.38 Network for deriving condition for reciprocity



Solution The given polynomial contains even functions only.

$$P'(s) = 8s^7 + 30s^5 + 8s^3 + 6s$$

The Routh array is given by,

s^8	1	5	2	3	1
s^7	8	30	8	6	0
s^6	1.25	1	2.25	1	
s^5	23.6	-6.4	-0.4	0	
s^4	1.33	2.27	1		
s^3	-46.6	-18.14	0		
s^2	1.75	1			
s^1	8.49				
s^0	1				

Since there is a sign change in the first column of the array, the polynomial is not Hurwitz.

Q3(B2):

Solution

Cauer I Form The Cauer I form is obtained by continued fraction expansion of $Z(s)$ about the pole at infinity. In the above function, the degree of the numerator is less than the degree of the denominator which indicates presence of a zero at infinity. Hence, the admittance function $Y(s)$ has a pole at infinity.

$$Y(s) = \frac{s^2 + 8s + 12}{s + 4}$$

By continued fraction expansion,

$$s + 4 \left) s^2 + 8s + 12 \left(s \leftarrow Y \right.$$

$$\frac{s^2 + 4s}{4s + 12} \left) s + 4 \left(\frac{1}{4} \leftarrow Z \right.$$

$$\frac{s + 3}{12} \left) 4s + 12 \left(4s \leftarrow Y \right.$$

$$\frac{4s}{12} \left) \frac{1}{12} \leftarrow Z \right.$$

$$\frac{1}{0}$$

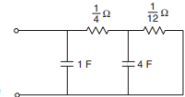


Fig. 10.55 The impedances are connected in series branches, whereas the admittances are connected in parallel branches. The network is shown in Fig. 10.55.

Foster I Form The Foster I form is obtained by partial fraction expansion of $Z(s)$.

$$Z(s) = \frac{s + 4}{(s + 2)(s + 6)}$$

By partial-fraction expansion,

$$Z(s) = \frac{K_1}{s + 2} + \frac{K_2}{s + 6}$$

where

$$K_1 = (s + 2)Z(s)|_{s=-2} = \frac{-2 + 4}{-2 + 6} = \frac{1}{2}$$

$$K_2 = (s + 6)Z(s)|_{s=-6} = \frac{-6 + 4}{-6 + 2} = \frac{1}{2}$$

$$Z(s) = \frac{1}{2} \frac{1}{s + 2} + \frac{1}{2} \frac{1}{s + 6}$$

These two terms represent the impedance of a parallel RC circuit for which

$$Z_{RC}(s) = \frac{1}{\frac{1}{R_1} + \frac{1}{sC_1}}$$

By direct comparison,

$$R_1 = \frac{1}{4} \Omega, \quad C_1 = 2 \text{ F}$$

$$R_2 = \frac{1}{12} \Omega, \quad C_2 = 2 \text{ F}$$

The network is shown in Fig. 10.56.

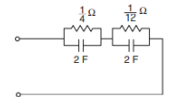


Fig. 10.56

Q3(B1-a):

Solution Even part of $P(s) = m(s) = s^4 + 2s^2 + 2$

Odd part of $P(s) = n(s) = s^3 + 3s$

$$Q(s) = \frac{m(s)}{n(s)}$$

By continued fraction expansion,

$$s^3 + 3s \left) s^4 + 2s^2 + 2 \left(s \right.$$

$$\frac{s^4 + 3s^2}{-s^2 + 2} \left) s^3 + 3s \left(-s \right.$$

$$\frac{s^3 - 2s}{5s} \left) -s^2 + 2 \left(-\frac{1}{5} s \right.$$

$$\frac{-s^2}{2} \left) 5s \left(\frac{5}{2} s \right.$$

$$\frac{5s}{0}$$

Since two quotient terms are negative, $P(s)$ is not Hurwitz.

Q3(B1-b):