

**University of Mumbai**  
**Examination 2021 under cluster 5 (Lead College: APSIT)**  
 Examinations Commencing from 10<sup>th</sup> April 2021 to 17<sup>th</sup> April 2021  
 Program: **Bachelor of Engineering**  
 Curriculum Scheme: **Electronics & Telecommunication (Rev2019 ‘C’ Scheme)**  
 Examination: **DSE Semester III**  
 Course Code: **ECC304** and Course Name: **Network Theory**

Time: 2 hour


Max. Marks: 80

<b>Q1.</b>	<b>Choose the correct option for following questions. All the Questions are compulsory and carry equal marks.</b>
1.	Which of the following conditions delivers maximum power to the load?
Option A:	$R_L > R_{TH}$
Option B:	$R_L = R_{TH}$
Option C:	$R_L < R_{TH}$
Option D:	Depends upon source.
2.	A network consists of dependent current source with value $4V_x$ . Which type of dependent source it is?
Option A:	Voltage Controlled Current Source
Option B:	Current Controlled Current Source
Option C:	Voltage Controlled Voltage Source
Option D:	Current Controlled Voltage Source
3.	Refer the following figure and determine current $I_1$ .
Option A:	0.5 A
Option B:	1 A
Option C:	2 A
Option D:	7 A
4.	Refer the following figure to find voltage $V_a$ .


Option A:	2 V
Option B:	8 V
Option C:	18 V
Option D:	1 V
5.	<p>Refer the following figure to find current <math>I_a</math>.</p>
Option A:	3 A
Option B:	2 A
Option C:	1 A
Option D:	0.5 A
6.	<p>If the graph consists of 4 nodes and 6 branches then the number of twigs and number of links are ----- and ----- respectively.</p>
Option A:	5, 5
Option B:	4, 4
Option C:	3, 4
Option D:	3, 3
7.	<p>For the graph shown in figure, the number of rows in complete incidence matrix are -----.</p>

Option A:	5
Option B:	4
Option C:	3
Option D:	6
8.	The number of maximum possible trees for a graph is calculated by -----.
Option A:	$N - 1$
Option B:	$b - (n+1)$
Option C:	$b + n - 1$
Option D:	$ AA^T $
9.	Which of the following is the correct generalized KCL equation in graph theory?
Option A:	$B \cdot Z_b \cdot B^T I_l = B \cdot V_s - B \cdot Z_b I_s$
Option B:	$Q Y_b Q^T \cdot V_t = Q I_s - Q Y_b V_s$
Option C:	$B \cdot Z_b \cdot B^T I_l = - B \cdot V_s$
Option D:	$Q Y_b Q^T \cdot V_t = Q Y_b + Q I_s V_s$
10.	Refer the following figure and determine current $i(t)$ in at $t=0^-$ .
Option A:	0 A
Option B:	1.25A
Option C:	1.1A
Option D:	1 A
11.	If $u(t)$ signal is applied to the R-C network where $R = 1 \text{ K}\Omega$ and $C = 1 \text{ }\mu\text{F}$ are connected in series. Calculate RC time constant ( $\tau$ ).
Option A:	3 $\mu\text{Sec}$
Option B:	63.2 mSec

Option C:	1 mSec
Option D:	2 mSec
12.	Time constant of a series connected R-L network is -----.
Option A:	L/R
Option B:	R/L
Option C:	Product of R and L
Option D:	LS
13.	Which of the following represent Voltage across inductors in time domain?
Option A:	$Lx \frac{di(t)}{dt}$
Option B:	$L \int i(t). dt$
Option C:	$Lxi(t)$
Option D:	$LxI(S)$
14.	If the inductor and capacitor are connected in series then equivalent impedance is ---.
Option A:	$1/LS + CS$
Option B:	$S(L+C)$
Option C:	$LS + 1/CS$
Option D:	$S^2(1+1/LC)$
15.	Pole-zero location of the transfer function T(s) is shown in the following figure. Determine T(s).
Option A:	$H x \frac{(s-1)(s-3)}{(s-2)(s-4)}$
Option B:	$H x \frac{(s-2)(s-4)}{(s-1)(s-3)}$
Option C:	$H x \frac{(s+1)(s+3)}{(s+2)(s+4)}$
Option D:	$H x \frac{(s+2)(s+4)}{(s+1)(s+3)}$
16.	A system is represented by transfer function $T(s) = \frac{18}{(s+3)(s+2)}$ , the DC gain of this system is -----.
Option A:	18
Option B:	3

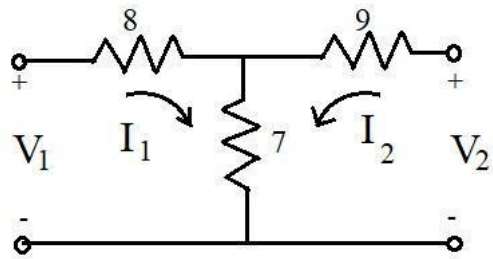Option C:	2
Option D:	6
17.	Which among the following represents the precise condition of reciprocity for transmission parameters?
Option A:	$AD-BC=1$
Option B:	$AB-CD=1$
Option C:	$AC-BD=1$
Option D:	$A=D$
18.	A two port network is represented by the following equation. $I_1 = 65 V_2 + 86 I_2$ $V_1 = 43 V_2 + 24 I_2$ A and B parameters of the networks are given by ----- and ----- respectively.
Option A:	43, 24
Option B:	65, 86
Option C:	65, -86
Option D:	43, -24
19.	Determine $Z_{11}$ and $Z_{12}$ parameters of the following network. 
Option A:	$Z_{11} = 15 \Omega, Z_{12} = -7 \Omega,$
Option B:	$Z_{11} = 17 \Omega, Z_{12} = 15 \Omega,$
Option C:	$Z_{11} = 7 \Omega, Z_{12} = 15 \Omega,$
Option D:	$Z_{11} = 15 \Omega, Z_{12} = 7 \Omega,$
20.	Z parameter of two port network are $Z_{11} = 20 \Omega, Z_{22} = 30 \Omega$ and $Z_{12}=Z_{21}=10 \Omega$ . Then the network is -----.
Option A:	Reciprocal
Option B:	Non-Reciprocal
Option C:	Symmetrical
Option D:	Neither reciprocal nor symmetrical

<b>Q2.</b>	<b>Answer the following:</b>
<b>A</b>	<b>Solve any One</b> <span style="float: right;"><b>10 marks each</b></span>
i.	<p>For the circuit shown in below, find current through <math>3 \Omega</math> using superposition theorem.</p>
ii.	<p>For the graph shown in figure find,</p> <ol style="list-style-type: none"> <li>1) Complete incidence matrix</li> <li>2) Reduced incidence matrix</li> <li>3) f-Tie-set matrix and</li> <li>4) f-Cutset matrix</li> </ol>
<b>B</b>	<b>Solve any two</b> <span style="float: right;"><b>5 marks each</b></span>
i.	<p>For the network shown in figure, plot poles and zeros function of <math>\frac{I_0}{I_i}</math>.</p>
ii.	Derive condition of symmetry for Z parameters.
iii.	Calculate number of possible trees of following graphs.

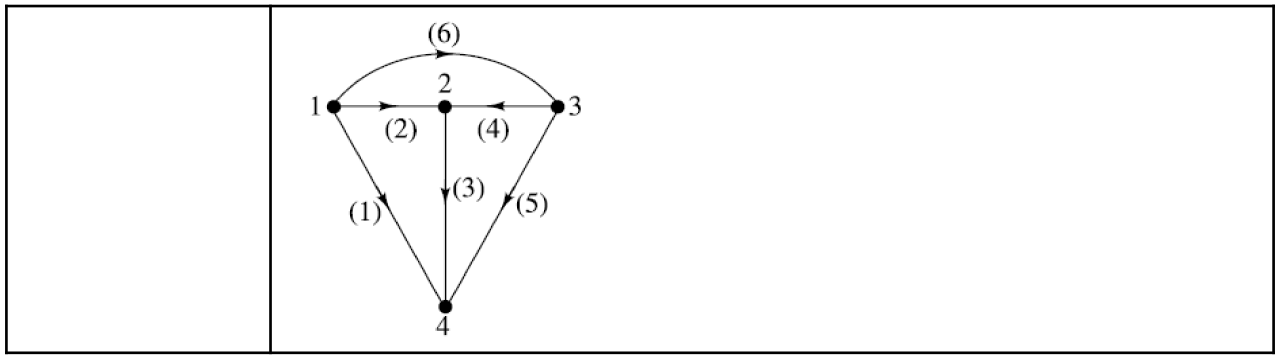

<b>Q3.</b>	<b>Answer the following :</b>
<b>A</b>	<b>Solve any One 10 marks each</b>
i.	<p>In the network shown in figure, the switch was at 1<sup>st</sup> position for a long time and then it is moved to 2<sup>nd</sup> position at <math>t=0</math>. Determine <math>V_c(t)</math>.</p>
ii.	<p>Determine ABCD parameter for the network shown in figure.</p>
<b>B</b>	<b>Solve any One 10 marks each</b>
i.	<p>The switch in the network shown was opened for a long time, then it is closed at <math>t = 0</math>. Determine the voltage across the capacitor using Laplace.</p>
ii.	<p>Write any five necessary conditions for driving point functions and transfer functions.</p>

**University of Mumbai**

**Examination 2021 under cluster 5 (Lead College: APSIT)**

**Examinations Commencing from 10<sup>th</sup> April 2021 to 17<sup>th</sup> April 2021**

**Program: Bachelor of Engineering**

**Curriculum Scheme: Electronics & Telecommunication (Rev2019 'C' Scheme)**

**Examination: DSE Semester III**

**Course Code: ECC304 and Course Name: Network Theory**

Time: 2 hour

Max. Marks: 80

---

---

<b>Question Number</b>	<b>Correct Option (Enter either 'A' or 'B' or 'C' or 'D')</b>
Q1.	B
Q2.	A
Q3.	C
Q4.	D
Q5.	B
Q6.	D
Q7.	C
Q8.	D
Q9.	B
Q10.	B
Q11.	C
Q12.	A
Q13.	A
Q14.	C
Q15.	C
Q16.	B
Q17.	A
Q18.	D
Q19.	D
Q20.	A