

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)

Examinations Commencing from June 01, 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2019

Examination: SE Semester IV

Course Code: ELC402 and Course Name: Electronic Devices and Circuits-II

Time: 2 hour



Max. Marks: 80

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	Which capacitors assists in preventing the loss of gain due to negative feedback without affecting the DC stability of R-C Coupled amplifier?
Option A:	Coupling capacitors (Cc)
Option B:	Bypass capacitors (Cs)
Option C:	Internal Capacitance Cgd
Option D:	Internal Capacitance Cgs
2.	An amplifier has an input signal voltage of 0.054 mV. The output voltage is 12.5 V. The voltage gain in dB is....
Option A:	53.6 dB.
Option B:	107.3 dB.
Option C:	231 dB.
Option D:	116 dB.
3.	A certain amplifier has a bandwidth of 22.5 kHz with a lower cutoff frequency of 600 Hz. What is the value of upper cut-off frequency?
Option A:	600 Hz
Option B:	22.5 kHz
Option C:	23.1 kHz
Option D:	21.9 kHz
4.	In Current Shunt Negative feedback topology.....
Option A:	Ri Increases and Ro Decreases
Option B:	Ri Increases and Ro Increases
Option C:	Ri Decreases and Ro Decreases
Option D:	Ri Decreases and Ro Increases
5.	An amplifier has a Rin = 1.2 kΩ. The coupling capacitor is 1 μF. Determine the approximate lower cutoff frequency.
Option A:	132.62 Hz
Option B:	1.33 kHz
Option C:	13.3 kHz
Option D:	133.55 kHz
6.	The gain of an amplifier without feedback is 100 db. If a negative feedback of 3 db is applied, the gain of the amplifier will become

Option A:	5 db
Option B:	300 db
Option C:	103 db
Option D:	97 db
7.	In Voltage Shunt Negative feedback topology.....
Option A:	Ri Increases and Ro Decreases
Option B:	Ri Increases and Ro Increases
Option C:	Ri Decreases and Ro Decreases
Option D:	Ri Decreases and Ro Increases
8.	If a three-stage amplifier has individual stage gains of 10 db, 5 db and 12 db, then total gain in db is
Option A:	600 db
Option B:	24 db
Option C:	14 db
Option D:	27 db
9.	The frequency of oscillations in an LC oscillator is L or C.
Option A:	Inversely proportional to square root of
Option B:	Directly proportional to
Option C:	Proportional to square of
Option D:	Independent of the values of
10.	The total gain of a multistage amplifier is less than the product of the gains of individual stages due to
Option A:	Power loss in the coupling device
Option B:	Loading effect of the next stage
Option C:	The use of many transistors
Option D:	The use of many capacitors
11.	If, $\Theta_{JC}=1.5\text{ }^{\circ}\text{C/W}$, $\Theta_{CS}=1\text{ }^{\circ}\text{C/W}$, $\Theta_{SA}=4\text{ }^{\circ}\text{C/W}$, $\Theta_{CA}=50\text{ }^{\circ}\text{C/W}$, $T_{J\text{Max}}=100\text{ }^{\circ}\text{C}$ and $T_{\text{AMB}}=25\text{ }^{\circ}\text{C}$, then Maximum power dissipation with and without Heat Sink will be.....
Option A:	16.75W, 2.45W
Option B:	18.75W, 1.45W
Option C:	20.75W, 3.45W
Option D:	19.25W, 2.45W
12.	Phase shift provided by each one phase shift network in RC Phase Oscillator in 3 stage RC network is
Option A:	90 degrees
Option B:	180 degrees
Option C:	60 degrees
Option D:	120 degrees
13.	Maximum Power Conversion Efficiency of transformed coupled Class-A Power Amplifier is.....
Option A:	75%
Option B:	25%

Option C:	50%
Option D:	100%
14.	In Class-B Power Amplifier, Q-Point is located at.....
Option A:	Cut-off Point
Option B:	Saturation Point
Option C:	Middle of the DC Load Line
Option D:	After Cut-off Point
15.	If a power amplifier having zero signal power dissipation of 5 watts and a.c. power output of 2 watts, What will be the collector efficiency?
Option A:	20%
Option B:	40%
Option C:	80%
Option D:	50%
16.	What is the meaning of Dual Input Balanced Output?
Option A:	Output is measured between collectors of any one transistor and the Differential amplifier with two input signals
Option B:	Output is measured between two collectors of transistors and the Differential amplifier with two input signals
Option C:	Output is measured between collector of first transistor and the Differential amplifier with two input signals
Option D:	Output is measured between collector of second transistor and the Differential amplifier with two input signals
17.	A Differential Amplifier should have collector resistor's value (R_{C1} & R_{C2}) as....
Option A:	$10k\Omega$, $15k\Omega$
Option B:	$15k\Omega$, $10k\Omega$
Option C:	$15k\Omega$, $15k\Omega$
Option D:	15Ω , $15k\Omega$
18.	The value of emitter resistance in Emitter Biased circuit are $R_{E1}=25k\Omega$ & $R_{E2}=20k\Omega$. Find R_E
Option A:	$45k\Omega$
Option B:	$11.11k\Omega$
Option C:	$5.11k\Omega$
Option D:	$100k\Omega$
19.	One of the most important condition to get sustained oscillation is
Option A:	A phase shift around the feedback loop of 0 degree or 360 degree
Option B:	A phase shift around the feedback loop of 180 degree
Option C:	A gain around the feedback loop of one-third
Option D:	A gain around the feedback loop of less than 1
20.	Why the size of Power MOSFET is made considerably large?
Option A:	To provide easy handling
Option B:	To dissipate Maximum Heat
Option C:	To get maximum Efficiency
Option D:	To facilitate connections

Q2 (20 Marks)	Solve any Four Questions out of Six	05 Marks each
A	Explain high frequency equivalent circuit of MOSFET.	
B	Draw and explain the working principle of CASCODE amplifier using MOSFET.	
C	What are the advantages and dis-advantages of negative feedback?	
D	State and explain Barkhausen's criterion.	
E	Draw the MOSFET differential amplifier with active load.	
F	Draw and explain the working of Class-AB output stage with diode biasing	

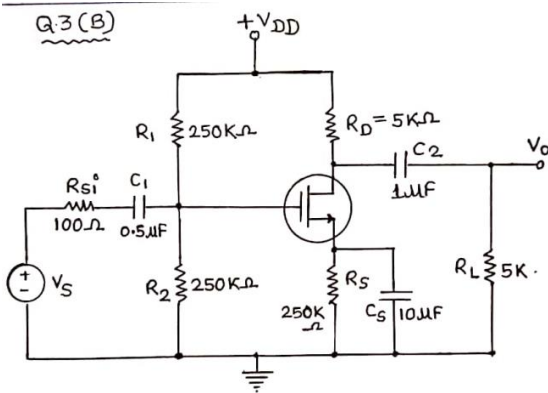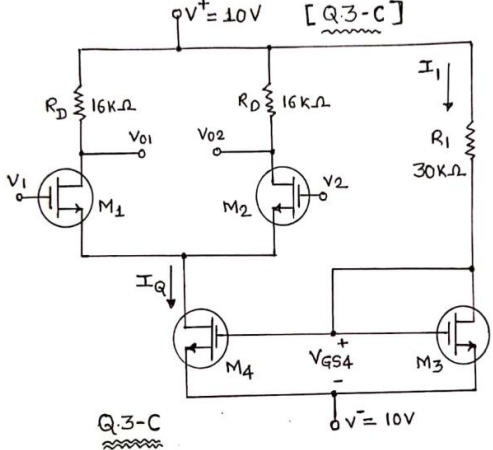Q3 (20 Marks)	Solve any Two Questions out of Three	10 marks each
A	Draw transformer coupled Class-A Power amplifier and load line, derive the maximum power conversion efficiency for the same.	
B	<p>For the CS MOSFET amplifier shown in figure below, calculate the values of f_H and f_L. Assume the following values for the MOSFET. $C_{gd}=2\text{pF}$, $C_{gs}=5\text{pF}$, $R_{si}=100\Omega$, $g_m=10\text{mS}$, $C_1=0.5\mu\text{F}$, $C_2=1\mu\text{F}$, $C_s=10\mu\text{F}$, $R_1=R_2=250\text{k}\Omega$, $R_D=5\text{k}\Omega$, $R_S=250\text{k}\Omega$ and $R_L=5\text{k}\Omega$</p> 	
C	<p>For the MOSFET differential amplifier, the transistor parameters are $K_{n1}=K_{n2}=0.1\text{mA/V}^2$, $K_{n3}=K_{n4}=0.3\text{mA/V}^2$, $V_{TN}=1\text{V}$ for all MOSFET's. $\lambda=0$ for M1, M2 and M3 and $\lambda=0.01\text{V}^{-1}$ for M4. Determine the bias current I_Q, O/P resistance of current source, A_d, A_{CM} and $CMRR$</p> 	

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)

Examination Commencing from June 01, 2021

Program: Electronics Engineering

Curriculum Scheme: Rev 2019

Examination: SE Semester IV

Course Code: ELC402 and Course Name: Electronic Devices and Circuits-II

Time: 2 hour

Max. Marks: 80

Q1:

Question Number	Correct Option (Enter either 'A' or 'B' or 'C' or 'D')
Q1.	B
Q2.	B
Q3.	C
Q4	D
Q5	A
Q6	D
Q7	C
Q8.	D
Q9.	A
Q10.	B
Q11.	B
Q12.	C
Q13.	C
Q14.	A
Q15.	B
Q16.	B
Q17.	C
Q18.	B
Q19.	A
Q20.	B

Important steps and final answer for the questions involving numerical example

Q3(B):

<p><u>Q-3-B :-</u></p> <p>* <u>Part-I :- Low Freq Response</u></p> <p><u>Step:1</u></p> <p>① <u>Time Constant of C_1 :- τ_{S1}</u></p> <p>* <u>Effective Resistance seen by C_1</u> $\therefore R_{C1} = 125.1 \text{ k}\Omega = R_{S1} + R_G$</p> <p>$\therefore \tau_{S1} = R_{C1} \cdot C_1 = 0.06255 \text{ sec} - \text{①}$</p> <p>② <u>Time Constant of C_2 :- τ_{S2}</u></p> <p>* <u>Effective Resistance seen by C_2</u> $\therefore R_{C2} = R_D + R_L = 10 \text{ k}\Omega$</p> <p>$\therefore \tau_{S2} = R_{C2} \cdot C_2 = 0.01 \text{ sec} - \text{②}$</p> <p>③ <u>Time Constant of C_5 :- τ_{CS}</u></p> <p>* <u>Effective Resistance seen by C_5</u> $\therefore R_{CS} = R_S \parallel \frac{1}{g_m}$</p> <p>$\therefore R_{CS} = 71.43 \Omega$</p> <p>$\therefore \tau_{CS} = R_{CS} \cdot C_5 = 7.143 \times 10^{-4} \text{ sec} - \text{③}$</p> <p><u>Step:2</u></p> <p><u>:- Find Lower cut-off freq f_L :-</u> will be the corresponds to the smallest time constant of C_1, C_2 & C_5</p>	<p>$\therefore \tau_{CS}$ is the smallest, so select τ_{CS} to find f_L</p> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 5px auto;"> $\therefore f_L = \frac{1}{2\pi \tau_{CS}} = 222.82 \text{ Hz}$ </div> <p>* <u>Part-II :- High Freq Response</u></p> <p>* <u>Step 1 :- Draw the high Freq equi-ckt.</u></p> <p>* <u>Step 2 :- Time constant of C_{GS} :- τ_{CS}</u></p> <p>* <u>Effective Resistance seen by C_{GS} :- R_{CS}</u> $\therefore R_{CS} = R_S \parallel R_G = 99.9 \Omega$</p> <p>$\therefore \tau_{CS} = R_{CS} \cdot C_{GS} = 0.4996 \text{ nsec} \approx 0.5 \text{ nsec}$</p> <p>* <u>Step 3 :- Time constant of C_{GD} :- τ_{CGD}</u></p> <p>* <u>Effective Resistance seen by C_{GD} :- R_{CGD}</u> $\therefore R_{CGD} = 5.1 \text{ k}\Omega$</p> <p>$\therefore \tau_{CGD} = R_{CGD} \cdot C_{GD} = 10.2 \text{ nsec}$</p> <p>* <u>Step 4 :- Find the Higher cut-off freq f_H</u> :- will be the highest time constants out of τ_{CS} and τ_{CGD}</p> <p>$\therefore \tau_{CGD}$ has the highest time constant.</p> <p>\therefore Select τ_{CGD} to calculate f_H</p> <p>\therefore <u>Higher cut-off freq - $f_H = \frac{1}{2\pi \tau_{CGD}}$</u></p> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 5px auto;"> $\therefore f_H = 15.6 \text{ MHz}$ </div>
--	---

Q3(C):

<p><u>Q-3-C :- Solution</u></p> <p>* <u>Step-1 :- calculate I_1 & V_{GS4}</u></p> <p>$\therefore V_{GS4} = 2.4 \text{ V}$</p> <p>$\therefore I_1 = 0.588 \text{ mA}$</p> <p>* <u>Step-2 :- Calculate I_Q</u></p> <p>$\therefore I_Q = I_1 = 0.588 \text{ mA}$</p> <p>* <u>Step-3 :- Calculate R_0</u></p> <p>$R_0 = \frac{1}{\lambda I_Q}$</p> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 5px auto;"> $\therefore R_0 = 170.068 \text{ k}\Omega$ </div>	<p>* <u>Step-4 :- Calculate A_d</u></p> <p>$A_d = \sqrt{\frac{K_n I_Q}{2}} \times R_D = \sqrt{\frac{0.1 \times 0.588}{2}} \times 16$</p> <p>$\therefore A_d = 2.74$</p> <p>* <u>Step-5 :- Calculate A_{cm}</u></p> <p>$A_{cm} = -0.047$</p> <p>* <u>Step-6 :- Calculate CMRR</u></p> <p>$CMRR = \left \frac{A_d}{A_{cm}} \right = \left \frac{2.74}{-0.047} \right$</p> <p>$\therefore CMRR = 58.29$</p> <p>$\therefore [CMRR]_{dB} = 20 \log_{10} 58.29$</p> <p>$\therefore [CMRR]_{dB} = 35.31 \text{ dB}$</p>
--	---