

# University of Mumbai

Examination June 2021

Examinations Commencing from 15<sup>th</sup> June 2021 to 26<sup>th</sup> June 2021

Program: Bachelor of Engineering

Curriculum Scheme: Electronics & Telecommunication (Rev2019 'C' Scheme)

Examination: DSE Semester III

Course Code: ECC302 and Course Name: Electronic Devices & Circuits


Time: 2 hour

Max. Marks: 80

<b>Q1.</b>	<b>Choose the correct option for following questions. All the Questions are compulsory and carry equal marks</b>
1.	In AC load line, slope is generally
Option A:	Greater than slope of DC load line
Option B:	Less than slope of DC load line
Option C:	Same as that of DC load line
Option D:	Greater than as well as less than slope of DC load line
2.	In AC load line ,the slope is represented by an equation is
Option A:	$Y = -1 / R_{ac}$
Option B:	$Y = 1 / R_{ac}$
Option C:	$Y = -1 / R_L$
Option D:	$Y = 1 / R_L$
3.	A transistor with $\beta = 120$ is biased to operate at a dc collector current of 1.2 mA. Find the value of $r_{\pi}$ .
Option A:	2.2 K $\Omega$
Option B:	2.35 K $\Omega$
Option C:	2.5 K $\Omega$
Option D:	2.45 K $\Omega$
4.	The SI units of transconductance is
Option A:	Volt/ Ampere
Option B:	Ohm
Option C:	Siemens
Option D:	Ampere/ Volt
5.	The enhancement MOSFET is
Option A:	Normally open MOSFET
Option B:	Useful as a very good constant voltage source
Option C:	Widely used because of easy in its fabrication
Option D:	Normally close MOSFET
6.	A CS amplifier has a voltage gain of
Option A:	$g_m (r_d    R_D)$
Option B:	$g_m r_d$

Option C:	$g_m R_s$
Option D:	$g_m r_s / (1 + g_m r_s)$
7.	For which of the following frequency region(s) can the coupling and bypass capacitors no longer be replaced by the short-circuit approximation?
Option A:	Low-frequency
Option B:	Mid-frequency
Option C:	High-frequency
Option D:	All frequency
8.	What is the normalized gain expressed in dB for the cut-off frequencies?
Option A:	-3 dB
Option B:	+3 dB
Option C:	-6 dB
Option D:	-20 dB
9.	The larger capacitive elements of the design will determine the _____ frequency.
Option A:	Lower cut off
Option B:	Middle
Option C:	Higher cut off
Option D:	Intermediate
10.	What is the ratio of the capacitive reactance $X_{CS}$ to the input resistance $R_i$ of the input RC circuit of a single-stage BJT amplifier at the low-frequency cut-off?
Option A:	0.25
Option B:	0.50
Option C:	0.75
Option D:	1.0
11.	Which of the lower cutoff -frequency determined by $C_{in}$ , $C_{out}$ , and $C_E$ will be the predominant factor in determining the low-frequency response for the complete system?
Option A:	Lowest
Option B:	Middle
Option C:	Highest
Option D:	Average
12.	Which of the following elements is (are) important in determining the gain of the system in the high-frequency region?
Option A:	Coupling capacitances
Option B:	Bypass capacitances
Option C:	Transconductance
Option D:	Inter-electrode, wiring and miller effect capacitances
13.	In a multistage amplifier, the overall frequency response is determined by the
Option A:	Frequency response of each stage depending on the relationships of the critical frequencies.
Option B:	Frequency response of the first amplifier.

Option C:	Frequency response of the last amplifier.
Option D:	Lower critical frequency of the first amplifier and the upper critical frequency of the final amplifier.
14.	In the mid frequency region, coupling capacitor acts as a _____ circuits and stray capacitance acts as a _____ circuits.
Option A:	Open, Short
Option B:	Short, Open
Option C:	Short, Short
Option D:	Open, Open
15.	Differential Amplifier amplifies
Option A:	Input signal with higher voltage
Option B:	Input voltage with smaller voltage
Option C:	Sum of the input voltage
Option D:	Difference between the input voltage
16.	If output is measured between two collectors of transistors, then the Differential amplifier with two input signal is said to be configured as
Option A:	Dual Input Balanced Output
Option B:	Dual Input Unbalanced Output
Option C:	Single Input Balanced Output
Option D:	Single Input Unbalanced Output
17.	To increase the value of CMRR, which circuit is used to replace the emitter resistance $R_E$ in differential amplifiers?
Option A:	Constant current bias
Option B:	Resistor in parallel with $R_E$
Option C:	Resistor in series with $R_E$
Option D:	Diode in parallel with $R_E$
18.	The input stage of an op amp is usually a
Option A:	Swamped amplifier
Option B:	Class B push-pull amplifier
Option C:	CE amplifier
Option D:	Differential amplifier
19.	Class _____ power amplifier has highest collector efficiency
Option A:	A
Option B:	B
Option C:	C
Option D:	AB
20.	The maximum efficiency of transformer coupled class A power amplifier is
Option A:	78.5 %
Option B:	50%
Option C:	30%
Option D:	25%

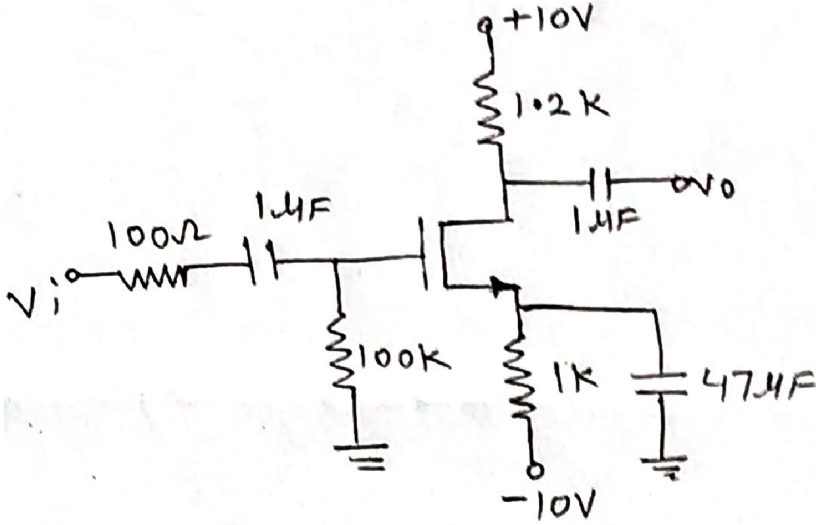Q2	Solve any Two Questions out of Three	10 marks each
A	Explain the concept of multistage amplifier with advantage, disadvantage and application.	
B	<p data-bbox="422 387 1422 533">For the circuit shown in Fig. 1, Transistor parameters are <math>K_n = 1 \text{ mA/V}^2</math>, <math>V_{tn} = 0.7 \text{ V}</math>, <math>C_{gs} = 2 \text{ pF}</math>, <math>C_{gd} = 0.2 \text{ pF}</math>, <math>\lambda = 0</math>, find the mid band voltage gain, miller capacitance and upper cut-off frequency.</p>  <p data-bbox="1027 1111 1094 1137">Fig.1</p>	
C	Draw a small signal equivalent structure of Diff-amp and derive the equation for its CMRR.	

Q3.	Solve any Two Questions out of Three	10 marks each
A	Derive the equation of $A_v$ , $Z_i$ and $Z_o$ of CE amplifier using un-bypass $R_E$ .	
B	Explain the effects of coupling, bypass capacitor and parasitic capacitor on frequency response of single stage amplifier.	
C	Draw a neat diagram of a transformer coupled Class A power amplifier and explain its working, hence find its efficiency.	

**University of Mumbai**

**Examination June 2021**

**Examinations Commencing from 15<sup>th</sup> June 2021 to 26<sup>th</sup> June 2021**

**Program: Bachelor of Engineering**

**Curriculum Scheme: Electronics & Telecommunication (Rev2019 'C' Scheme)**

**Examination: DSE Semester III**

**Course Code: ECC302 and Course Name: Electronic Devices & Circuits**

Time: 2 hour

Max. Marks: 80

---

---

<b>Question Number</b>	<b>Correct Option (Enter either 'A' or 'B' or 'C' or 'D')</b>
Q1.	A
Q2.	A
Q3.	C
Q4.	D
Q5.	A
Q6.	A
Q7.	A
Q8.	A
Q9.	A
Q10.	D
Q11.	C
Q12.	D
Q13.	A
Q14.	B
Q15.	D
Q16.	A
Q17.	A
Q18.	D
Q19.	C
Q20.	B

