

**K. J. Somaiya Institute of Engineering and Information Technology, Sion,
Mumbai-22**

(Autonomous College Affiliated to University of Mumbai)

End Semester Exam

Nov – Dec 2021

Program: B.Tech

Examination: SY Semester: III

Course Code: IUEX303 and Course Name: Electronic Devices and Circuits

Duration: 03 Hours

Max. Marks: 60

Instructions:

- (1) All questions are compulsory.
- (2) Draw neat diagrams wherever applicable.
- (3) Assume suitable data, if necessary.

		Max. Mar ks	CO	BT level
Q 1	Solve any six questions out of eight:	12		
i)	State the mathematical equation of PN junction diode current.	2	CO3	U
ii)	Define differential mode gain and common mode gain.	2	CO2	U

iii)	Differentiate class A, class B power amplifier	2	CO6	Ap
iv)	Draw hybrid pi model of BJT.	2	CO3	U
v)	Explain the concept of DC load line.	2	CO2	U
vi)	Draw symbol of N- MOSFET and P- MOSFET	2	CO2	R
vii)	Compare self bias and fixed bias (BJT biasing).	2	CO2	Ap
viii)	If a transistor has beta 100, base current is 50 microampere then find emitter current and collector current.	2	CO3	Ap
Q.2	Solve any four questions out of six.	16		
i)	What is crossover distortion and suggest a solution over it.	4	CO2	Ap
ii)	Compare E- MOSFET with D-MOSFET.	4	CO3	Ap
iii)	What is biasing? Explain the need of biasing.	4	CO4	U
iv)	Explain the effect of bypass capacitor and parasitic capacitance on frequency response of an amplifier	4	CO5	U
v)	Draw and explain the energy band diagram of BJT.	4	CO1	U
vi)	Find the position of Q point if $\beta = 100$, $R_1 = 39k\Omega$, $R_2 = 3.9k\Omega$, $R_C = 10k\Omega$, $R_E = 1.5k\Omega$, $V_{CC} = 22V$. (Voltage divider biasing)	4	CO2	Ap

Q.3	Solve any two questions out of three.	16		
i)	What is line and load regulation? Explain the working of zener diode regulator with varying load resistance and varying input voltage.	8	CO2	U
ii)	Explain the terms drift and diffusion current density. Calculate drift current density for given semiconductor. Consider silicon at $T=300\text{K}$ doped with arsenic atoms at a concentration of $N_D=8 \times 10^{15} \text{cm}^{-3}$. Assume mobility values of $\mu_n=1350 \text{cm}^2/\text{V}\cdot\text{S}$ $\mu_p=480 \text{cm}^2/\text{V}\cdot\text{S}$. Assume the applied electric field is $100 \text{V}/\text{cm}$.	8	CO1	Ap
iii)	Design the bias of a MOSFET circuit such that Q point is in the middle of the saturation region and $I_{DQ}=2\text{mA}$. Determine the resulting small signal voltage gain. Refer Figure 1. Let $R_1 \parallel R_2=100\text{K}\Omega$. A transistor with parameters $V_{TO}=1\text{V}$, $k_n'=80\mu\text{A}/\text{V}^2$, $W/L=25$ and $\lambda=0.015\text{V}^{-1}$ is available.	8	CO5	Ap
Figure 1				
Q.4	Solve any two questions out of three.	16		
i)	Calculate the maximum gain of a bipolar common emitter circuit with coupling capacitor. For the circuit shown in Figure.2 Parameters are $R_1=51.2\text{K}\Omega$, $R_2=2\text{K}$, $R_E=0.4\text{K}$, $R_{Si}=0.1\text{K}$, $C_C=1\mu\text{F}$ and $V_{CC}=10\text{V}$. The transistor parameter are: $V_{BE(\text{on})}=0.7\text{V}$, $\beta=100$, and	8	CO4	Ap

$V_A = \infty$.

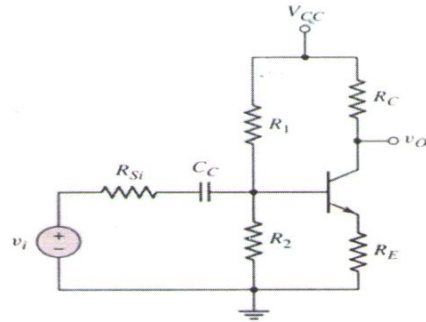


Figure 2

ii)

Derive for the corner frequency and maximum gain of a bipolar common emitter circuit with coupling capacitor. For the circuit shown in Figure 3.

8

CO3

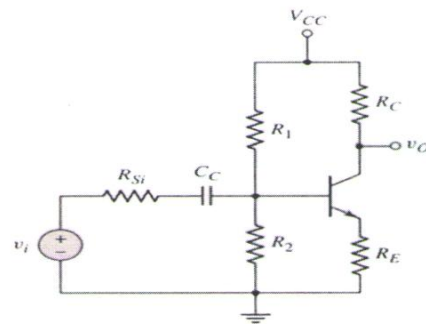


Figure 3

iii)

Derive the expression of CMRR for differential amplifier using E-MOSFET.

8

CO6

Ap