

K. J. Somaiya Institute of Engineering and Information Technology, Sion, Mumbai-22

(Autonomous College Affiliated to University of Mumbai)

(DEC-21) Feb-2022

Program: B.Tech *EATC*

Examination: SY Semester: III

Course Code: 1UEX303 and Course Name: Electronic Devices and Circuits


Duration: 03 Hours



Max. Marks: 60


Instructions:

- (1) All questions are compulsory.
- (2) Draw neat diagrams wherever applicable.
- (3) Assume suitable data, if necessary.

		Max. Marks	CO	BT level
Q 1	Solve any six questions out of eight	12		
i)	Illustrate Drain Characteristics of E-MOSFET with graph.	2	2	U
ii)	Derive for Transfer function of series coupling RC circuit.	2	2	U
iii)	Define diode current equation.	2	1	U
iv)	Illustrate ac equivalent model of MOSFET with circuit diagram.	2	1	U
v)	Define Channel Length Phenomenon in MOSFET.	2	1	U

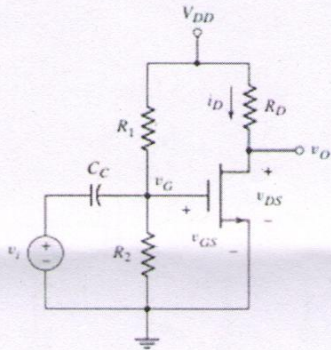vi)	Draw symbol of N- MOSFET and P- MOSFET	2	1	U
vii)	For a MOSFET circuit, If expression for I_D is $I_D = K_n(V_{GS} - V_{to})^2$ Then Derive for gm.	2	1	U
viii)	Define differential mode gain and common mode gain.	2	2	U
Q.2	Solve any four questions out of six.	16		
i)	Illustrate transfer characteristic with various region of operation using graph and current equation.	4	1	U
ii)	Explain the working of E- MOSFET with constructional detail	4	1	U
iii)	Compare low and high frequency ac model of MOSFET.	4	3	AP
iv)	MOSFET can act as current source. Justify the statement	4	3	AP
v)	Analyze circuit in given figure to find DC voltages and current. <div style="text-align: center;">  </div> <p style="text-align: center;">Figure 1</p>	4	4	AN
vi)	Compare Rectifier diode with Zener diode.	4	3	AP

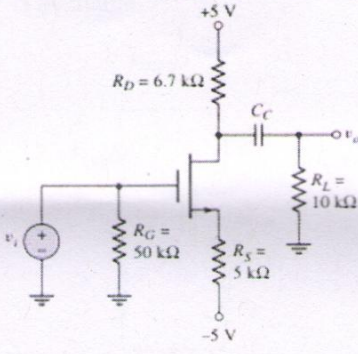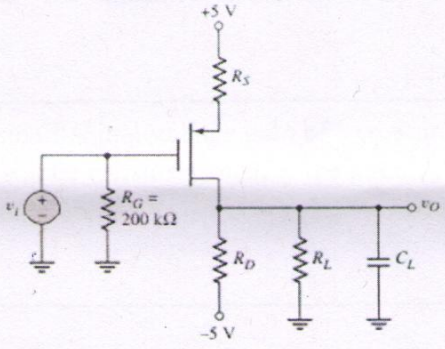Q.3	Solve any two questions out of three	16		
i)	Analyze effect of Miller's capacitance on frequency response of CS amplifier ?	8	4	AN
ii)	<p>The circuit in Figure is to be used as a simple audio amplifier. Design the circuit such that the lower corner frequency is $f_L = 50$ Hz.</p>  <p style="text-align: center;">Figure 2</p>	8	5	AP
iii)	<p>Determine the corner frequency and maximum gain asymptote of a MOSFET amplifier. For the circuit in Figure the parameters are: $R_S = 3.2$ k , $R_D = 10$ k , $R_L = 20$ k , and $C_L = 10$ pF. The transistor parameters are: $V_{TP} = -2$ V, $K_P = 0.25$ mA/V², and $\lambda = 0$. $I_{DQ} = 0.5$ mA, $V_{SGQ} = 3.41$ V, and $V_{SDQ} = 3.41$ V.</p>  <p style="text-align: center;">Figure 3</p>	8	4	AN

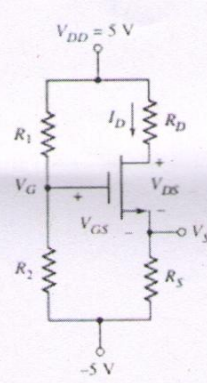Q.4	Solve any two questions out of three.	16		
i)	<p>Design the dc bias of a MOSFET circuit to meet a set of specifications. The circuit configuration to be designed is shown in Figure. The quiescent Q-point values are to be $I_{DQ} = 0.25\text{mA}$, $V_{DSQ} = 4\text{V}$. The voltage across R_S should be $V_{RS} \approx 1\text{V}$. The current in the bias resistors should be approximately $20\ \mu\text{A}$. A transistor with parameters of $k'_n = 80\ \mu\text{A}/\text{V}^2$, $W/L = 4$, and $V_{TN} = 1.2\text{V}$ is available.</p>  <p style="text-align: center;">Figure 4</p>	8	5	AP
ii)	<p>Explain the terms diffusion current density. Calculate diffusion current density for given semiconductor. Consider silicon at $T=300\text{K}$. Assume the electron concentration varies linearly from $n=10^{12}\text{cm}^{-3}$ to $n=10^{16}\text{cm}^{-3}$ over the distance from $x=0$ to $x=3\ \mu\text{m}$. Assume $D_n=35\text{cm}^2/\text{s}$.</p>	8	1	U
iii)	<p>Determine the small-signal voltage gain of a common-source circuit containing a source resistor. Consider the circuit in Figure. The transistor parameters are $V_{TN} = 0.8\text{V}$, $K_n = 1\text{mA}/\text{V}^2$ and $\lambda = 0$.</p>	8	4	AN

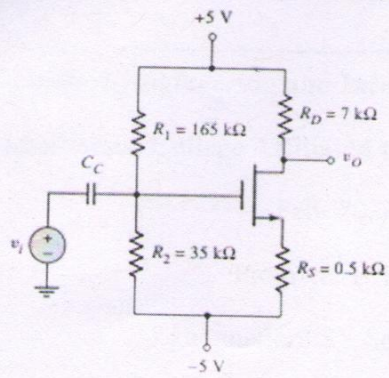


Figure 5