

K. J. Somaiya Institute of Technology, Sion, Mumbai-22
(Autonomous College Affiliated to University of Mumbai)

April – May 2023

(B. Tech) Program: B. Tech. (Electronics and Telecommunication) Scheme: II

Examination: LY Semester: VIII

Course Code: **EXDLC8032** and Course Name: **RF DESIGN**

Date of Exam: 18.05.2023

Duration: 2.5 Hours

Max. Marks: 60

Instructions:

- (1). All questions are compulsory.
- (2). Draw neat diagrams wherever applicable.
- (3). Assume suitable data, if necessary.

		Max. Marks	CO	BT level
Q 1	Solve any six questions out of eight:	12		
i)	Draw the final four stage diagram of composite filter and Compare the high pass and low pass composite filter design?	2	1	U
ii)	Calculate the number of elements (N) required to design maximally low pass filter with a cut off frequency of 2 GHz, source and load impedance of 50 Ω and this LPF is having 30 dB decay in amplitude at 4 GHz.	2	1	Ap
iii)	Define: Stability, power gain, available power gain and transducer power gain.	2	2,6	U
iv)	Draw the signal flow graph for linear two port microwave network?	2	2	U
v)	Explain the Kurokawa's criterion for oscillations?	2	3	U
vi)	Justify how field effect transistor (FET) can be used as mixer.	2	4	U
vii)	Explain EMI and its sources.	2	5	U
viii)	What are the three criteria to be satisfied by any system to become electromagnetically compatible?	2	5	U
Q.2	Solve any four questions out of six.	16		
i)	One-port oscillator uses a negative resistance diode having $\Gamma_{in} = 1.25 \angle 40^\circ$ ($Z_0 = 50 \Omega$) at its desired operating point, for $f = 6$ GHz. Calculate a load matching network (Z_L) for a 50 Ω load impedance.	4	3	Ap
ii)	Write a short notes on insertion loss method of filter design?	4	1	U
iii)	A silicon bipolar junction transistor has the following scattering parameters at 1.0 GHz, with a 50 Ω reference impedance: $S_{11} = 0.38 \angle -158^\circ$ $S_{12} = 0.11 \angle 54^\circ$ $S_{21} = 3.50 \angle 80^\circ$ $S_{22} = 0.40 \angle -43^\circ$ The source impedance is $Z_S = 25 \Omega$ and the load impedance is $Z_L = 40 \Omega$.	4	2	Ap

K. J. Somaiya Institute of Technology, Sion, Mumbai-22
(Autonomous College Affiliated to University of Mumbai)

April – May 2023

(B. Tech) Program: B. Tech. (Electronics and Telecommunication) Scheme: II
Examination: LY Semester: VIII

Course Code: EXDLE8032 and Course Name: RF DESIGN

Date of Exam: 18.05.2023

Duration: 2.5 Hours

Max. Marks: 60

	Compute the power gain, the available power gain, and the transducer power gain.																																																																																																																																							
iv)	Define: 1-dB compression point, dynamic range, conducted and radiation emission.	4	2,5	U																																																																																																																																				
v)	What do you mean by “EMI Quantification” and give different considerations for the same.	4	5	U																																																																																																																																				
vi)	Compare single ended and balanced mixer.	4	4	U																																																																																																																																				
Q.3	Solve any two questions out of three.	16																																																																																																																																						
i)	Design a maximally flat low-pass filter with a cutoff frequency of 2 GHz, impedance of 50 Ω, and at least 15 dB insertion loss at 3 GHz. (Use Table for ref.) <table border="1"> <caption>TABLE Element Values for Maximally Flat Low-Pass Filter Prototypes ($\epsilon_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)</caption> <thead> <tr> <th>N</th> <th>ϵ_1</th> <th>ϵ_2</th> <th>ϵ_3</th> <th>ϵ_4</th> <th>ϵ_5</th> <th>ϵ_6</th> <th>ϵ_7</th> <th>ϵ_8</th> <th>ϵ_9</th> <th>ϵ_{10}</th> <th>ϵ_{11}</th> </tr> </thead> <tbody> <tr><td>1</td><td>2.0000</td><td>1.0000</td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td>2</td><td>1.4142</td><td>1.4142</td><td>1.0000</td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td>3</td><td>1.0000</td><td>2.0000</td><td>1.0000</td><td>1.0000</td><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td>4</td><td>0.7654</td><td>1.8478</td><td>1.8478</td><td>0.7654</td><td>1.0000</td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td>5</td><td>0.6180</td><td>1.6180</td><td>2.0000</td><td>1.6180</td><td>0.6180</td><td>1.0000</td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td>6</td><td>0.5176</td><td>1.4142</td><td>1.9318</td><td>1.9318</td><td>1.4142</td><td>0.5176</td><td>1.0000</td><td></td><td></td><td></td><td></td></tr> <tr><td>7</td><td>0.4450</td><td>1.2470</td><td>1.8019</td><td>2.0000</td><td>1.8019</td><td>1.2470</td><td>0.4450</td><td>1.0000</td><td></td><td></td><td></td></tr> <tr><td>8</td><td>0.3902</td><td>1.1111</td><td>1.6629</td><td>1.9615</td><td>1.9615</td><td>1.6629</td><td>1.1111</td><td>0.3902</td><td>1.0000</td><td></td><td></td></tr> <tr><td>9</td><td>0.3473</td><td>1.0000</td><td>1.5321</td><td>1.8794</td><td>2.0000</td><td>1.8794</td><td>1.5321</td><td>1.0000</td><td>0.3473</td><td>1.0000</td><td></td></tr> <tr><td>10</td><td>0.3129</td><td>0.9080</td><td>1.4142</td><td>1.7820</td><td>1.9754</td><td>1.9754</td><td>1.7820</td><td>1.4142</td><td>0.9080</td><td>0.3129</td><td>1.0000</td></tr> </tbody> </table> <p><small>Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, <i>Microwave Filters, Impedance-Matching Networks, and Coupling Structures</i>, Artech House, Dedham, Mass., 1980, with permission.</small></p>	N	ϵ_1	ϵ_2	ϵ_3	ϵ_4	ϵ_5	ϵ_6	ϵ_7	ϵ_8	ϵ_9	ϵ_{10}	ϵ_{11}	1	2.0000	1.0000										2	1.4142	1.4142	1.0000									3	1.0000	2.0000	1.0000	1.0000								4	0.7654	1.8478	1.8478	0.7654	1.0000							5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000						6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000					7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000				8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000			9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000		10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000	8	1	Ap
N	ϵ_1	ϵ_2	ϵ_3	ϵ_4	ϵ_5	ϵ_6	ϵ_7	ϵ_8	ϵ_9	ϵ_{10}	ϵ_{11}																																																																																																																													
1	2.0000	1.0000																																																																																																																																						
2	1.4142	1.4142	1.0000																																																																																																																																					
3	1.0000	2.0000	1.0000	1.0000																																																																																																																																				
4	0.7654	1.8478	1.8478	0.7654	1.0000																																																																																																																																			
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000																																																																																																																																		
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000																																																																																																																																	
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000																																																																																																																																
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000																																																																																																																															
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000																																																																																																																														
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000																																																																																																																													
ii)	Summarize the different types of mixers and compare the properties in terms of VSWR, RF/LO isolation, conversion loss and third order intercept.	8	4	U																																																																																																																																				
iii)	Explain the different types of coupling in details.	8	5	U																																																																																																																																				
Q.4	Solve any two questions out of three.	16																																																																																																																																						
i)	Design an amplifier for maximum gain at 4 GHz using single-stub matching sections. The transistor is a GaAs MESFET with the following scattering parameters ($Z_0 = 50 \Omega$): $[S_{11}] = 0.72 \angle -116^\circ$ $[S_{12}] = 0.03 \angle 57^\circ$ $[S_{21}] = 2.6 \angle 76^\circ$ $[S_{22}] = 0.73 \angle -54^\circ$	8	2	Ap																																																																																																																																				
ii)	For two port oscillator at steady state oscillation condition prove that if $\Gamma_L \Gamma_{in} = 1$ then $\Gamma_T \Gamma_{out} = 1$.	8	3	Ap																																																																																																																																				
iii)	Explain the EMI Diagnostics and Fixes.	8	5	U																																																																																																																																				
