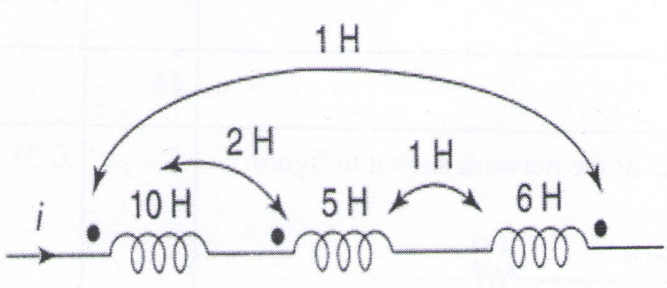
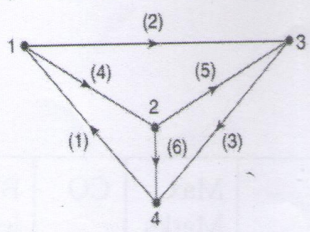
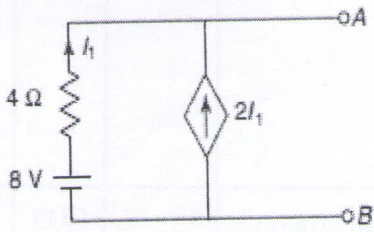
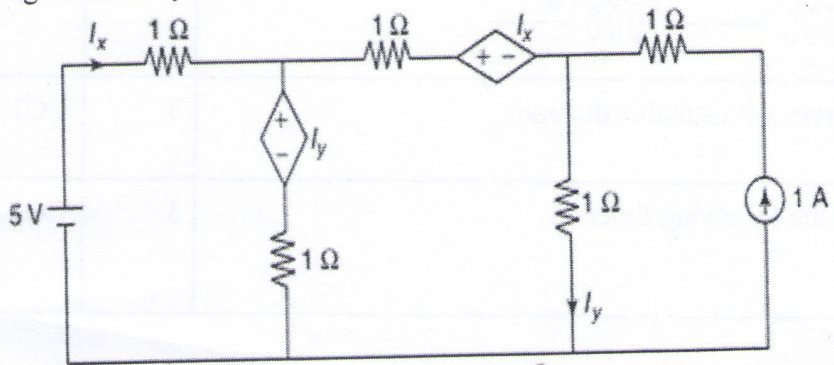


Supplementary Examination August 2023
Program: B.Tech (Electronics and Telecommunication)
Examination: SY Semester: III
Course Code: EXC305 and Course Name: Electrical Network Theory
Duration: 02 Hours **Max. Marks: 45**

Instructions:

- (1) All questions are compulsory.
- (2) Draw neat diagrams wherever applicable.
- (3) Assume suitable data, if necessary.

		Max. Marks	CO	BT level
C1	Solve any 5 questions out of six.	15		
i)	Write equations and condition for symmetry of Z parameters.	3	CO4	R
ii)	The reduced incidence matrix of an oriented graph is given below. Draw the oriented graph. $A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$	3	CO2	Ap
iii)	Test the following polynomials whether Hurwitz or not using Routh array. $P(s) = s^4 + s^3 + 2s^2 + 3s + 2$	3	CO5	Ap
☺	Find the equivalent inductance of the network shown in Figure. 	3	CO1	Ap
v)	State the superposition theorem with suitable diagram.	3	CO1	R
vi)	Obtain the pole zero plot of the following function. $F(s) = \frac{s(s+1)}{(s+2)^2(s+3)}$	3	CO5	Ap

Q.2	Solve any three questions out of four.	15		
i)	<p>The graph of a network is shown in Figure, Write the (a) incidence matrix, (b) tieset matrix, and (c) f-cutset matrix.</p> 	5	CO2	Ap
ii)	<p>Test the following polynomials whether Hurwitz or not is Hurwitz? (Use Routh Array method) $P(s) = S^4 + 7S^3 + 6S^2 + 21S + 8$</p>	5	CO5	Ap
iii)	<p>Find Thevenin's equivalent network across terminals A and B of the following network.</p> 	5	CO1	Ap
iv)	<p>Test the following polynomials whether Hurwitz or not using continued fraction expansion. $P(s) = s^4 + 7s^3 + 6s^2 + 21s + 8$</p>	5	CO5	Ap
Q.3	Solve any three questions out of four.	15		
i)	<p>Find the mesh currents in the three meshes of the network shown in figure using mesh analysis.</p> 	5	CO1	Ap

ii)	Test whether given function is positive real function? $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$	5	CO6	Ap
iii)	In the network shown, the switch is closed at $t=0$. With zero current in the inductor, Find the values of i , di/dt and d^2i/dt^2 at $t=0^+$	5	CO3	Ap
iv)	Find the Z parameters for the network shown.	5	CO4	Ap
