

**University of Mumbai**

**Examination 2020 under cluster 5 (Lead College: APSIT)**

Examinations Commencing from 23<sup>rd</sup> December 2020 to 6<sup>th</sup> January 2021 and from 7<sup>th</sup> January 2021 to 20<sup>th</sup> January 2021

Program: **Electronics and Telecommunication Engineering**



Curriculum Scheme: Rev-2019


Examination: SE Semester III



Course Code: ECC304 and Course Name: Network Theory

Time: 2 Hour

Max. Marks: 80
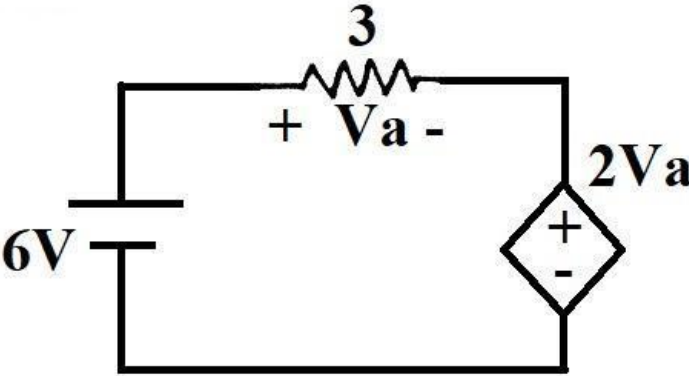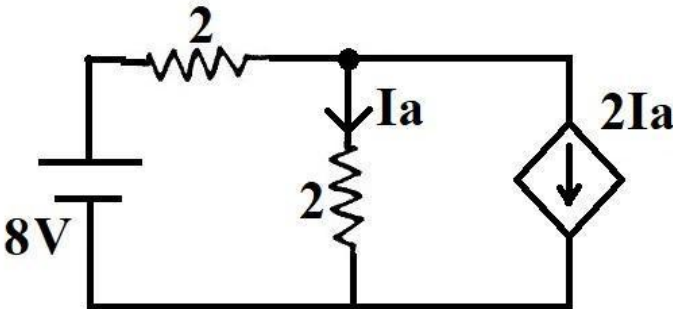
<b>Q1.</b>	<b>Choose the correct option for following questions. All the Questions are compulsory and carry equal marks</b>
1.	Which of the following conditions delivers maximum power to the load? Option A: $R_L > R_{TH}$ Option B: $R_L = R_{TH}$ Option C: $R_L < R_{TH}$ Option D: Depends upon source.
2.	Determine value of $V_a$ shown in the following figure. 
Option A:	1 V
Option B:	2 V
Option C:	3 V
Option D:	4 V
3.	Refer the following figure to find current $I_a$ . 
Option A:	4 A

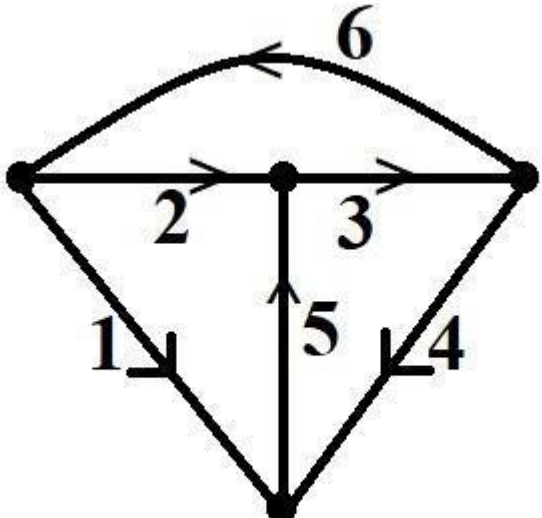Option B:	3 A
Option C:	2 A
Option D:	1 A
4.	Two inductively coupled coils are connected in series with the Aiding method, where $L_1=6\text{mH}$ , $L_2=6\text{mH}$ and $M=1\text{mH}$ . Determine Total inductance of combination.
Option A:	12 mH
Option B:	13 mH
Option C:	14 mH
Option D:	10 mH
5.	Number of fundamental cutsets in following oriented graphs are -----.
	
Option A:	3
Option B:	4
Option C:	5
Option D:	6
6.	Which of the following is the correct generalized KCL equation in graph theory?
Option A:	$B \cdot Z_b \cdot B^T I_l = B \cdot V_s - B \cdot Z_b I_s$
Option B:	$Q Y_b Q^T \cdot V_t = Q I_s - Q Y_b V_s$
Option C:	$Y = Q Y_b Q^T$
Option D:	$Q Y_b Q^T \cdot V_t = Q (1 - Q Y_b V_s)$
7.	Reduced Incidence matrix can be obtained by -----
Option A:	Eliminating a row of complete incidence matrix
Option B:	Multiplying complete incidence matrix with its transpose
Option C:	$ A A^T $
Option D:	Obtaining tree
8.	Laplace transform of $\int_0^t f(t) \cdot dt$ is equal to -----.
Option A:	$d F(S) / dS$

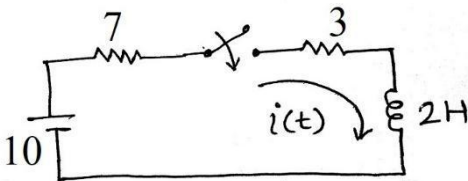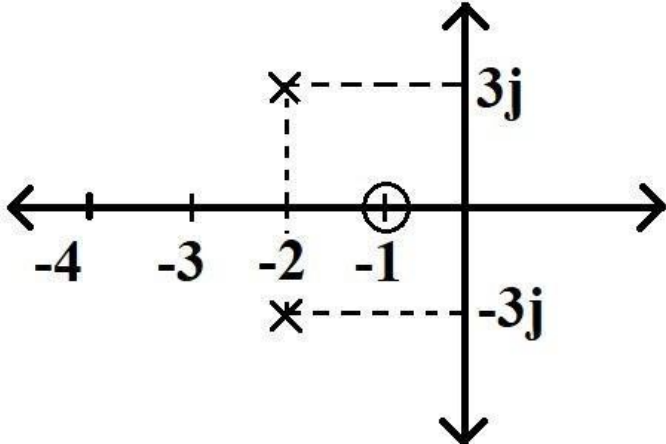Option B:	$S F(S) - f(0)$
Option C:	$F(S) / S$
Option D:	$F(S+a)$
9.	Voltage source $V$ is applied to series connected $R$ and $L$ networks. Equation of the current in the inductor is -----.
Option A:	$i(t) = V(1 - e^{-t/R}) / R$
Option B:	0
Option C:	$i(t) = V(1 - e^{-t/L}) / R$
Option D:	$i(t) = (e^{-t/L})$
10.	In the following figure, a switch was opened for a long time and then closed at $t = 0$ . Determine $i(t)$ at $t = 0^+$ . 
Option A:	1 A
Option B:	0.3 A
Option C:	0.7 A
Option D:	0 A
11.	For a series connected $R$ - $C$ network where $R = 100$ ohm and $C = 0.1$ uF connected in series. Time constant ( $\tau$ ) of a given circuit is -----.
Option A:	10 uSec
Option B:	1 / 100 Sec
Option C:	100 uSec
Option D:	1 uSec
12.	The driving point impedance function $Z(S)$ of a network has pole-zero location shown in figure, then $Z(S)$ is given by -----. 
Option A:	$\frac{H (S+2-3j)(S+2+3j)}{(S+1)}$
Option B:	$\frac{H (S-1)}{(S-2-3j)(S-2+3j)}$

Option C:	$\frac{H(S+1)}{(S+2-3j)(S+2+3j)}$
Option D:	$\frac{H(S+1)}{(S-2-3j)(S-2+3j)}$
13.	Polynomial $P(S) = 3S^3 + 4S^2 + 2S + 1$ is to be tested for Hurwitz. Elements in the first column of Routh's array are -----.
Option A:	3, 4, 2, 1
Option B:	3, 4, -1.25, 1
Option C:	3, 4, -2, 1
Option D:	3, 4, 1.25, 1
14.	If inductor and capacitor are connected in series then equivalent impedance is ---
Option A:	$L + C$
Option B:	$LS + 1 / CS$
Option C:	$\frac{LC+1}{CS}$
Option D:	$(S + L) C$
15.	Two two port networks are connected in parallel. The combination is to be represented as a single two-port network. The parameters obtained by adding individuals are ----.
Option A:	Z-parameter matrix
Option B:	h-parameter matrix
Option C:	ABCD-parameter matrix
Option D:	Y-parameter matrix
16.	A Two port network has the following equations. $I_2 = 10 I_1 + 2 V_2$ and $V_1 = 5 I_1 + 6 V_2$ and Hybrid parameters are $h_{11} = \text{-----}$ and $h_{12} = \text{-----}$ respectively.
Option A:	6 and 5
Option B:	10 and 2
Option C:	5 and 6
Option D:	2 and 10
17.	A two port network is said to be symmetrical if ----
Option A:	Voltage to current ratio at one port is the same as the voltage to current ratio at another port with one port open circuited.
Option B:	Voltage gain and current gain are the same.
Option C:	Ratio of excitation at one port to response at another port is the same if excitation and response is interchanged.
Option D:	Current gain is same if ports are interchanged
18.	Driving point impedance function $Z(S) = \frac{3}{S+4}$ is -----
Option A:	Series combination of two inductors
Option B:	Parallel combination of Inductor and Resistor
Option C:	Parallel combination of resistor and capacitor
Option D:	Series combination of two capacitors

19.	Realization of function using Cauer-II can be obtained by -----.
Option A:	Partial fraction expansion on Y(S)
Option B:	Partial fraction expansion on Z(S)
Option C:	Division operation on Z(S)
Option D:	Continued fraction expansion
20.	Function $F(S) = \frac{(S-3)}{S^2+9S+20}$ is not positive real function because ---
Option A:	A zero is right half of S-Plane
Option B:	Poles are lies on left side of S plane
Option C:	A zero is at left half of S plane
Option D:	All poles lie on left half of S-Plane

Q2	Solve any Two Questions out of Three	10 marks each
A	Find Thevenin's equivalent across X and Y terminals for a given network.	
B	Realize the following function using Cauer-I and Cauer-II form $Z(S) = \frac{S^2+4S+3}{S^2+2S}$	
C	The switch is changed from position-1 to position-2 at $t=0$ . Steady state condition was reached before switching. Determine $i(t)$ , $\frac{di(t)}{dt}$ and $\frac{d^2i(t)}{dt^2}$ at $t=0+$ .	

Q3	Solve any Two Questions out of Three	10 marks each
----	--------------------------------------	---------------

A

Find ABCD parameters of a given network.

B

Find network function  $\frac{V_1}{I_1}$ ,  $\frac{V_2}{I_1}$ ,  $\frac{V_2}{V_1}$

C

The graph of the network shown in below. Obtain f-tieset, f-cutset and Incidence matrix.

**University of Mumbai**

**Examination 2020 under cluster 5 (Lead College: APSIT)**

**Examinations Commencing from 23<sup>rd</sup> December 2020 to 6<sup>th</sup> January 2021 and from 7<sup>th</sup> January 2021 to 20<sup>th</sup> January 2021**

**Program: Electronics and Telecommunication Engineering**

Curriculum Scheme: Rev-2019

Examination: SE Semester III

Course Code: ECC304 and Course Name: Network Theory

Time: 2 hour

Max. Marks: 80

---

---

<b>Question Number</b>	<b>Correct Option (Enter either 'A' or 'B' or 'C' or 'D')</b>
Q1.	B
Q2.	B
Q3.	D
Q4.	C
Q5.	A
Q6.	B
Q7.	A
Q8.	C
Q9.	C
Q10.	D
Q11.	A
Q12.	C
Q13.	D
Q14.	B
Q15.	D
Q16.	C
Q17.	A
Q18.	C
Q19.	D
Q20.	A