

University of Mumbai
Examination 2020 under Cluster 06
(Lead College :- Vidyavardhini's College of Engineering & Technology)

Examinations Commencing from 7th January 2021 to 20th January 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev. 2019

Examination: S.E. Semester III

Course Code: ELC302 and Course Name: Electronic Devices & Circuits – I

Time: 2 hour

Max. Marks: 80

Q.1	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks.
1.	The capacitance in a reverse biased PN junction is called as :-
Option A:	Terminal capacitance
Option B:	Junction capacitance
Option C:	Diffusion capacitance
Option D:	Transition capacitance
2.	In any semiconductor material, the diffusion current is proportional to :-
Option A:	Applied electric field
Option B:	Concentration gradient of charge carriers
Option C:	Square of applied electric field
Option D:	Cube of applied electric field
3.	The phenomenon of Zener breakdown occurs in :-
Option A:	Heavily doped PN junction
Option B:	Lightly doped PN junction
Option C:	Moderately doped PN junction
Option D:	Forward biased PN junction
4.	Forward break-over voltage (V_{FBO}) of a typical silicon diode is approximately :-
Option A:	0.6 V – 0.7 V
Option B:	0.2 V – 0.3 V
Option C:	1.1 V – 1.2 V
Option D:	0.1 V – 0.2 V
5.	When a reverse current in Zener diode increases from 20 mA to 30 mA, Zener voltage changes from 5.6 V to 5.65 V. The Zener resistance (r_z) is given by :-
Option A:	2 Ω
Option B:	3 Ω
Option C:	4 Ω
Option D:	5 Ω
6.	In bipolar junction transistor (BJT) which mode of operation is not commonly used in real life applications ?
Option A:	The inverse / reverse mode of operation
Option B:	The cut-off mode of operation
Option C:	The saturation mode of operation
Option D:	The forward active / linear mode of operation

7.	In bipolar junction transistor (BJT) the Early effect is due to :-
Option A:	Decrease in width of the emitter due to reverse bias of collector-to-base junction
Option B:	Decrease in width of the base due to reverse bias of collector-to-base junction
Option C:	Decrease in width of collector due to reverse bias of collector-to-base junction
Option D:	Temperature variations resulting in thermally generated minority carriers
8.	In PNP bipolar junction transistor (BJT), stream of current in active region is due to :-
Option A:	Drift of holes
Option B:	Drift of electrons
Option C:	Diffusion of holes
Option D:	Diffusion of electrons
9.	In a bipolar junction transistor (BJT) if $\beta = 100$ & collector current (I_C) is 30 mA then what is the value of base current (I_B) ?
Option A:	0.03 mA
Option B:	0.3 mA
Option C:	3 mA
Option D:	300 mA
10.	The field effect transistor (FET) is :-
Option A:	Power controlled device
Option B:	Energy controlled device
Option C:	Current controlled device
Option D:	Voltage controlled device
11.	Pinch-off voltage in field effect transistor (FET) is :-
Option A:	Drain-to-source voltage giving zero (no) drain-to-source current
Option B:	Drain-to-source voltage giving maximum drain-to-source current
Option C:	Gate-to-source voltage giving zero (no) drain-to-source current
Option D:	Gate-to-source voltage giving maximum drain-to-source current
12.	Which of the following statement is not true for any field effect transistor (FET) ?
Option A:	FET has very high input resistance / impedance as compared to BJT
Option B:	FET is a majority carrier operated (unipolar) device
Option C:	FET has excellent operating stability against temperature variations compared to BJT
Option D:	FET has higher transconductance compared to BJT
13.	In junction field effect transistor (JFET), the amplification factor (μ) is expressed by which of the following mathematical expressions ?
Option A:	$\mu = g_m \times r_d$
Option B:	$\mu = g_m + r_d$
Option C:	$\mu = g_m - r_d$
Option D:	$\mu = g_m / r_d$
14.	For metal oxide semiconductor field effect transistor (MOSFET), the input impedance or the input resistance (R_i or Z_i) is :-
Option A:	Less than JFET but more than BJT
Option B:	More than both, JFET & BJT
Option C:	More than JFET but less than BJT
Option D:	Less than both, JFET & BJT

15.	In MOSFET, which terminal is electrically isolated from the entire device structure ?
Option A:	Source (S)
Option B:	Drain (D)
Option C:	Gate (G)
Option D:	Bulk or Body or Substrate (SS)
16.	In design of filters, which of these has the lowest value of ripple factor (γ) ?
Option A:	Capacitor (C) Filter
Option B:	Inductor (L) Filter
Option C:	Inductor & Capacitor (L-C) Filter
Option D:	C-L-C or ' π ' Filter
17.	Maximum operating efficiency of a full wave bridge type rectifier to be considered during the design process is :-
Option A:	25 %
Option B:	40.6 %
Option C:	81.2 %
Option D:	50 %
18.	Which of these statements is not true for any type of BJT common base (CB) configuration amplifier ?
Option A:	It has a low input impedance / resistance
Option B:	It has a high output impedance / resistance
Option C:	It has moderate to high voltage gain
Option D:	It produces a phase shift in amplified output signal with respect to input signal applied
19.	Which process of electron-hole pair (EHP) is responsible for emitting of light ?
Option A:	Recombination
Option B:	Diffusion
Option C:	Breakdown
Option D:	Ionization
20.	Which of these diodes does not work in the reverse bias mode of operation ?
Option A:	Light emitting diode (LED)
Option B:	Zener diode
Option C:	Varactor diode
Option D:	Photo diode

Q.2 (20 Marks)	Solve any Four out of Six	05 Marks Each
A	Explain the effects of temperature on the V – I characteristics of PN junction diode with a neat sketch / diagram & appropriate mathematical expressions.	
B	Describe forward bias V – I characteristics of PN junction diode with neat labeled diagram & appropriate sketch.	
C	Explain working of Center Tap type full wave rectifier with help of circuit diagram.	
D	Discuss the working / operation of dual end clipper circuit with a neat labeled diagram showing appropriate waveforms of the resulting clipped output voltage.	
E	Explain the operation of Zener diode as a voltage regulator with a neat sketch for condition where supply / source voltage remains constant but load resistor varies.	

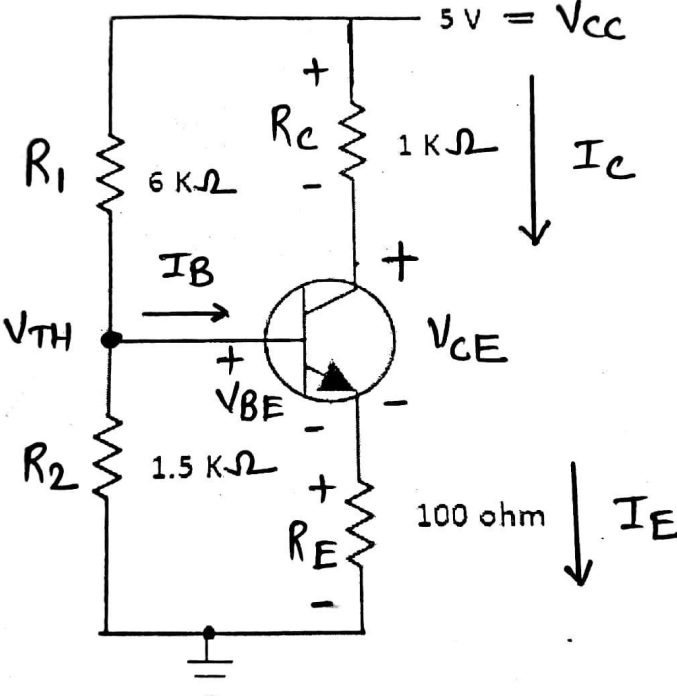
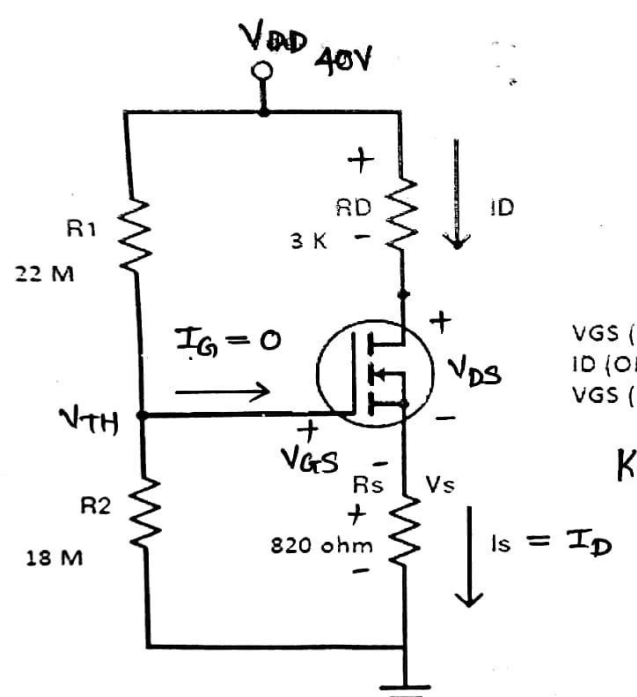
F	With a neat sketch, describe the operating principle & the construction of the light emitting diode (LED).	
Q.3 (20 Marks)	Solve any Two out of Three	10 Marks Each
A	<p>For a voltage divider bias circuit shown in Fig. 1 using Silicon (Si) BJT with $\beta = 100$ calculate the Q – point where $Q = [V_{CE}, I_C]$.</p>  <p style="text-align: center;">Fig. 1 for Q.3 (A)</p>	
B	<p>For the voltage divider bias circuit shown in Fig. 2 using N-channel E-MOSFET calculate Q – point where $Q = [V_{DS}, I_D]$.</p>  <p style="text-align: right;"> $V_{GS} (Th) = 5 V$ $I_D (ON) = 3 mA$ $V_{GS} (ON) = 10 V$ $K_n = 0.12 mA/V^2$ </p>	

Fig. 2 for Q.3 (B)

Fig. 3 shows a single stage CE – BJT amplifier using BC 547 where $\beta = 300$ & $V_{BE} = 0.7$ V. Calculate the input resistance (R_i), output resistance (R_o) & small signal voltage gain (A_v).

C

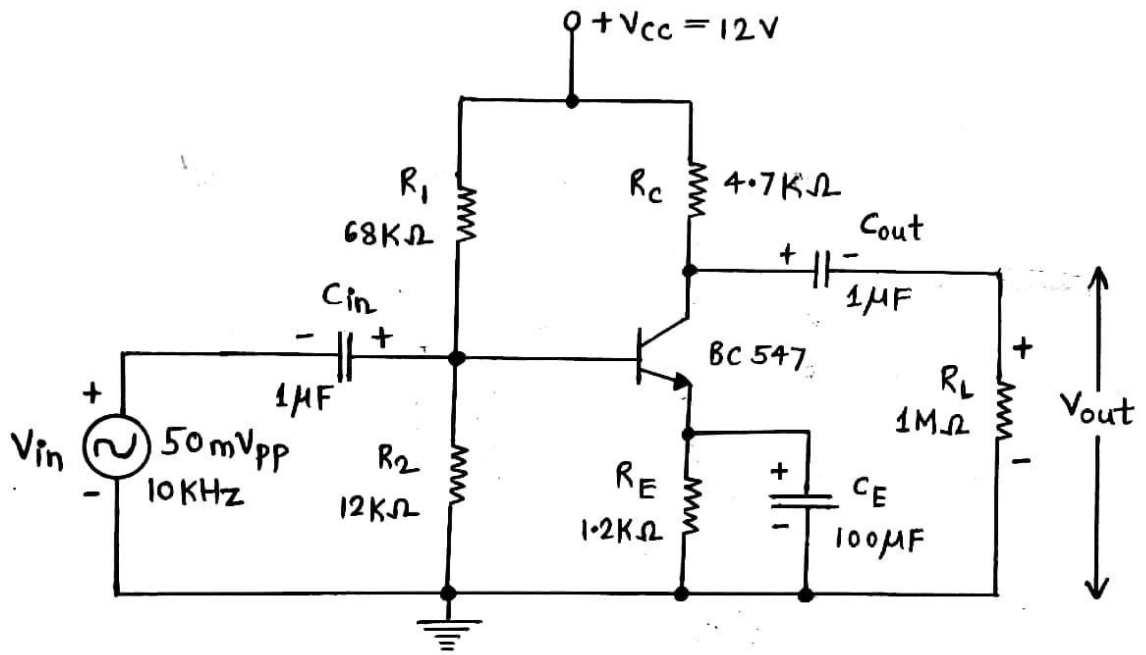


Fig. 3 for Q.3 (C)

University of Mumbai
Examination 2020 under Cluster 06
(Lead College :- Vidyavardhini's College of Engineering & Technology)
Examinations Commencing from 7th January 2021 to 20th January 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev. 2019

Examination: S.E. Semester III

Course Code: ELC302 and Course Name: Electronic Devices & Circuits – I

Time: 2 hour

Max. Marks: 80

Q.1

Question No.	Correct Option (Enter either 'A' or 'B' or 'C' or 'D')
Q.1	D
Q.2	B
Q.3	A
Q.4	A
Q.5	D
Q.6	A
Q.7	B
Q.8	C
Q.9	B
Q.10	D
Q.11	C
Q.12	D
Q.13	A
Q.14	B
Q.15	C
Q.16	D
Q.17	C

Q.18	D
Q.19	A
Q.20	A

Q.2 (A) - Explain the effects of temperature on the V - I characteristics of PN junction diode with a neat sketch / diagram & appropriate mathematical expressions.

* EFFECT OF TEMP. ON DIODE CHARACTERISTICS :-

As we know that the forward current through diode is given by eqn:

$$I_f = I_s (e^{V_D/nVT} - 1)$$

For the values of V_D $e^{V_D/nVT} \gg 1$.

$$\therefore I_f = I_s e^{V_D/nVT}$$

$$\therefore \frac{I_f}{I_s} = e^{V_D/nVT}$$

\therefore Taking \log_e on both sides, we get

$$\log_e e^{V_D/nVT} = \log_e \left(\frac{I_f}{I_s} \right)$$


$$\therefore \frac{V_D}{n \cdot VT} \log_e e = \log_e \left(\frac{I_f}{I_s} \right)$$

$$\therefore \frac{V_D}{\eta V_T} = \log_e \left(\frac{I_f}{I_s} \right)$$

$$\therefore V_D = \eta V_T \log_e \left(\frac{I_f}{I_s} \right) \quad \longrightarrow \textcircled{A}$$

The above Equation indicates that forward voltage drop across diode depends upon the Reverse saturation current I_s . The reverse saturation current I_s of diode doubles in magnitude for every 10°C increase in temp., it means that increase in temp. increases I_s , and hence forward voltage drop V_D across diode decreases. From the equation \textcircled{A} , V_D also depends upon the V_T , but change in V_T due to temp. is comparatively less as change in I_s . Thus increase in level of I_s , will overpower the smaller percentage change in V_T .

 Thus as the temp. of the diode increases then the forward voltage drop i.e. V_D decreases, hence, diode conducts earlier, due to which the forward characteristics of the diode moves to the left with increase in temperature.



Q.3 (A) – For the voltage divider bias circuit shown in Fig. 1 using silicon (Si) BJT with $\beta = 100$ calculate the Q – point where $Q = [V_{CE}, I_C]$.

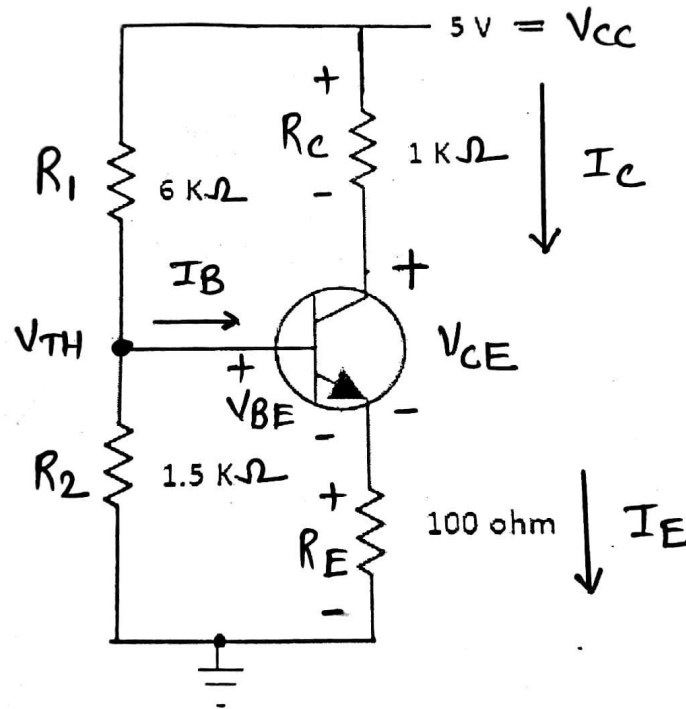


Fig. 1 for Q.3 (A)

② BJT voltage Divider Biasing

Data Given :-

$$R_1 = 6K\Omega \text{ \& } R_2 = 1.5K\Omega$$

$$R_C = 1K\Omega \text{ \& } R_E = 100\Omega$$

$$\beta = 100 \text{ \& } V_{BE} = 0.7V$$

$$R_{TH} = R_1 // R_2 = 6K // 1.5K = 1.2K\Omega \longrightarrow \textcircled{1}$$

$$V_{TH} = \frac{V_{CC} \cdot R_2}{R_1 + R_2} = \frac{5 \times 1.5K}{6K + 1.5K} = 1V \longrightarrow \textcircled{2}$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E} = \frac{1 - 0.7}{1.2K + (101) \times 100} = 26.55 \mu A \longrightarrow \textcircled{3}$$

$$I_C = \beta \cdot I_B = 100 \times 26.55 \times 10^{-6} = 2.65mA \longrightarrow \textcircled{4}$$

$$V_{CE} = V_{CC} - I_C [R_C + R_E] = 5 - 2.65 [1 + 0.1] = 2.09V$$

Hence $Q = [V_{CE}, I_C] = [2.09V, 2.65mA]$

Q.3 (B) – For the voltage divider bias circuit as shown in Fig. 2 using N-channel E-MOSFET calculate the Q – point where $Q = [V_{DS}, I_D]$.

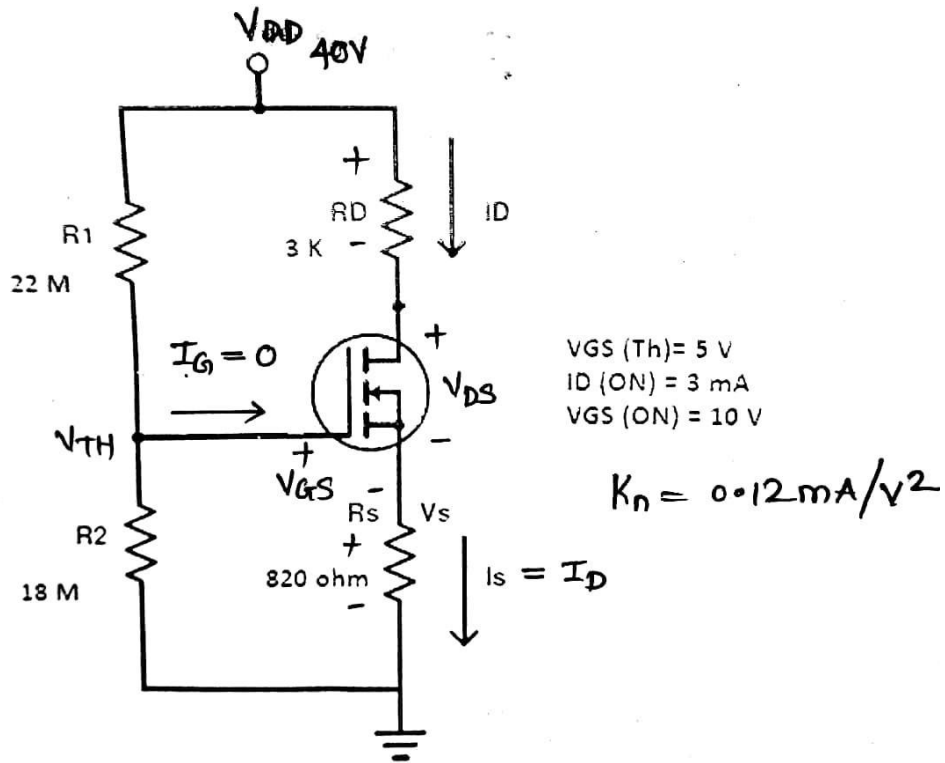


Fig. 2 for Q.3 (B)

E-MOSFET voltage Divider Biasing

$$K_n = \frac{I_{D(QN)}}{[V_{GS(QN)} - V_{GS(TH)}]^2} = \frac{3 \text{ mA}}{[10 - 5]^2} = 0.12 \text{ mA/V}^2 \longrightarrow \textcircled{1}$$

$$V_{GS} = V_{TH} - I_D R_S = 18 - 0.82 I_D \longrightarrow \textcircled{2}$$

$$I_D = K_n [V_{GS} - V_{GS(TH)}]^2 \longrightarrow \textcircled{3}$$

$$I_D = 0.12 [18 - 0.82 I_D - 5]^2 \longrightarrow \textcircled{4}$$

$$\boxed{\text{Hence } I_D = 6.725 \text{ mA}} \longrightarrow \textcircled{5}$$

$$V_{DS} = V_{DD} - I_D [R_D + R_S] = 40 - 6.725 [3 + 0.82] \longrightarrow \textcircled{6}$$

$$\boxed{\text{Hence } V_{DS} = 14.31 \text{ V}}$$

Hence the Q-point is located at $Q = [V_{DS}, I_D]$

$$\underline{\underline{Q = [14.31 \text{ V}, 6.725 \text{ mA}]}}$$

Q.3 (C) - Fig. 3 shows a single stage CE - BJT amplifier using BC 547 where $\beta = 300$ & $V_{BE} = 0.7 \text{ V}$. Calculate the input resistance (R_i), output resistance (R_o) & small signal voltage gain (A_v).

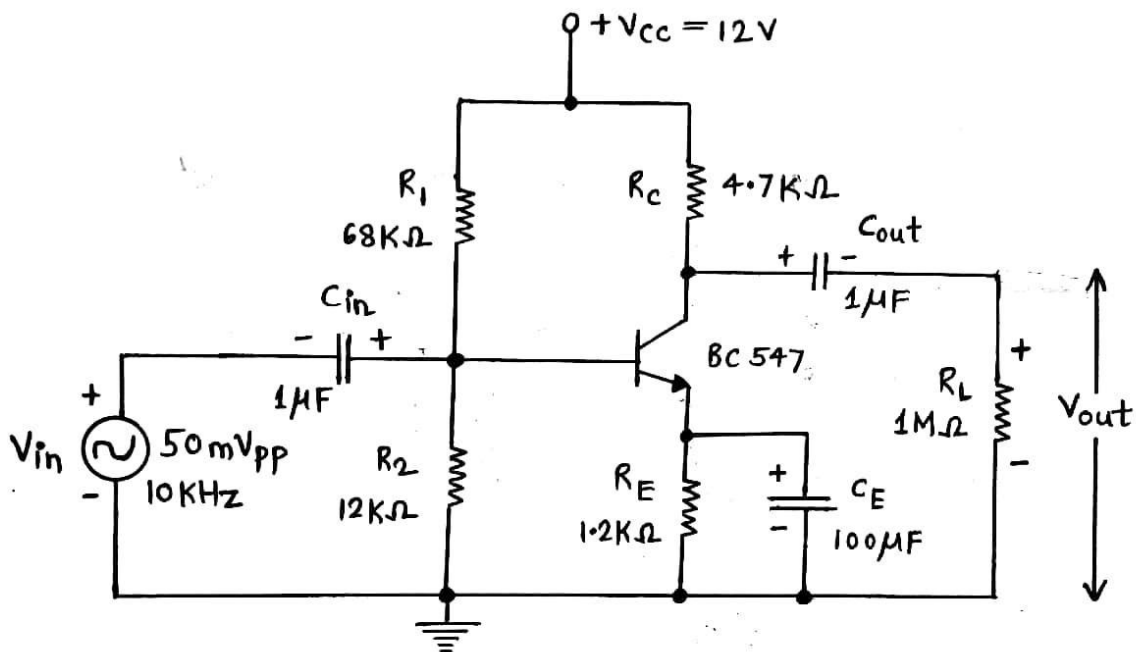


Fig. 3 for Q.3 (C)

Q.2(a) DC operating conditions :-

$$V_{TH} = \frac{V_{CC} \cdot R_2}{R_1 + R_2} = \frac{12 \times 12K}{12K + 68K} = 1.8V \longrightarrow \textcircled{1}$$

$$R_{TH} = R_1 // R_2 = 68K // 12K = 10.2K\Omega \longrightarrow \textcircled{2}$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)R_E} = \frac{1.8 - 0.7}{10.2K + (1 + 300) \times 1.2K} = 2.96 \mu A \longrightarrow \textcircled{3}$$

$$r_{\pi} = \frac{26mV}{I_B} = \frac{26 \times 10^{-3}}{2.96 \times 10^{-6}} = 8.783K\Omega \longrightarrow \textcircled{4}$$

AC operating conditions :-

$$R_i = R_1 // R_2 // r_{\pi} = 68K // 12K // 8.78K = 4.72K\Omega \longrightarrow \textcircled{5}$$

$$R_o = R_c = 4.7K\Omega \longrightarrow \textcircled{6}$$

$$R_{eq} = R_E // \left[\frac{r_{\pi}}{1 + \beta} \right] = 1.2K // 29.28 = 28.58\Omega \longrightarrow \textcircled{7}$$

$$|A_v| = \left[R_c // R_L \right] \left[\frac{1 + \beta}{r_{\pi}} \right] = 160.32 \longrightarrow \textcircled{8}$$