

University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)

Examination Commencing from 15th June 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2019

Examination: SE Semester III

Course Code: ELC304 and Course Name: Electrical Network Analysis and Synthesis




Time: 2 hour

Max. Marks: 80

Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	According to Kirchhoff's voltage law, the algebraic sum of all IR drops and e.m.fs. in any closed loop of a network is always
Option A:	Negative
Option B:	Positive
Option C:	Determined by battery e.m.fs.
Option D:	Zero
2.	A dependent source
Option A:	May be a current source or a voltage source
Option B:	Is always a voltage source
Option C:	Is always a current source
Option D:	Neither a current source nor a voltage source
3.	For determining the polarity of a voltage drop across a resistor, it is necessary to know the
Option A:	Value of resistor
Option B:	Value of current
Option C:	Direction of current flowing through the resistor
Option D:	Value of e.m.f. in the circuit
4.	In superposition theorem, when we consider the effect of one voltage source, all the other voltage sources are
Option A:	Shorted
Option B:	Opened
Option C:	Removed
Option D:	Undisturbed
5.	Thevenin resistance is found by
Option A:	Shorting all voltage sources
Option B:	Opening all current sources
Option C:	Shorting all voltage sources and opening all current sources
Option D:	Opening all voltage sources and shorting all current sources
6.	For magnetically coupled circuits, $M = K\sqrt{L_1L_2}$, where K represents

Option A:	Inductance
Option B:	Coefficient of coupling
Option C:	Reluctance
Option D:	Constant
7.	A capacitor with initial voltage zero, what will be equivalent circuit at $t=0^+$
Option A:	Open circuit
Option B:	Short Circuit
Option C:	Voltage source
Option D:	Current source
8.	A inductor with initial current I_0 , what will be equivalent circuit at $t=\infty$
Option A:	Short circuit
Option B:	Open circuit
Option C:	Short circuit across current source
Option D:	open circuit in series with voltage source
9.	A step function voltage is applied to an RLC series circuit having $R=2\Omega$, $L=1H$ and $C=1 F$. The Transient response would be
Option A:	over damped
Option B:	under damped
Option C:	Undamped
Option D:	critically damped
10.	The transient currents are due to
Option A:	resistance of the circuit
Option B:	impedance of the circuit
Option C:	voltage applied to the circuit
Option D:	charges stored in inductors and capacitor
11.	The necessary and sufficient condition for a rational function $F(s)$ to be the driving-point impedance of an RC network is that all poles and zeros should be
Option A:	complex and lie in the left half of s-plane
Option B:	simple and lie on the negative real axis in the s-plane
Option C:	complex and lie in the right half of s-plane
Option D:	simple and lie on the positive real axis of the s-plane
12.	As the poles of a network shift away from the x-axis, the response
Option A:	Remains constant
Option B:	becomes less oscillating
Option C:	become more oscillating
Option D:	No oscillation
13.	A Two-port resistive network satisfy the condition $A = D = (3/2)B = (4/3)C$. Find the value of Z_{11} for the network
Option A:	$4/3$
Option B:	$3/4$
Option C:	$2/3$
Option D:	$3/2$

14.	Which of the following ABCD parameters is unit less?
Option A:	A and D
Option B:	A and B
Option C:	B and C
Option D:	A and C
15.	An RC driving -point impedance function has zeros at $S=-2$ and $S=-5$. The admissible poles for the function would be
Option A:	$S=0, S=-6$
Option B:	$S=0, S=-1$
Option C:	$S=-3, S=-4$
Option D:	$S=-1, S=-3$
16.	Determine the range of 'k' so that $P(s)=s^3 + 3s^2 + 2s+k$ is Hurwitz
Option A:	$0 < k < 6$
Option B:	$0 < k < 5$
Option C:	$1 < k < 0$
Option D:	$k > 0$
17.	The passband of typical filter network with Z_1 and Z_2 as the series and shunt-arm impedance is characterized by
Option A:	$-1 < z_1/4z_2 < 0$
Option B:	$-1 < z_1/4z_2 < 1$
Option C:	$0 < z_1/4z_2 < 1$
Option D:	$z_1/4z_2 > 0$
18.	Find the value of Inductor for Constant K Low Pass "T" Section, if cutoff frequency is 4KHz and nominal characteristic impedance is 500ohm
Option A:	39.79mH
Option B:	29.79mH
Option C:	19.9mH
Option D:	29.9mH
19.	The Cauer - II form is obtained by
Option A:	Continued Fraction Expansion about the pole at infinity
Option B:	Partial Fraction Expansion of the admittance function $Y(S)$
Option C:	Continued Fraction Expansion about the pole at origin
Option D:	Partial Fraction Expansion of the impedance function $Z(S)$
20.	If $Z_{11} = 10\Omega$, $Z_{12}=Z_{21}=5\Omega$, $Z_{22}=20\Omega$. Find the value of Z_1 , Z_2 and Z_3 for the equivalent T-network
Option A:	$Z_1=5, Z_2=5, Z_3=15$
Option B:	$Z_1=10, Z_2=10, Z_3=15$
Option C:	$Z_1=5, Z_2=10, Z_3=15$
Option D:	$Z_1=10, Z_2=10, Z_3=10$

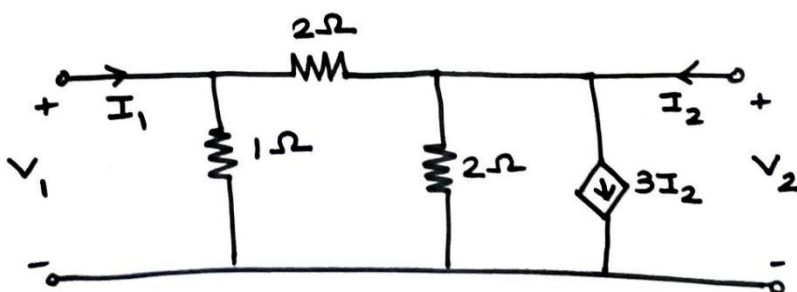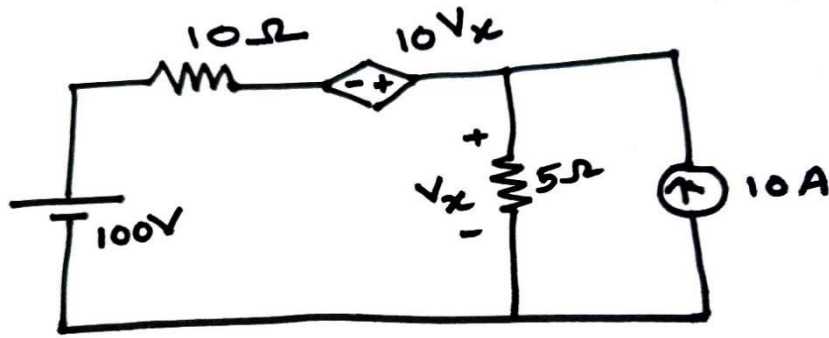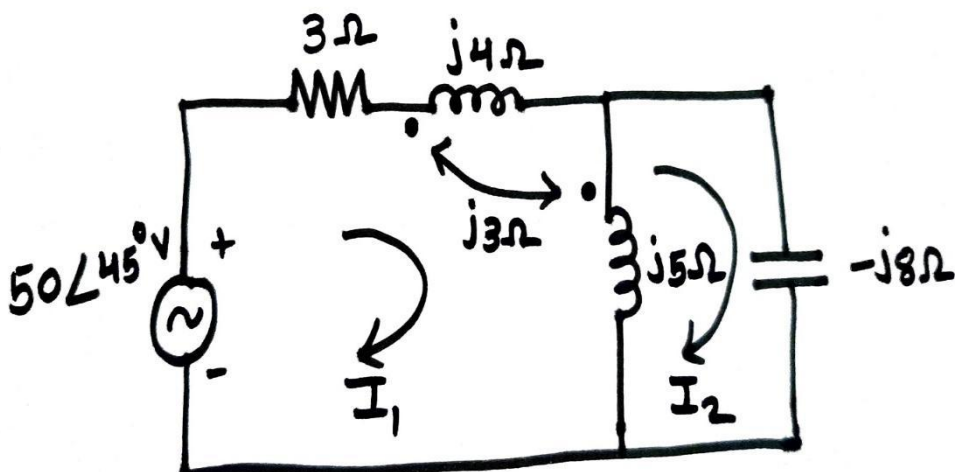Q2 (20 Marks)		
A	Solve any Two	5 marks each
i.	<p>For the Network shown in figure, find Z parameters.</p> 	
ii.	<p>Find the current in the 10 Ω resistor using Thevenin's theorem.</p> 	
iii.	<p>Find the current through the capacitor using mesh analysis.</p> 	
B	Solve any One	10 marks each

i. The switch in the network shown in figure is closed at $t=0$. Find $V_2(t)$ for all $t>0$. Assume zero initial current in the inductor.

ii. The network shown in figure has the driving-point admittance $Y(s)$ of the form


$$Y(s) = H \frac{(s-s_1)(s-s_2)}{(s-s_3)}$$

(a) Express s_1, s_2, s_3 in terms of R, L and C .

(b) When $s_1 = -10 + j10^4, s_2 = -10 - j10^4$ and $Y(j0) = 10^{-1}$ mho, Find the values of R, L and C and determine the value of s_3 .

Q3 (20 Marks)	
A	Solve any Two 5 marks each
i.	Test whether the polynomial $P(s)$ is Hurwitz. $P(s) = S^5 + S^3 + S$

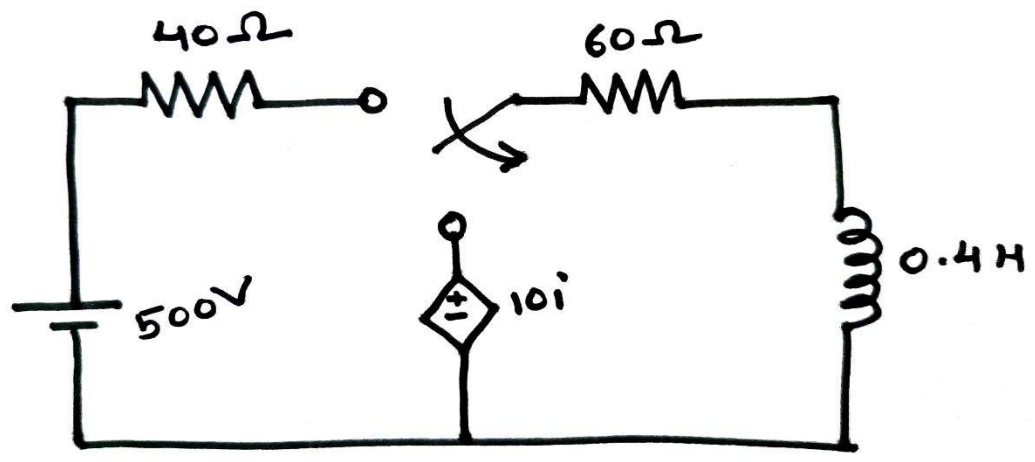ii. For the network shown in figure. Find the current $i(t)$ when the switch is changed from the position 1 to 2 at $t=0$.



iii. Convert Y-parameter in terms of Hybrid parameter. 10 marks each


B Solve any One

i. Obtain the Cauer -I and Cauer -II forms of the RC impedance function.

$$Z(s) = (S+2)(S+6)$$

$$2(S+1)(S+3)$$

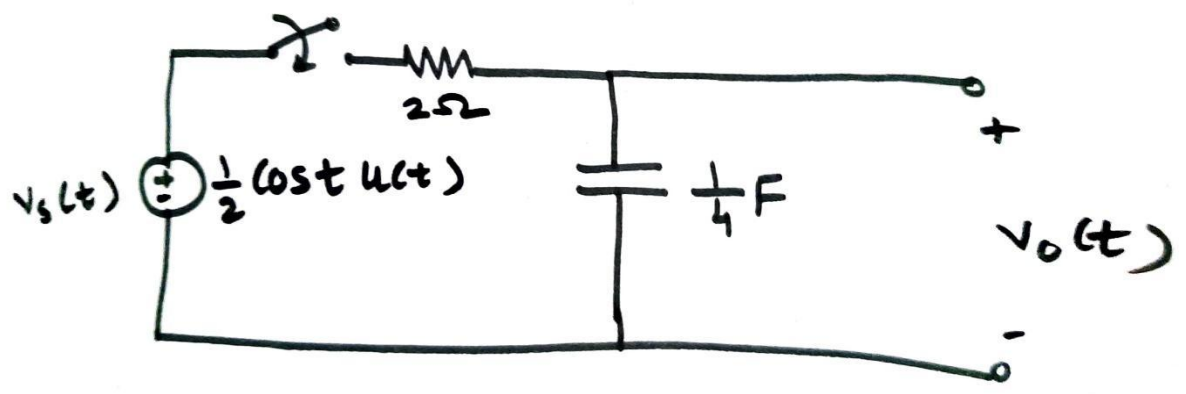ii. Find the network shown in Figure, Find the response $v_o(t)$.



University of Mumbai
Examination 2021 under Cluster 06
(Lead College: Vidyavardhini's College of Engg Tech)

Examination Commencing from 15th June 2021

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2019

Examination: SE Semester III

Course Code: ELC304 and Course Name: Electrical Network Analysis and Synthesis

Time: 2 hour

Max. Marks: 80

Q1:

Question Number	Correct Option (Enter either 'A' or 'B' or 'C' or 'D')
Q1.	D
Q2.	A
Q3.	C
Q4.	A
Q5.	C
Q6.	B
Q7.	B
Q8.	C
Q9.	D
Q10.	D
Q11.	B
Q12.	C
Q13.	A
Q14.	A
Q15.	D
Q16.	A
Q17.	A
Q18.	C
Q19.	C
Q20.	A

2(A):

Q: 2
A)

i) The network is redrawn by source transformation.

KVL to mesh 1,
 $V_1 = I_1 - I_3$ — (i)

KVL to mesh 2,
 $V_2 = 2(I_2 + I_3) - 6I_2$
 $= -4I_2 + 2I_3$ — (ii)

KVL to mesh 3,
 $-(I_3 - I_1) - 2I_3 - 2(I_2 + I_3) + 6I_2 = 0$
 $5I_3 = I_1 + 4I_2$
 $I_3 = \frac{1}{5}I_1 + \frac{4}{5}I_2$ — (iii)

Substituting Eq. (iii) in Eq. (i)
 $V_1 = I_1 - \frac{1}{5}I_1 - \frac{4}{5}I_2 = \frac{4}{5}I_1 - \frac{4}{5}I_2$


Substituting Eq. (iii) in eq. (ii)

$$V_2 = -4I_2 + 2\left(\frac{1}{5}I_1 + \frac{4}{5}I_2\right)$$

$$-\frac{2}{5}I_1 = \frac{12}{5}I_2$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 4/5 & -4/5 \\ 2/5 & -12/5 \end{bmatrix}$$

ii) Step I
Calculation of V_{Th}

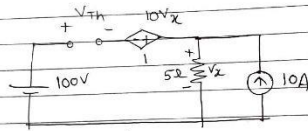

$$V_x = 50V$$

$$100 - V_{Th} + 10V_x - V_x = 0$$

$$100 - V_{Th} + 9V_x = 0$$

$$100 - V_{Th} + 9(50) = 0$$

$$V_{Th} = 550V$$

Step II
Calculation of I_N

$$V_x = 5(I_N + 10)$$

KVL to mesh 1,

$$100 + 10V_x - V_x = 0$$

$$V_x = -\frac{100}{9}$$

$$\therefore I_N = -\frac{550}{45} A$$


Step III Calculation of R_{Th}

$$R_{Th} = -45 \Omega$$

Step IV Calculation of I_L

$$I_L = \frac{550}{-45 + 10} = -\frac{110}{7} A$$

iii)

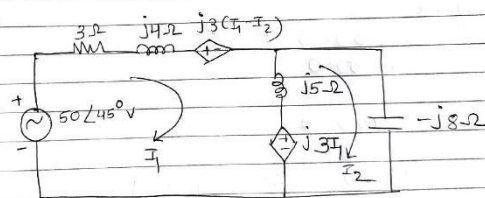

KVL to mesh 1,

$$(3 + j15)I_1 - j8I_2 = 50\angle 45^\circ \quad \text{--- (i)}$$

KVL to mesh 2,

$$-j8I_1 - j3I_2 = 0 \quad \text{--- (ii)}$$

$$\begin{bmatrix} 3 + j15 & -j8 \\ -j8 & -j3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50\angle 45^\circ \\ 0 \end{bmatrix}$$

$$I_2 = \begin{bmatrix} 3 + j15 & 50\angle 45^\circ \\ -j8 & 0 \end{bmatrix}$$

$$\begin{bmatrix} 3 + j15 & -j8 \\ -j8 & -j3 \end{bmatrix}$$

$$I_2 = 3.66 / -310.33^\circ A$$

B)


i) At $t = 0^-$

$$i_1(0^-) = 0$$

$$i_2(0^-) = 0$$

$$i_2(0^+) = 0$$
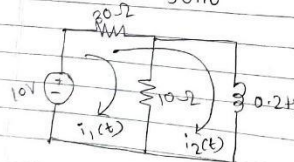
$$i_1(0^+) = \frac{10}{30 + 10} = 0.25 A$$



$$10 - 30(i_1 + i_2) - 10i_1 = 0$$

and

$$10 - 30(i_1 + i_2) - 0.2 \frac{di_2}{dt} = 0$$

$$i_1 = \frac{10 - 30i_2}{40} = 0.25 - 0.75i_2$$

$$\frac{di_2}{dt} + 37.5i_2 = 2.5$$

$$P = 37.5, Q = 2.5$$

$$i_2(t) = e^{-Pt} \int Qe^{Pt} dt + Ke^{-Pt}$$

$$= 0.067 + Ke^{-37.5t}$$

At $t = 0, i_2(0) = 0$

$$0 = 0.067 + K$$

$$K = -0.067$$

$$i_2(t) = 0.067 - 0.067e^{-37.5t}$$

$$V_2(t) = 0.2 \frac{di_2}{dt}$$

$$= 0.2 \frac{d}{dt} (0.067 - 0.067e^{-37.5t})$$

$$V_2(t) = 0.5e^{-37.5t} \quad \text{for } t > 0$$

$$ii, Y(s) = \frac{Cs + 1}{Ls + R} = \frac{(Ls + R)(Cs + 1)}{Ls + R}$$

$$= \frac{L(Cs^2 + Rcs + 1)}{Ls + R}$$

$$= C \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right)$$

$$Y(s) = \frac{H(s-s_1)(s-s_2)}{(s-s_3)}$$

$$s_1, s_2 = \frac{-R \pm \sqrt{(R)^2 - 4 \frac{1}{LC}}}{2}$$

$$= \frac{-R \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}{2L}$$

$$s_3 = \frac{-R}{L}$$

$$s_1 = -10 + j10^4$$

$$s_2 = -10 - j10^4$$

$$Y(s) = H \frac{(s+10-j10^4)(s+10+j10^4)}{s-s_3}$$

$$= H \frac{s^2 + 20s + 10^8}{s-s_3}$$

$$\frac{R}{L} = 20$$

$$s_3 = -20$$

$$Y(s) = H \frac{(s^2 + 20s + 10^8)}{(s+20)}$$

At $s = j\omega$,

$$Y(j\omega) = H \frac{(10^8)}{20} = 10^{-1}$$

$$H = 0.02 \times 10^{-6}$$

$$Y(s) = 0.02 \times 10^{-6} \frac{(s^2 + 20s + 10^8)}{(s+20)}$$

$$C = 0.02 \times 10^{-6} \text{ F} = 0.02 \mu\text{F}$$

$$\frac{1}{LC} = 10^8$$

$$L = \frac{1}{2} \text{ H}$$

$$\frac{R}{L} = 20$$

$$R = 10 \Omega$$

Q. 3

(A)

i) $P(s) = s^5 + s^3 + s$

$P'(s) = \frac{d}{ds} P(s) = 5s^4 + 3s^2 + 1$


$Q(s) = \frac{P(s)}{P'(s)}$

$(5s^4 + 3s^2 + 1) \frac{s^5 + s^3 + s}{5s^4 + 3s^2 + 1}$

$$\begin{array}{r} s^5 + \frac{3}{5}s^3 + \frac{1}{5}s \\ \underline{5s^4 + 3s^2 + 1} \\ \frac{2}{5}s^3 + \frac{4}{5}s \\ \underline{-7s^2 + 1} \\ \frac{2}{5}s^3 - \frac{2}{5}s \\ \underline{-\frac{2}{5}s^3 + \frac{2}{5}s} \\ -7s^2 + 1 \end{array}$$


Since quotient terms are negative, $P(s)$ is not Hurwitz.

ii)

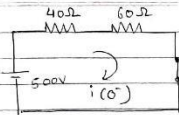

$i(0^+) = \frac{500}{40+60} = 5A$

$i(0^+) = 5A$

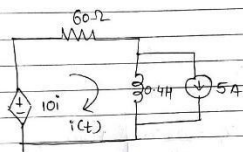

$10i - 60i - 0.4 \frac{di}{dt} = 0$

$\frac{di}{dt} + 125i = 0$

$P = 125$

$i(t) = Ke^{-Pt} = Ke^{-125t}$

$K = 5$
 $i(t) = 5e^{-125t}$ for $t > 0$.

iii)

$v_1 = h_{11}I_1 + h_{12}V_2$
 $I_2 = h_{21}I_1 + h_{22}V_2$

$I_1 = \frac{1}{h_{11}}v_1 - \frac{h_{12}}{h_{11}}v_2$

$I_1 = Y_{11}v_1 + Y_{12}v_2$

$Y_{11} = \frac{1}{h_{11}}$

$Y_{12} = -\frac{h_{12}}{h_{11}}$

$I_2 = h_{21} \left[\frac{1}{h_{11}}v_1 - \frac{h_{12}}{h_{11}}v_2 \right] + h_{22}v_2$

$Y_{21} = \frac{h_{21}}{h_{11}}$

$Y_{22} = \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{11}} = \frac{\Delta h}{h_{11}}$

B

i) Case - I

$Z(s) = \frac{s^2 + 8s + 12}{2s^2 + 8s + 6}$

By CFE

$\frac{2s^2 + 8s + 6}{2s^2 + 8s + 6} \frac{s^2 + 8s + 12}{2s^2 + 8s + 6} \left(\frac{1}{2} \leftarrow Z \right)$

$\frac{s^2 + 4s + 3}{4s + 9} \frac{2s^2 + 8s + 6}{2s^2 + 8s + 6} \left(\frac{1}{2} s \leftarrow Y \right)$

$\frac{7s + 6}{4s + 9} \frac{4s + 9}{7} \left(\frac{8}{7} \leftarrow Z \right)$

$\frac{15}{7} \frac{7}{2} s + 6 \left(\frac{49}{30} s \leftarrow Y \right)$


$\frac{7}{2} s$

$6 \frac{15}{7} \left(\frac{5}{14} \leftarrow Z \right)$

$\frac{15}{7}$

$\frac{7}{2}$

0

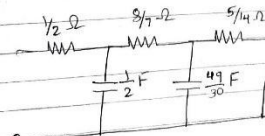

ii) Cont II

$$Z(s) = \frac{12 + 8s + s^2}{6 + 8s + 2s^2}$$

By CFE

$$\begin{array}{r} 6 + 8s + 2s^2 \overline{) 12 + 8s + s^2} \quad (2) \\ \underline{12 + 16s + 4s^2} \\ -8s - 3s^2 \end{array}$$

$$Y(s) = \frac{6 + 8s + 2s^2}{12 + 8s + 2s^2}$$

$$\begin{array}{r} 12 + 8s + 2s^2 \overline{) 6 + 8s + 2s^2} \quad (\frac{1}{2} \leftarrow Y) \\ \underline{6 + 4s + \frac{1}{2}s^2} \end{array}$$

$$\begin{array}{r} 4s + \frac{3}{2}s^2 \overline{) 12 + 8s + 2s^2} \quad (\frac{3}{2} \leftarrow Z) \\ \underline{12 + 6s} \end{array}$$

$$\begin{array}{r} \frac{7}{2}s + s^2 \overline{) 4s + \frac{3}{2}s^2} \quad (\frac{8}{7} \leftarrow Y) \\ \underline{4s + \frac{8}{7}s} \end{array}$$

$$\frac{5}{14}s^2 \overline{) \frac{3}{2}s^2}$$


$$\frac{5}{14}s^2 \overline{) \frac{3}{2}s^2} \quad (\frac{149}{85} \leftarrow Z)$$

$$\frac{1}{2}s$$

$$\frac{5}{14}s^2 \overline{) \frac{1}{2}s^2} \quad (\frac{5}{14} \leftarrow Y)$$

$$\frac{5}{14}s^2$$

0

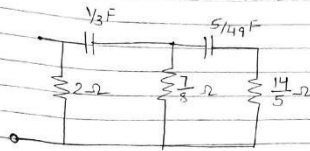

ii) $V_o(s) = \frac{1}{2} \frac{s}{s^2 + 1}$

$$V_o(s) = V_s(s) \times \frac{4/s}{2 + 4/s} = \frac{2V_s(s)}{s+2} = \frac{s}{(s^2+1)(s+2)}$$

$$V_o(s) = \frac{As+B}{s^2+1} + \frac{C}{s+2}$$

$$s = (As+B)(s+2) + C(s^2+1)$$

$$s = (A+C)s^2 + (2A+B)s + (2B+C)$$

$$A+C=0$$

$$2A+B=1$$

$$2B+C=0$$

$$A=0.4, B=0.2, C=-0.4$$

$$V_o(s) = \frac{0.4s+0.2}{s^2+1} - \frac{0.4}{s+2}$$

$$V_o(t) = 0.4 \cos t + 0.2 \sin t - 0.4 e^{-2t} \text{ for } t > 0$$