

**University of Mumbai**  
**Examination 2021 under Cluster 06**  
**(Lead College: Vidyavardhini's College of Engg Tech)**  
**Examinations Commencing from 15<sup>th</sup> June 2021**

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2019

Examination: SE Semester III

Course Code: ELC302 and Course Name: Electronic Devices and Circuits I

Time: 2 hour


Max. Marks: 80


Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	The transition capacitance $C_T$ of PN junction diode decreases
Option A:	With decrease in the reverse voltage
Option B:	With decrease in the forward voltage
Option C:	With increase in the reverse voltage
Option D:	With increase in the forward voltage
2.	Fermi energy level for n-type semiconductors lies -----and P type semiconductor lies -----
Option A:	Close to conduction band, Close to valence band
Option B:	Close to conduction band, Close to conduction band
Option C:	Close to valence band, Close to conduction band
Option D:	Close to valence band, Close to valence band
3.	When a PN junction diode is operated in the forward biased mode , an increased in temperature results in
Option A:	Increase in forward voltage
Option B:	decrease in forward voltage
Option C:	Forward voltage remains same
Option D:	Forward voltage becomes infinite
4.	In the construction of Schottky diode,
Option A:	A PN junction is formed between p type semiconductor and N type semiconductor material.
Option B:	A Metal semiconductor junction is formed between a metal and N type semiconductor material.
Option C:	A Metal Oxide junction is formed between a metal and SiO <sub>2</sub> material.
Option D:	An insulator semiconductor junction is formed between an insulator and P type semiconductor material.
5.	Name the device in which energy is released in the form of light when the recombination of electrons and holes takes place.
Option A:	Zener diode
Option B:	Solar cell
Option C:	LED
Option D:	Photodiode
6.	Name the device which is always operated in reverse bias condition.


Option A:	Schottky diode
Option B:	Solar cell
Option C:	LED
Option D:	Photodiode
7.	In fixed bias circuit using an NPN transistor, if $V_{CC} = 12V$ , $V_{BE} = 0.7V$ , Base resistor $R_B = 100\text{ k}$ then $I_B$ is
Option A:	$80\ \mu A$
Option B:	$113\ \mu A$
Option C:	$130\ \mu A$
Option D:	$130\text{ mA}$
8.	Which Configuration has a high input impedance and low output impedance
Option A:	Common Base Configuration
Option B:	Common Collector Configuration
Option C:	Common Emitter Configuration
Option D:	Collector Emitter Configuration
9.	The emitter current in transistor
Option A:	is almost equal to leakage current
Option B:	is equal to base current
Option C:	is equal to difference between base current and collector current
Option D:	is equal to sum of base current and collector current
10.	The value of current gain $\beta$ in CE Configuration, is ----- as compared to the current gain $\alpha$ in CB Configuration
Option A:	lower
Option B:	higher
Option C:	Same
Option D:	zero
11.	Hybrid $\pi$ model consists of parameters such as
Option A:	small signal resistance $r_\pi$ and a dependent current source $g_m V_\pi$
Option B:	input impedance, reverse voltage gain, current gain and output conductance
Option C:	small signal resistance $r_e$ and a controlled current source
Option D:	small signal resistance $r_\pi$ and an independent current source $g_m V_\pi$

12.	
	Identify biasing circuit
Option A:	DMOSFET fixed bias circuit.
Option B:	EMOSFET Voltage divider bias circuit.
Option C:	EMOSFET feedback biasing circuit
Option D:	Collector to base bias circuit.
13.	In case of JFET, transconductance $g_m$ is given by,
Option A:	$g_m = I_c / V_t$
Option B:	$g_m = 2K_n(V_{gs} - V_t)$
Option C:	$g_m = g_{m0}[1 - (V_{gs}/V_p)]$
Option D:	$g_m = V_a / I_c$
14.	The N channel connecting two N regions is absent in
Option A:	N channel DMOSFET
Option B:	N channel EMOSFET
Option C:	P channel DMOSFET
Option D:	P channel EMOSFET
15.	The input impedance of the MOSFET is very high .Give reason
Option A:	The $SiO_2$ layer is present between gate terminal and channel.
Option B:	Metallic contacts are used for connecting the Drain, gate and source terminals.
Option C:	A P type semiconductor is used as a substrate
Option D:	A N type semiconductor is used as a substrate.
16.	In a N channel EMOSFET when a gate-to-source voltage $V_{gs}$ is 0 V then value of drain current is
Option A:	Maximum
Option B:	infinite
Option C:	zero
Option D:	drain current does not depend on $V_{gs}$
17.	The ripple factor of C Filter is decreases by
Option A:	Increasing with the load resistance
Option B:	decreasing with the load resistance
Option C:	Does not depend on the load resistance
Option D:	has the lowest value
18.	In a center tap full wave rectifier, the value of the average load current $I_{LDC}$ is

Option A:	$I_m/\pi$
Option B:	$2 I_m/\pi$
Option C:	$I_m/2$
Option D:	$I_m/\sqrt{2}$
19.	Reactance of capacitor is given by
Option A:	$X_c= 1/2 \pi f C$
Option B:	$X_c= 1/2 \pi R C$
Option C:	$X_c= 1 / 2 \pi L C$
Option D:	$X_c= 1/ 2 \pi R L$
20.	In the design steps for RC coupled CE amplifiers, the voltage drop across emitter resistor $R_E$ should be ----- as compared to base emitter voltage of transistor.
Option A:	lower
Option B:	higher
Option C:	same
Option D:	zero

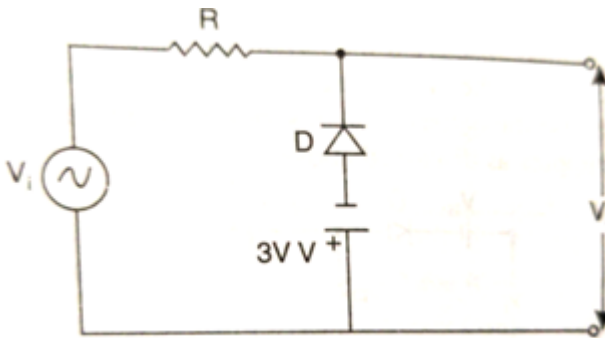
<b>Q2.</b> <b>(20 Marks )</b>	<b>Solve any Four out of Six .</b>	<b>5 marks each</b>
A	Draw and explain the small signal model of a PN Junction diode.	
B	<p>Sinusoidal waveform of 10 V peak to peak is applied at input signal <math>V_i</math>. Biased voltage <math>V= 3V</math>. Identify this circuit and Draw the input and output waveforms for the given circuit.</p> 	
C	Draw and explain the construction of solar cell. What is the array of solar cell?	
D	Explain the operation of Bridge type full wave rectifier and draw the output waveform for $V_{LDC}$ and $I_{LDC}$ .	
E	Compare C and L filters.	
F	Draw Energy band diagram of PN junction diode under Forward biased, Reverse biased and Zero biased	

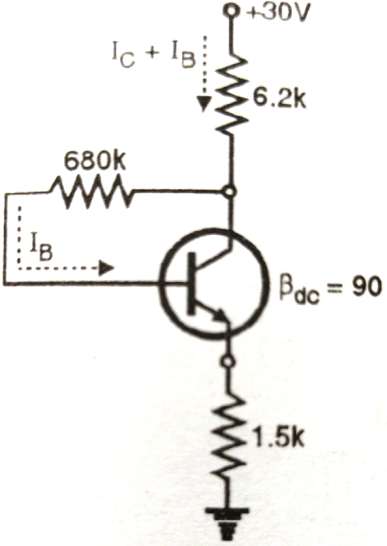Q3. (20 Marks)	Solve any Two Questions out of Three.	10 marks each
A	<p>For the given circuit calculate <math>I_{BQ}</math>, <math>I_{CQ}</math> and <math>V_{CEQ}</math></p>  <p>Here <math>V_{CC}=30V</math>, <math>R_B=680K</math>, <math>B=90</math>, <math>R_C=6.2K</math>, <math>R_E=1.5K</math></p>	
B	<p>For the given circuit, calculate</p> <ol style="list-style-type: none"> <li>1) Voltage gain <math>A_V</math>s</li> <li>2) input resistance</li> <li>3) output resistance</li> </ol> <p><math>\beta= 100</math>, <math>V_A=100</math> and <math>V_{BE}=0.7 V</math></p>	

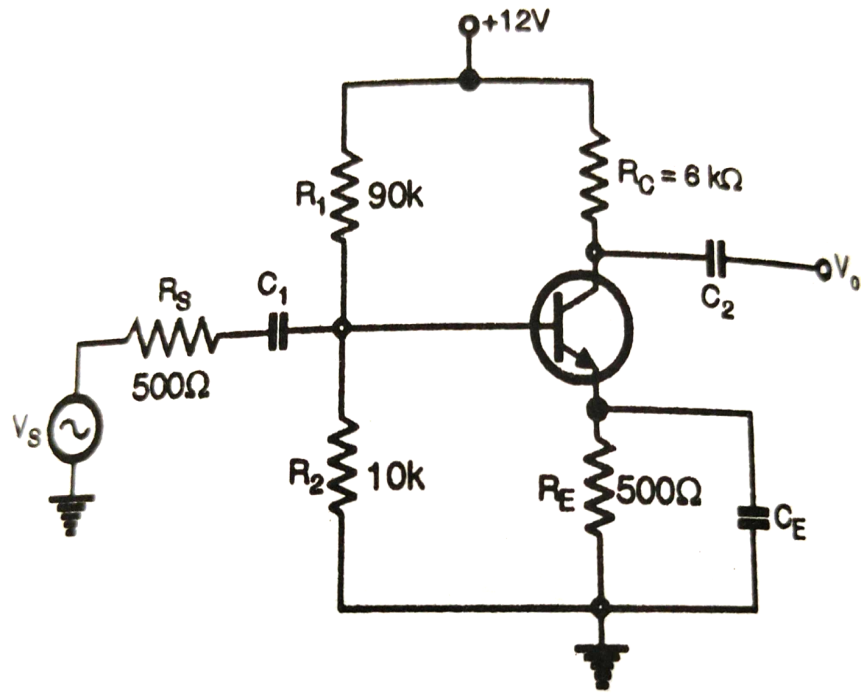

For the given circuit calculate Q point co-ordinates( $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DSQ}$ )

C

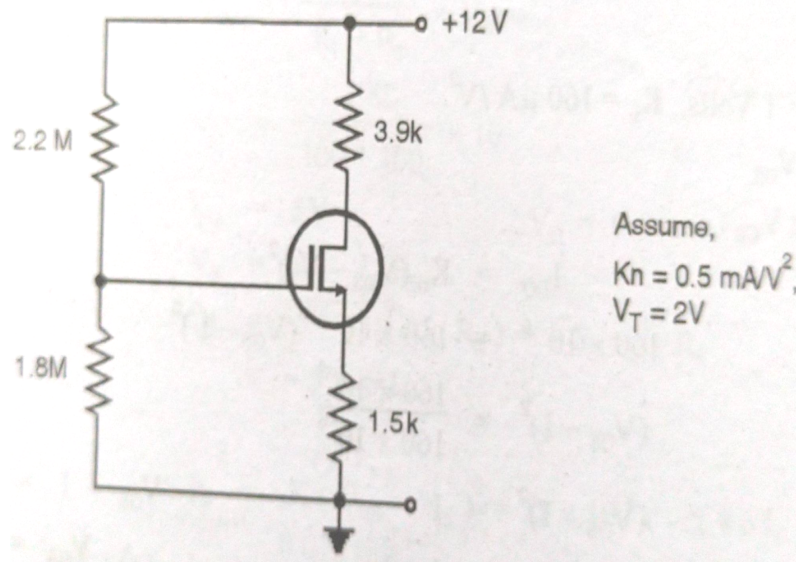

**University of Mumbai**  
**Examination 2021 under Cluster 06**  
**(Lead College: Vidyavardhini's College of Engg Tech)**

**Examinations Commencing from 15<sup>th</sup> June 2021**

Program: **Electronics Engineering**

Curriculum Scheme: Rev 2019

Examination: SE Semester III

Course Code: ELC302 and Course Name: Electronic Devices and Circuits I

Time: 2 hour

Max. Marks: 80

---


---

**Q1:**

<b>Question Number</b>	<b>Correct Option (Enter either 'A' or 'B' or 'C' or 'D')</b>
Q1.	C
Q2.	A
Q3.	B
Q4	B
Q5	C
Q6	D
Q7	B
Q8.	B
Q9.	D
Q10.	B
Q11.	A
Q12.	C
Q13.	C
Q14.	B
Q15.	A
Q16.	C
Q17.	A
Q18.	B
Q19.	A
Q20.	B

**Important steps and final answer for the questions involving numerical example**

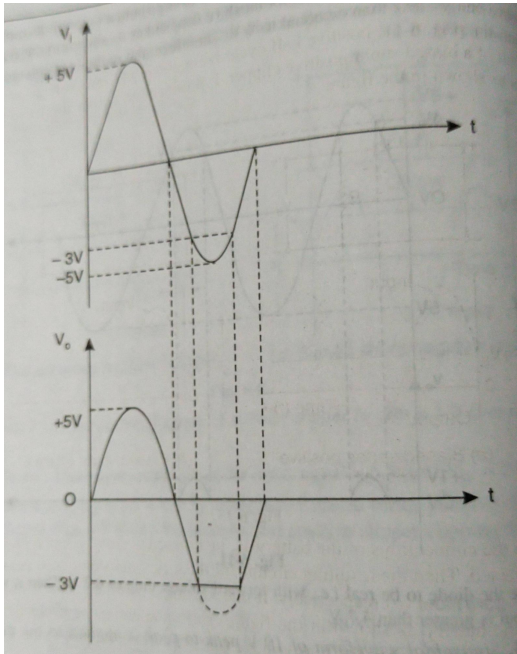Q2(B): This is a biased negative shunt clipper circuit.



Q.3 A)

Solution to Q.3 A)

1) Base current  $I_B$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)(R_C + R_E)}$$

$$= \frac{30 - 0.65}{68k + 91(6.2k + 1.5k)}$$

$$I_B = 21.25 \mu A$$

2) Collector current  $I_C$

$$I_C = \beta I_B$$

$$= 90 \times 21.25 \times 10^{-6}$$

$$= 1.913 \text{ mA}$$

3) Collector-Emitter Voltage

$$V_{CE} = V_{CC} - (I_C + I_B)(R_C + R_E)$$

$$= 30 - [1.91 \times 10^{-3} + 21.25 \times 10^{-6}] [6.2k + 1.5k]$$

$$V_{CE} = 15.1 \text{ V.}$$



Q.3 B)

DC analysis

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

$$= \frac{10}{10 + 90} \times 12$$

$$= 1.2V$$

$$R_{TH} = R_1 \parallel R_2 = 10k \parallel 90k$$

$$= 9k$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)R_E}$$

$$= \frac{1.2 - 0.7}{9k + (101 \times 0.5k)}$$

$$= 8.4 \mu A$$

$$I_C = \beta I_B = 0.84 mA$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 12 - (0.84 \times 10^{-3} \times 6k) - (0.84 \times 10^{-3} \times 0.5k)$$

$$= 6.53V$$

$$r_{\pi} = \frac{V_T \times \beta}{I_C} = \frac{26mV \times 100}{0.84 \times 10^{-3}}$$

$$= 3.095 k\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{0.84 \times 10^{-3}}{0.026}$$

$$= 32.3 \frac{mA}{V}$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{0.84} = 119k$$

Hybrid  $\pi$  equ. ckt

$$R_i = r_{\pi} = 3.095 k\Omega$$

$$R_i' = R_i \parallel R_{TH} = 2.3 k\Omega$$

$$A_{Vs} = \frac{V_o}{V_s} = \frac{V_o}{V_{\pi}} \times \frac{V_{\pi}}{V_s}$$

$$\frac{V_o}{V_{\pi}} = -g_m (r_o \parallel R_C)$$

$$\frac{V_{\pi}}{V_s} = \frac{R_i'}{R_s + R_i'}$$

$$\therefore A_{Vs} = -151.54$$

$$R_o = r_o = 119 k\Omega$$

$$R_o' = r_o \parallel R_C$$

$$= 5.71 k\Omega$$

Q.3 C)

find  $V_{GS}$

$$R_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{1.8}{2.2 + 1.8} \times 12$$
$$= 5.4V$$

$$V_{GS} = V_G - I_D R_S = 5.4 - 1.5 I_D$$

find  $I_D$

$$I_D = k_n (V_{GS} - V_{TH})^2$$
$$= 0.5 (5.4 - 1.5 I_D - 2)^2$$
$$I_D = 4.2 \text{ mA or } 1.22 \text{ mA}$$

Choose  $I_D = 1.22 \text{ mA}$

find  $V_{DS}$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$
$$= 12 - 1.22 (3.9 + 1.5)$$
$$= 5.412V$$