

K. J. Somaiya Institute of Technology, Sion, Mumbai-22
(Autonomous College Affiliated to University of Mumbai)

Nov – Dec 2024

Program: B.Tech Scheme IIB/II

Backlog Examination: SY Semester: III

Course Code: EXC305 and Course Name: Electrical Network Theory




Date of Exam: 30/11/24

Duration: 02 Hours





Max. Marks: 45

Instructions:





- (1) All questions are compulsory.
- (2) Draw neat diagrams wherever applicable.
- (3) Assume suitable data, if necessary.

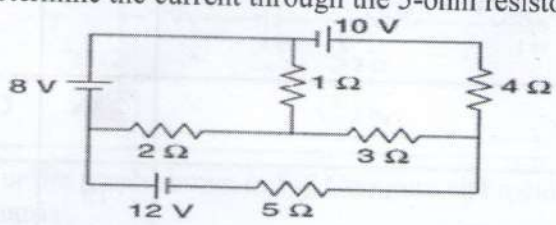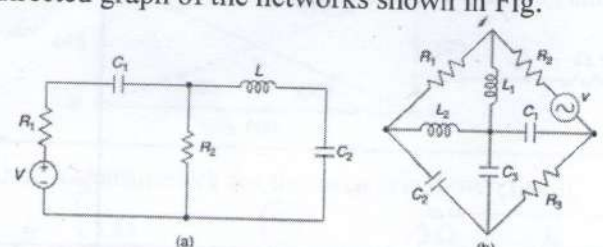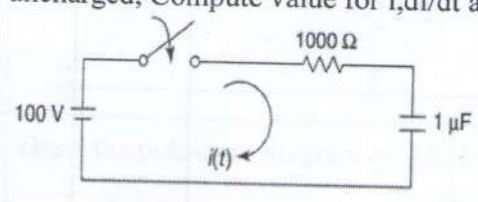		Max. Marks	CO	BT level
Q 1	Solve any 5 questions out of six.	15		
i)	Determine the current through the 5-ohm resistor of the network shown in fig 	3	CO1	AP
ii)	Draw directed graph of the networks shown in Fig. 	3	CO2	R
iii)	In the network of Fig the switch is closed at $t = 0$. With the capacitor uncharged, Compute value for $i, di/dt$ at $t=0+$ 	3	CO3	Ap
iv)	Calculate the Z parameters for the network shown in Fig.	3	CO4	Ap

K. J. Somaiya Institute of Technology, Sion, Mumbai-22
(Autonomous College Affiliated to University of Mumbai)

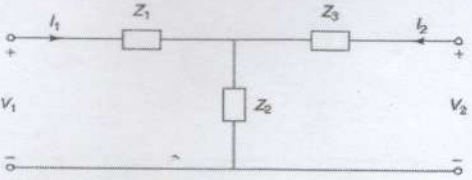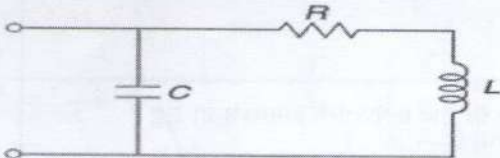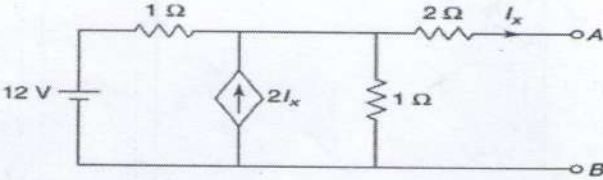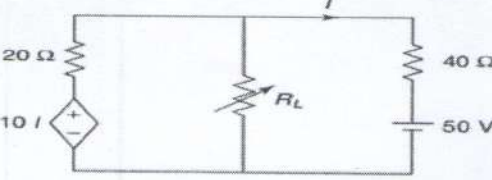Nov – Dec 2024 Program: B.Tech Scheme IIB/II Backlog Examination: SY Semester: III Course Code: EXC305 and Course Name: Electrical Network Theory Date of Exam: 30/11/24 Duration: 02 Hours Max. Marks: 45				
				
v)	Find the driving-point impedance function of a one-port network shown in Fig 	3	CO5	AP
vi)	Enlist the properties of positive real functions.	3	CO6	U
Q.2	Solve any three questions out of four.	15		
i)	Compute V_{Th} and R_{Th} between terminals A and B of the network shown in Fig. 		CO1	Ap
ii)	For the network shown in Fig. Calculate the value of R_L for maximum power transfer. Also, calculate maximum power. 		CO1	Ap
iii)	Find the Laplace transforms of following functions: i..Constant Function K ,ii..Function f(t),iii.3.Unit step function iv..Unit ramp function, v..Unit impulse function		CO3	R

K. J. Somaiya Institute of Technology, Sion, Mumbai-22
(Autonomous College Affiliated to University of Mumbai)

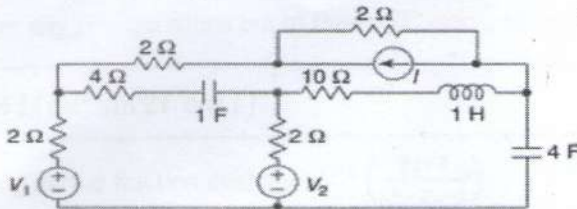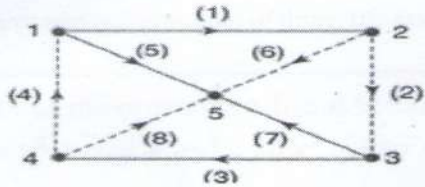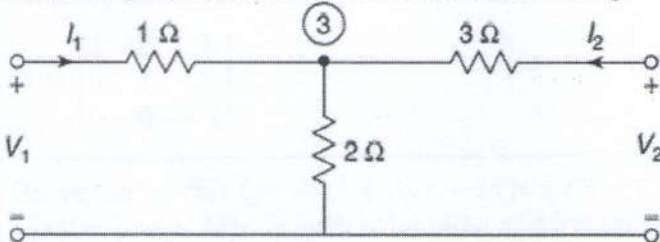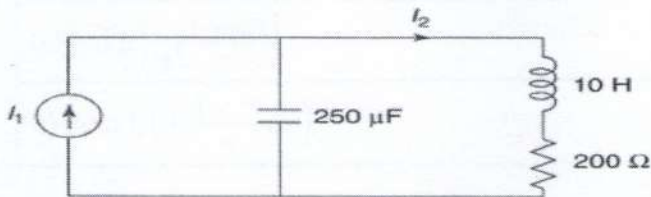Nov – Dec 2024 Program: B.Tech Scheme IIB/II Backlog Examination: SY Semester: III Course Code: EXC305 and Course Name: Electrical Network Theory Date of Exam: 30/11/24 Duration: 02 Hours Max. Marks: 45				
iv)	Test whether the following function is positive real function $F(s) = \frac{s^2 + 1}{s^3 + 4s}$		CO6	Ap
Q.3	Solve any three questions out of four.	15		
i)	For the network shown in Fig. draw the oriented graph and Estimate the incidence matrix 		CO2	U
ii)	For the graph shown in Fig Compute the incidence matrix and f-cutset matrix. 		CO2	Ap
iii)	Calculate Y-parameters for the network shown in Fig 		CO4	Ap
iv)	Draw the pole-zero diagram of I_2/I_1 for the network shown in Fig 		CO5	Ap