
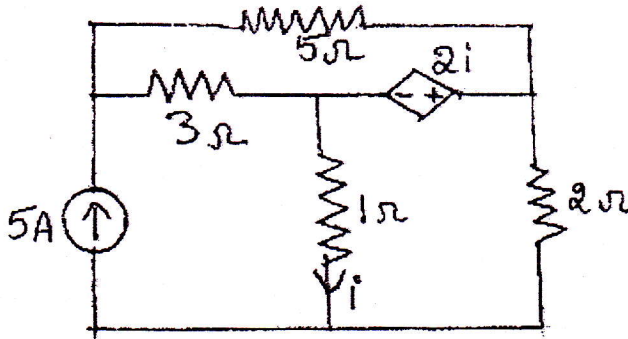


- N.B: 1. Question No. 1 is compulsory.  
 2. Attempt any three from the remaining questions.

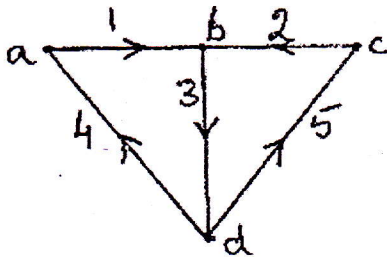
1. (a) Find the voltage drop across  $5\Omega$  resistor in the circuit given below. 5



(b) For the graph given below obtain the incidence matrix and find the number of possible trees. 5



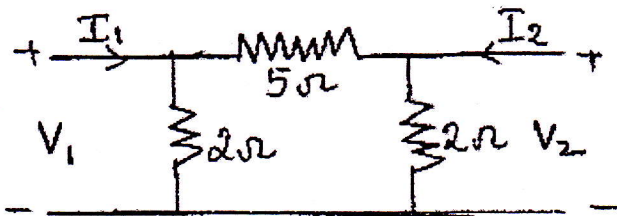
(c) Find y parameters for the two-port network shown in figure. 5



(d) Check whether the following polynomials are Hurwitz 5

- (i)  $P(s) = s^4 + 7s^3 + 6s^2 + 21s + 8$
- (ii)  $P(s) = s^5 + 2s^3 + s$

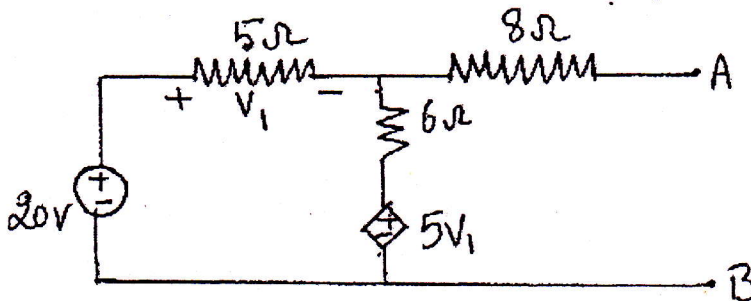
2. (a) Find the Thevenin's equivalent across AB and find the power dissipated in a  $25\Omega$  load. 10



[TURN OVER


(b) Find h parameters for the following Two-port network.

5

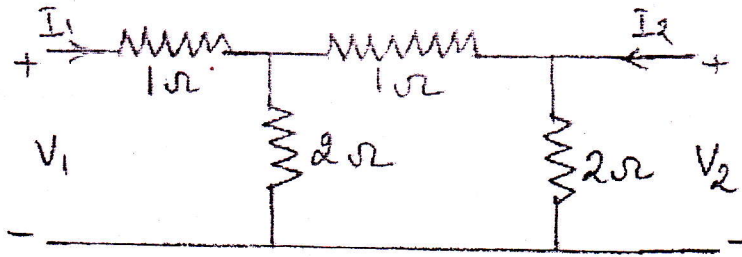


(c) In the network shown below the switch is closed at  $t = 0$ . Assuming all initial conditions to be zero, find  $i$ ,  $di/dt$ ,  $d^2i/dt^2$  for  $t = 0^+$ .

5

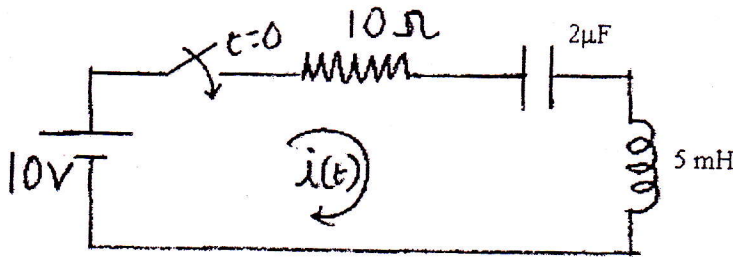

3. (a) Find the tie-set and f-cutset matrix for the oriented graph shown below.

10

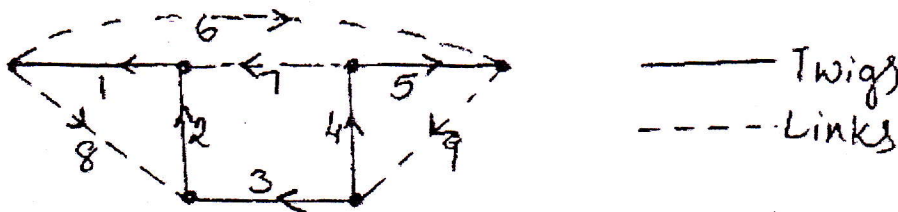


(b) Realize the following function in Foster I and Foster - II forms.

10

$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)}$$

4. (a) A switch is in position A for a long time and then thrown to position B at  $t = 0$ . Find  $i(t)$  for  $t > 0$ . At what value of 't' the current  $i(t)$  will become half of current at  $t=0$


10

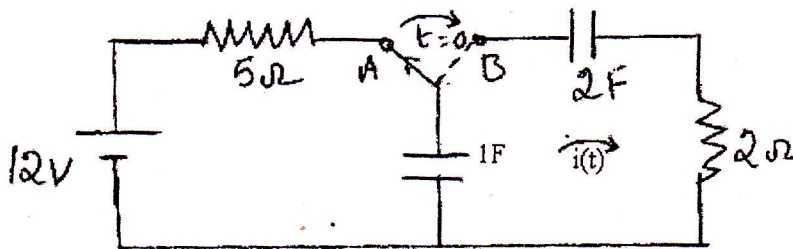

[TURN OVER

(b) For the following network find the driving point impedance function.

5

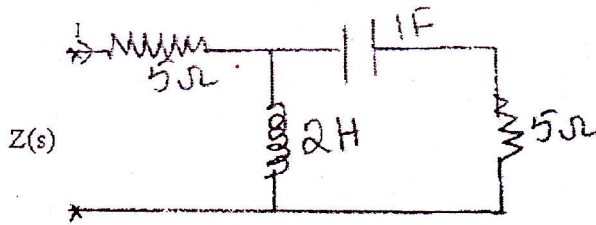


(c) Find the condition for symmetry and reciprocity for a two port network using any one parameter.

5

5. (a) Obtain the ABCD parameters of the following network. If two such networks are cascaded find the overall ABCD parameter.

10

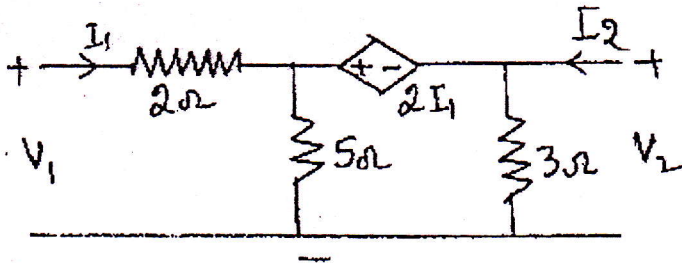

(b) Check whether the following function is positive real or not.

5

$$F(s) = \frac{(s^2 + 6s + 5)}{(s^2 + 9s + 14)}$$


(c) Find the oriented graph if the incidence matrix of the network is as given below.

5

$$A = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & -1 & 0 & 1 & 0 \end{bmatrix}$$


(a) Find the mesh currents if the coupling factor  $k = 0.6$

10

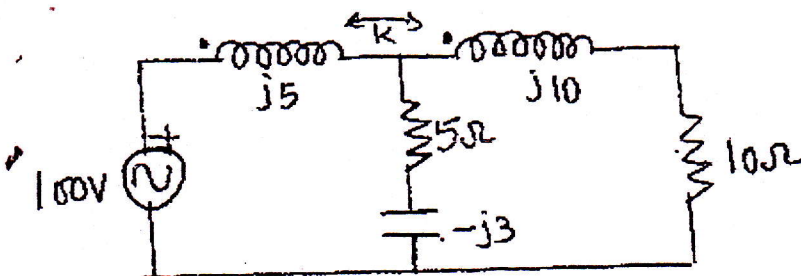

[TURN OVER

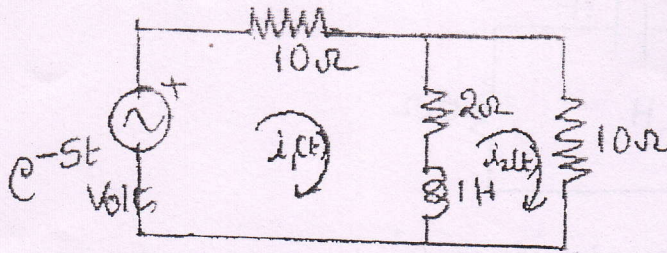
(b) Find  $i_2(t)$  using Laplace transform.



- N. B. :** (1) Question No. 1 is compulsory.  
 (2) Attempt any **three** questions from **remaining** questions.  
 (3) Assume suitable **data** if **necessary**.

Q.1 (a) List name of bridges for RLC measurement with proper classification. 04

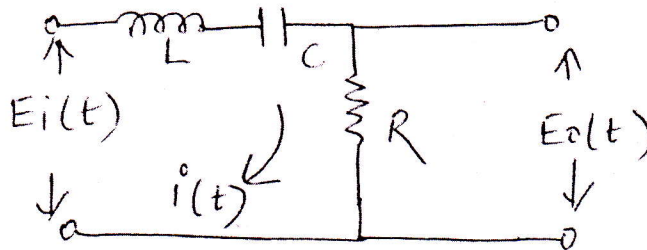Q.1 (b) Find transfer function of given network. 04




Q.1 (c) What is cold junction compensation in thermocouples? 04

Q.1 (d) Draw a block diagram of generalized data acquisition system and explain its components. 04

Q.1 (e) Check whether given system is stable  
 $s^6 + 3s^5 + 2s^4 + 9s^3 + 5s^2 + 12s + 20 = 0$  04

Q.2 (a) Explain Kelvin's double bridge and its application in low resistance measurement. 05

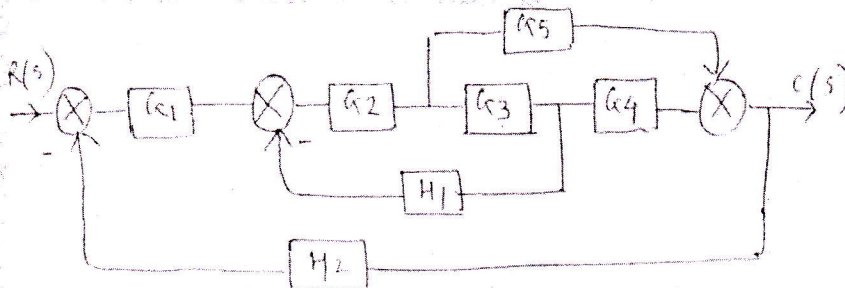(b) Obtain  $C[s] / R[s]$  using block diagram reduction technique 10



Q.3 (a) For unity gain system having 10

$$G(s) = \frac{K}{S(S+5)(S+3)}$$

Sketch root locus and comment on stability.

(b) Draw Bode plot for following transfer function is 10

$$G(s)H(s) = \frac{800}{s^2(s+10)(s+40)}$$

And predict stability.

TURN OVER

Q.4 (a) What is multiplexing ?compare FDM with TDM 05


(b) The system has 05

$$G(S)H(S) = \frac{K}{S(S + 2)(S + 4)(S + 8)}$$

Using Routh criterion find range of K for stability.

(c) Explain working of strain gauge and its application in load measurement. 10

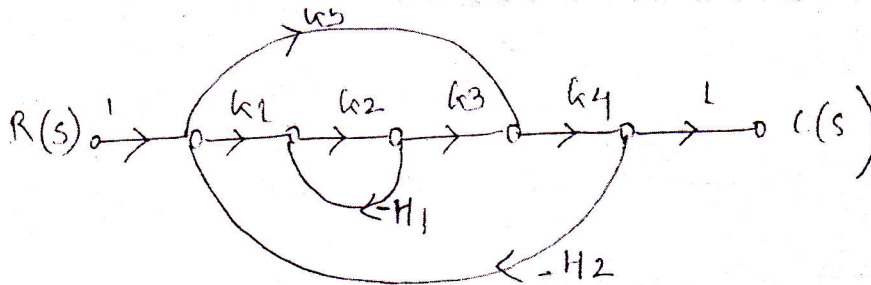Q.5 (a) Find C(s)/R(s) using Mason's gain formula 10



(b) Draw and discuss Hay bridge and its application in measurement of inductance. 10

Q.6 (a) Explain landline telemetry and discuss about any one landline telemetry system. 05

(b) For a system with transfer function  $\frac{64}{s^2 + 5s + 64}$  with unit step input 05

Find damping ratio, damped frequency of oscillations and time for peak overshoot.

(c) Compare temperature transducers Thermistors and thermocouples on the basis of principle, characteristics, ranges and applications. 05

(d) Explain how the stability of system is analyzed using Nyquist criteria. 05

Q. P. Code: 24393

(3 Hours)

[Total Marks: 80]

N.B.: 1) Question No. 1 is Compulsory.

2) Answer any THREE questions from Q.2 to Q.6.

3) Figures to the right indicate full marks.

Q 1. a) Evaluate the Laplace transform of  $\sqrt{1 + \sin t}$  [5]

b) Find directional derivative of  $\phi = 4xz^2 + x^2yz$ , at  $(1, -2, -1)$  in direction of  $2i - j - 2k$  [5]

c) Find orthogonal trajectories of the family of curves  $e^x \cos y - xy = c$ . [5]

d) Obtain half range sine series for  $f(x) = x$ ,  $0 < x < 2$ . [5]

Q 2. a) If  $u + v = e^{2x}(x \cos 2y - y \sin 2y)$  then find analytic function  $f(z)$  by Milne Thomson Method [6]

b) Find the Fourier series for  $f(x) = 9 - x^2$ ,  $-3 \leq x \leq 3$  [6]

c) Find the Laplace transform of the following

i)  $L[t\sqrt{1 + \sin t}]$       ii)  $L\left[\frac{\sinh 2t}{t}\right]$  [8]

Q 3. a) Using Convolution theorem, find Inverse Laplace of  $\frac{s}{(s^2 + 4)^2}$ . [6]

b) Prove that  $J_{\frac{3}{2}}(x) = \sqrt{\frac{2}{\pi x}} \left[ \frac{3}{x} \sin x + \frac{(3-x^2)}{x^2} \cos x \right]$ . [6]

c) Find Fourier series for  $f(x) = (\pi - x)^2$  in  $0 \leq x \leq 2\pi$ . Hence deduce that

$$\frac{\pi^2}{8} = \frac{1}{1^2} + \frac{1}{3^2} + \frac{1}{5^2} + \dots$$
 [8]

Q 4 a) Find the Fourier transform of  $f(t) = e^{-|t|}$  [6]

b) Show that the function  $f_1(x) = 1$ ,  $f_2(x) = x$  are orthogonal on  $(-1, 1)$  and determine the constant A & B so that functions  $f_3(x) = 1 + Ax + Bx^2$  is orthogonal to both  $f_1(x)$  and  $f_2(x)$  on that interval. [6]

c) Find bilinear transformation which maps the points  $z=1, i, -1$  onto the points  $w=i, 0, -i$  hence

**Q. P. Code: 24393**

find the image of  $|z| < 1$  on to w plane find invariant points of this transformation [8]

Q 5 a) Solve using Laplace Transform  $\frac{d^2y}{dt^2} + 2\frac{dy}{dt} + y = te^{-t}$  given  $y(0) = 4$  and  $y'(0) = 2$ . [6]

b) Find Complex form of the Fourier series for  $f(x) = e^{ax}$  in  $-\pi < x < \pi$  where 'a' is a

real constant. Hence deduce that  $\frac{\pi}{a \sinh a\pi} = \sum_{n=-\infty}^{\infty} \frac{(-1)^n}{n^2 + a^2}$  [6]

c) Verify Green's Theorem in the plane for  $\int_C (3x^2 - 8y^2) dx + (4y - 6xy) dy$  where C is

the boundary of the region defined by  $y = x^2$  and  $y = \sqrt{x}$ . [8]

Q 6. a) Prove that  $J'_n(x) = J_{n-2}(x) - 2J_n(x) + J_{n+2}(x)$  [6]

b) Find the map of the line  $x-y=1$  by transformation  $w = \frac{1}{z}$  [6]

c) Evaluate  $\iint_S \bar{F} \cdot d\bar{s}$  where  $\bar{F} = 4x\hat{i} - 2y^2\hat{j} + z^2\hat{k}$  where S is the region bounded by

$x^2 + y^2 = 4$ ,  $z = 0$ ,  $z = 3$  using Gauss divergence theorem. [8]

\*\*\*\*\*



(3 Hours)

80 Marks

Uib

- N.B.: (1) Question No. 1 is compulsory.  
(2) Solve any **three** questions from the **remaining five**  
(3) Figures to the right indicate full marks  
(4) Assume suitable data if necessary and mention the same in answer sheet.

Q.1 a) If  $F(A, B, C) = \sum m(0, 3, 5, 7)$  with its truth table and express F in SOP and POS form [20]

- b) Compare TTL and CMOS Logic families  
c) Perform the following operation using 2's compliment  
i)  $(7)_{10} - (15)_{10}$   
ii)  $(50)_{10} - (2A)_{16}$

Comment on results of (i) and (ii)  
d) Compare SRAM with DRAM

Q.2 a) Implement following Boolean function using 8:1 multiplexer [10]  
 $F(A, B, C, D) = \bar{A} B \bar{D} + A C D + \bar{B} C D + \bar{A} \bar{C} D$

b) Design 3 bit Binary to Gray code Converter [10]

Q.3 a) What are shift registers? How are they classified? Explain working of any one type of shift register. [10]

b) Write VHDL code for 3 bit up counter. [10]

Q.4 a) Explain Master slave JK Flip flop [5]

b) Convert T flip flop to D flip flop. [5]

c) Minimize the following expression using Quine McClusky Technique [10]  
 $F(A, B, C, D) = \sum m(1, 3, 7, 9, 10, 11, 13, 15)$

Q.5 a) State and prove Demorgan's theorem [5]

b) Convert  $(532.125)_8$  into decimal, binary and hexadecimal. [5]

c) Explain Full Adder circuit using PLA having three inputs, 8 product terms and two outputs. [10]

Q.6 a) Prove that NAND and NOR gates are universal gates [10]

b) Draw and explain 3 bit asynchronous binary counter using positive edge triggered JK flip flop. Draw the waveforms. [10]

\*\*\*\*\*

- N.B. : (1) Question No. 1 is compulsory.  
(2) Solve any three questions from the remaining five  
(3) Figures to the right indicate full marks  
(4) Assume suitable data if necessary and mention the same in answer sheet.

Q.1 Attempt any 5 questions [20]

- a) Prove that for a JFET the gate-source bias for zero temperature drift of drain current is at  $|V_p| - 0.63$  volts.  
b) Explain the hybrid pi model of BJT.  
c) Explain Zener as voltage regulator.  
d) Consider a BJT has parameters  $f_T = 500\text{MHz}$  at  $I_C = 1\text{mA}$ ,  $\beta = 100$  and  $C_u = 0.3\text{pF}$ . Calculate bandwidth of  $f_\beta$  and capacitance  $C_\pi$  of a BJT.  
e) Draw and explain small-signal model of a diode.  
f) Why should  $R_C$  be as large as possible in the design of CE amplifier?

Q.2 a) Design a voltage divider bias network using a supply of 24 V, a transistor with  $\beta = 110$  and an operating point of  $I_{CQ} = 4\text{mA}$  and  $V_{CEQ} = 8\text{V}$ . Assume [10]

$$V_E = \frac{1}{8} V_{CE}$$

- b) Explain the fabrication steps of passive elements. [5]  
c) What are the important JFET parameters and define it from characteristics. [5]

Q.3 a) Design the resistors of a single stage CS amplifier for audio frequency with BFW11 with  $I_{DS} = (3.3 \pm 0.6)\text{mA}$  and  $|A_v| = 12$ . [10]

b) Draw CS JFET amplifier with self bias circuit and derive the expression for voltage gain input impedance and output impedance. [10]

Q.4 a) Draw small signal hybrid parameter equivalent circuit for CE amplifier and define the same. What are the advantages of h parameters? [10]

b) For the circuit shown below in Fig.4b, the transistor parameters are  $V_{BE} = 0.7\text{V}$ ,  $\beta = 200$  and  $V_A = \infty$ . [10]

i) Derive the expression for lower cut-off frequency (or time constant) due to input coupling capacitor.

ii) Determine lower cut-off frequency and midband voltage gain.

TURN OVER

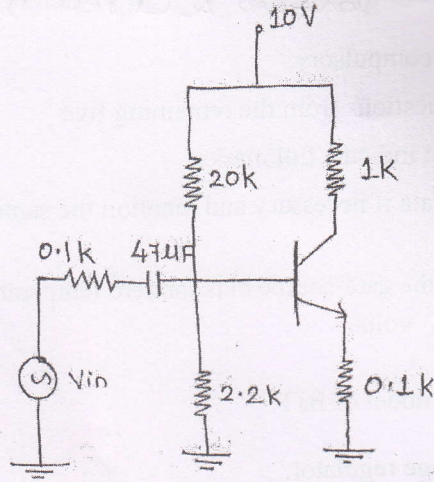


Fig.4b

- Q.5 a) Design an L section LC filter with full wave rectifier to meet the following specifications: The DC output voltage  $V_{DC} = 220$  V, deliver  $I_L = (70 \pm 20)$  mA to the resistive load and the required ripple factor is 0.04. [10]
- b) For the circuit shown below in Fig.5b, the transistor parameters are  $V_{BE(on)} = 0.7$  V,  $\beta = 100$  and  $V_A = \infty$ . Determine  $Z_i$ ,  $Z_o$  and  $A_v$ . [10]

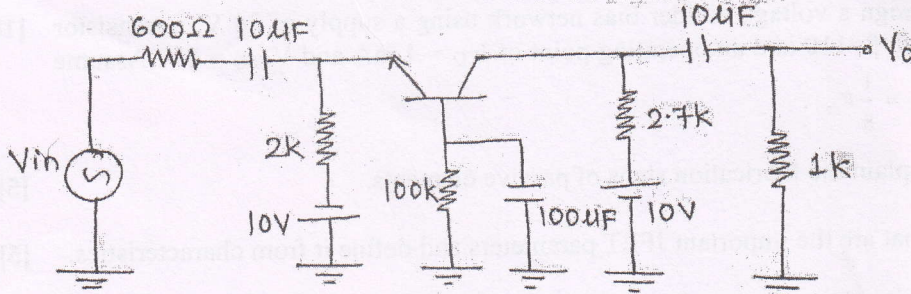


Fig. 5b

- Q.6 Short notes on: (Attempt any four) [20]
- BJT high frequency equivalent circuit
  - Types of resistors and capacitors
  - Stability factors of various biasing techniques of BJT
  - Different types of filters
  - Comparison of BJT CE and JFET CS amplifier

TURN OVER

EXTC  
choice base

Q. P. Coue. 1972

Transistor type	P <sub>max</sub> @ 25°C Watts	V <sub>ce</sub> Form. @ 25°C Volts	V <sub>ce</sub> d.c.	V <sub>ce</sub> (SUS) Volts d.c.	V <sub>ce</sub> (SUS) Volts d.c.	V <sub>ce</sub> (SUS) Volts d.c.	V <sub>ce</sub> (SUS) Volts d.c.	V <sub>ce</sub> (SUS) Volts d.c.	V <sub>ce</sub> (SUS) Volts d.c.	V <sub>ce</sub> (SUS) Volts d.c.	D.C. current gain			h <sub>FE</sub> max.	V <sub>ce</sub> max.	D <sub>rate</sub> above 25°C W/F°C		
											min	typ.	max.					
2N 3055	115-5	15-0	1-1	100	60	70	90	7	200	20	50	70	15	50	120	1-8	1-5	0-7
ECN 055	50-0	5-0	1-0	60	50	55	60	5	200	25	50	100	25	75	125	1-5	3-5	0-4
ECN 149	30-0	4-0	1-0	50	40	65	—	8	150	30	50	110	33	60	90	1-2	4-0	0-3
ECN 100	5-0	0-7	0-6	70	60	50	—	6	200	115	180	280	50	90	280	0-9	—	—
BC147A	0-25	0-1	0-25	50	45	50	—	6	125	35	290	65	—	45	—	—	—	—
2N 525(PNP)	0-25	0-1	0-25	50	45	50	—	6	125	200	450	240	—	330	500	—	—	—
BC147B	0-25	0-1	0-25	50	45	50	—	6	125	200	450	240	—	330	500	—	—	—

Transistor type	h <sub>FE</sub>	h <sub>FE</sub>	h <sub>FE</sub>	BFW 11-JFEI MUTUAL CHARACTERISTICS													
				0-0	0-2	0-4	0-6	0-8	1-0	1-2	1-6	2-0	2-4	2-5	3-0	3-5	4-0
RC 147A	2.7 K Ω	145 Ω	15 × 10 <sup>-4</sup>	0-0	0-2	0-4	0-6	0-8	1-0	1-2	1-6	2-0	2-4	2-5	3-0	3-5	4-0
2N 525 (PNP)	1-4 K Ω	250 Ω	3-2 × 10 <sup>-4</sup>	10	9-0	8-3	7-5	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
RC 147B	4.5 K Ω	300 Ω	2 × 10 <sup>-4</sup>	10	9-0	8-3	7-5	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
ECN 100	500 Ω	—	—	10	9-0	8-3	7-5	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
ECN 149	250 Ω	—	—	10	9-0	8-3	7-5	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
ECN 055	100 Ω	—	—	10	9-0	8-3	7-5	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
2N 3055	25 Ω	—	—	10	9-0	8-3	7-5	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0

N-Channel JFET	Type	V <sub>gs</sub> max. Volts	V <sub>gs</sub> max. Volts	V <sub>gs</sub> max. Volts	P <sub>max</sub> @ 25°C	I <sub>DS</sub> max.	I <sub>DS</sub> (typ.)	I <sub>DS</sub> min.	g <sub>m</sub> (typical)	-V <sub>r</sub> Volts	I <sub>r</sub>	D <sub>rate</sub> above 25°C
2N3822		50	50	50	300 mW	2 mA	3000 μD	6	50 KΩ	—	—	0-50°C/mW
BFW 11 (typical)		30	30	30	300 mW	7 mA	5600 μD	2-5	50 KΩ	—	—	0-50°C/mW

A6770F25C124EB77F6B935C4L143C9B1

F765B4AF9629D2B23406B13A0EBA989A