


**K. J. Somaiya Institute of Technology, Sion, Mumbai-22**  
(Autonomous College Affiliated to University of Mumbai)

~~Nov-Dec 2024~~ **Jan-Feb 2025**

Program: B.Tech. (Electronics and Telecommunication) Scheme IIB  
**Supplementary** Regular Examination: SY Semester: III  
Course Code: EXC 303 and Course Name: Electronic Devices & Circuits  
Date of Exam: **29-01-25** Duration: 02.5 Hours Max. Marks: 60

**Instructions:**

- (1) All questions are compulsory.
- (2) Draw neat diagrams wherever applicable.
- (3) Assume suitable data, if necessary.

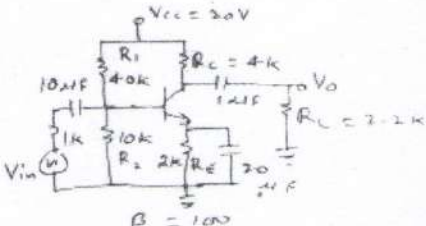Q. No.	Question	Max. Marks	CO	BT level
Q 1	Solve any <b>two</b> questions out of three: (05 marks each)	10		
a)	Compare drift current and diffusion current.		1	1
b)	Draw the circuit diagram of zener diode as a voltage regulator and explain its operation?		2	2
c)	Draw the circuit diagram of voltage divider biasing for BJT amplifier and explain its operation?		3	3
Q 2	Solve any <b>two</b> questions out of three: (05 marks each)	10		
a)	Draw the circuit diagram of voltage divider biasing for MOSFET amplifier and explain its operation?		3	2
b)	Explain the effect of coupling and bypass capacitors in frequency response of the amplifier?		4	3
c)	What is the function of power amplifiers? Explain its classification?		6	3
Q.3	Solve any <b>two</b> questions out of three. (10 marks each)	20		
a)	Determine low cut off frequency for the amplifier shown below... $V_{CC} = 14$ Volts, $\beta = 100$ , $V_{BE} = 0.7$ Volts 		2	4
b)	What are different types of coupling methods used in multistage amplifiers? State its advantages, disadvantages and applications..		5	2

**K. J. Somaiya Institute of Technology, Sion, Mumbai-22**  
(Autonomous College Affiliated to University of Mumbai)

<del>Nov-Dec 2024</del> <b>Jan-Feb 2025</b>	
Program: B.Tech. (Electronics and Telecommunication) Scheme IIB <i>Supplementary</i> Regular Examination: SY Semester: III Course Code: EXC 303 and Course Name: Electronic Devices & Circuits Date of Exam: <b>29-01-25</b> Duration: 02.5 Hours Max. Marks: 60	

c)	Compare Voltage amplifier and power amplifier.		6	2
Q.4	Solve any <b>two</b> questions out of three. (10 marks each)	20		
a)	Draw the circuit diagram and explain the operation of MOSFET differential amplifier? Define CMRR, Differential and common mode gain		3	3
b)	Draw the circuit diagram and derive the equation of voltage gain, input and output impedance for CS MOSFET amplifiers?		3	3
c)	Calculate the forward bias current of a Si diode when forward bias voltage of 0.4V is applied, the reverse saturation current is $1.17 \times 10^{-9} \text{A}$ and the thermal voltage is 25.2mV. Assume $\eta = 1$ .		1	4

\*\*\*\*\*