

**K. J. Somaiya Institute of Technology, Sion, Mumbai-22**  
**(Autonomous College Affiliated to University of Mumbai)**

Nov – Dec 2025

(B. Tech)Program: EXTC Scheme I/II/IIB/III: III

Regular/Supplementary Examination: SY Semester: III

Course Code:EXC303 and Course Name: Electronic Devices and Linear circuits

Date of Exam: 02/12/2025

Duration: 02.5 Hours

Max. Marks: 60

**Instructions:**

- (1)All questions are compulsory.
- (2)Draw neat diagrams wherever applicable.
- (3)Assume suitable data, if necessary.

Q. No.	Question	Max. Marks	CO	BT level
Q 1	Solve any <b>two</b> questions out of three: (05 marks each)	10		
a)	Draw the basic circuit diagram of IC 566 as a VCO .		6	U
b)	Explain N-Channel MOSFET characteristic.		1	U
c)	Draw a neat block diagram off OP-AMP IC 741 also, compare its ideal and practical characteristic	10	2	Ap
Q 2	Solve any <b>two</b> questions out of three: (05 marks each)			
a)	Design a 555 astable circuit to generate a 1 kHz signal with 60% duty cycle.		5	U
b)	Explain Voltage to Current and Current to Voltage Converter.	10	3	Ap
c)	Draw and Explain the circuit for Zero crossing Detector.		4	U
Q.3	Solve any <b>two</b> questions out of three. (10 marks each)	20		
a)	Explain Phase locked loop using Block diagram. State role of all sub block of VCO used in PLL.		6	Ap
b)	Draw summing amplifier circuit using opamp and Derive $V_o$ for summing amplifier.		2	An
c)	Explain half wave and Full wave precision rectifier.	20	4	U
Q.4	Solve any <b>two</b> questions out of three. (10 marks each)			
a)	Explain the significance of biasing in a transistor amplifier. Explain any One biasing circuits		1	U
b)	Explain 555 IC Astable mode of operation.		5	U
c)	Explain working of RC phase shift Oscillator.		3	U