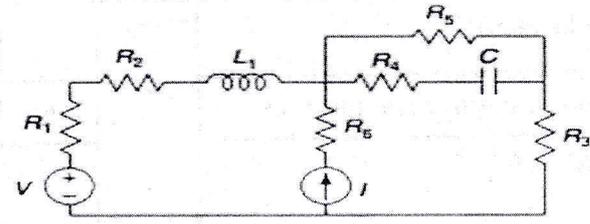
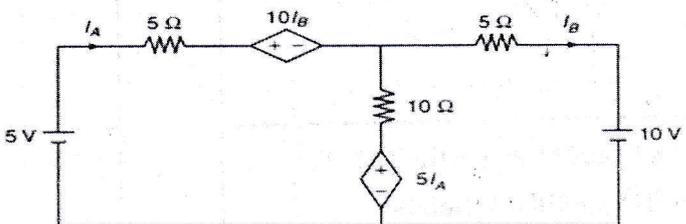
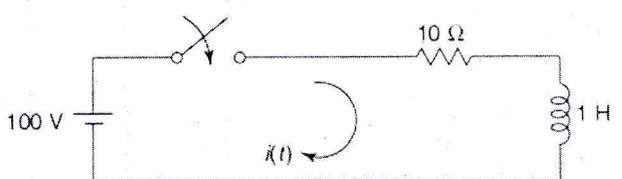


K. J. Somaiya Institute of Technology, Sion, Mumbai-22
(Autonomous College Affiliated to University of Mumbai)

Nov – Dec 2025
 Program: B. Tech_Scheme III
 Supplementary Examination: SY Semester: III
 Course Code:EXC305_and Course Name:Electrical Network Theory
 Date of Exam: **7-2-26** Duration: 02.5 Hours Max. Marks: 60

Instructions:
 (1) All questions are compulsory.
 (2) Draw neat diagrams wherever applicable.
 (3) Assume suitable data, if necessary.

Q. No.	Question	Max. Marks	CO	BT level
Q 1	Solve any two questions out of three: (05 marks each)	10		
a)	For the circuit shown in Fig., draw the oriented graph and write the incidence matrix. 		2	Ap
b)	Obtain the branch currents in the network shown in Fig. 		1	Ap
c)	In the given network of Fig. , the switch is closed at $t = 0$. With zero current in the inductor, find $i(t)$ at $t = 0+$ 		3	Ap

Nov - Dec 2025

Program: B. Tech_Scheme III




Supplementary Examination: SY Semester: III

Course Code: EXC305 and Course Name: Electrical Network Theory

Date of Exam: 7-2-26

Duration: 02.5 Hours

Max. Marks: 60

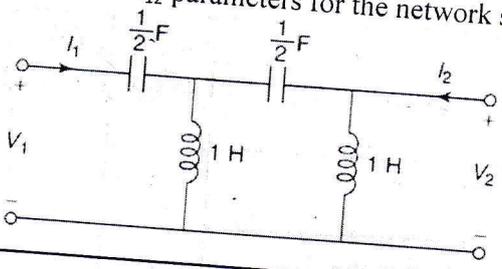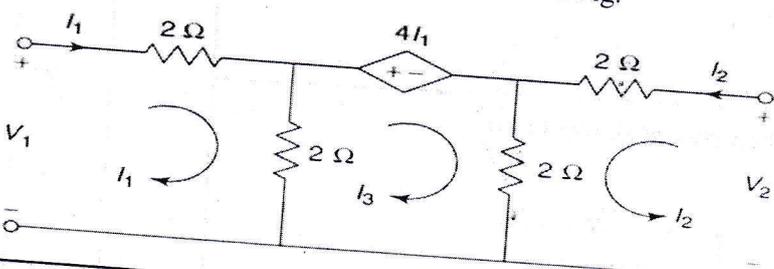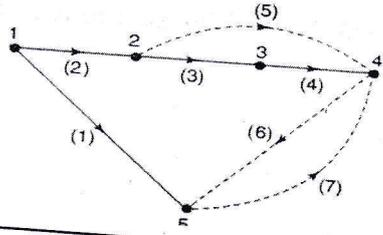Q 2	Solve any two questions out of three: (05 marks each)	10		
a)	What are the properties of Positive Real Functions	6		U,R
b)	Find h_{11} and h_{12} parameters for the network shown in Fig. 	4		Ap
c)	Test whether the polynomial $P(s) = S^3 + 4S^2 + 5S + 2$ is Hurwitz	5		Ap
Q.3	Solve any two questions out of three. (10 marks each)	20		
a)	Test whether $F(s) = \frac{S(S+3)(S+5)}{(S+1)(S+4)}$ is positive real function.	6		Ap
b)	Find Z and h-parameters for the network shown in Fig. 	4		Ap
c)	The graph of a network is shown in Figure. Write the (a) incidence matrix, and (b) tieset matrix c) cutset matrix 	2		Ap
Q.4	Solve any two questions out of three. (10 marks each)	20		

Nov – Dec 2025




Program: B. Tech_Scheme III

Supplementary Examination: SY Semester: III

Course Code:EXC305_and Course Name:Electrical Network Theory

Date of Exam: **7-2-26** Duration: 02.5 Hours

Max. Marks: 60

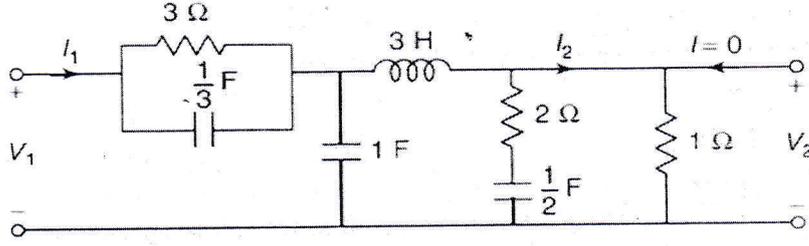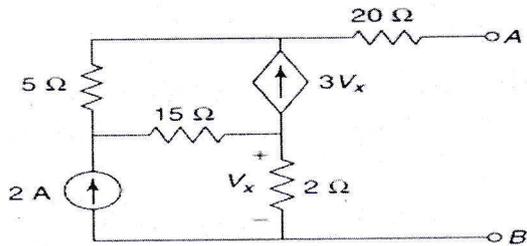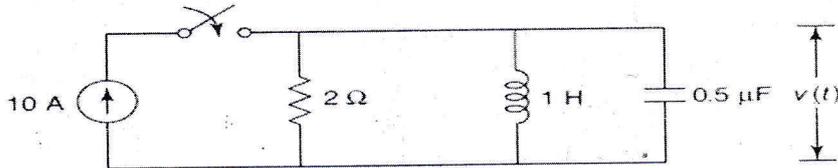a)	<p>Determine the voltage ratio V_2/V_1, current ratio I_2/I_1, transfer impedance V_2/I_1 and driving-point impedance V_1/I_1 for the network shown in Fig.</p> 	5	Ap
b)	<p>For the network shown in Fig. find Norton's equivalent network</p> 	1	Ap
c)	<p>In the network, the switch is closed at $t = 0$. With the capacitor uncharged, find value for v, dv/dt, d^2v/dt^2 at $t = 0+$</p> 	3	Ap
