

**University of Mumbai**  
**Examination 2020 under Cluster 06**  
**(Lead College: Vidyavardhini's College of Engg Tech)**  
**Examination Commencing from 7<sup>th</sup> January 2021 to 20<sup>th</sup> January 2021**  
**Program: Electronics Engineering**  
**Curriculum Scheme: Rev 2019**  
**Examination: SE Semester III**  
**Course Code: ELC303 and Course Name: Digital Logic Circuits**

Time: 2 hour

Max. Marks: 80


<b>Q1.</b>	<b>Choose the correct option for following questions. All the Questions are compulsory and carry equal marks</b>
1.	What is the decimal equivalent of $(11111)_2$ .
Option A:	$(41)_{10}$
Option B:	$(21)_{10}$
Option C:	$(31)_{10}$
Option D:	$(11)_{10}$
2.	What is the reflected binary code of $(100101)_2$ .
Option A:	111000
Option B:	101010
Option C:	101111
Option D:	110111
3.	Given the two binary numbers $x=1010100$ and $y=1000011$ perform the subtraction $x-y$ , using 2's complement.
Option A:	0010001
Option B:	1101110
Option C:	1111111
Option D:	0000111
4.	How many two-input AND and OR gates are required to realize $Y = AB+CD+E$ ?
Option A:	2,2
Option B:	2,3
Option C:	3,2
Option D:	3,3
5.	If a half adder has A and B as the inputs, then the sum is given by
Option A:	A EX-NOR B
Option B:	A OR B
Option C:	A AND B
Option D:	A XOR B
6.	What are the number of select lines required for a 8:1 multiplexer?
Option A:	1

Option B:	2
Option C:	3
Option D:	4
7.	A decoder converts 'n' inputs to _____ number of outputs.
Option A:	$2^n$
Option B:	n
Option C:	$n^2$
Option D:	2n
8.	A basic latch circuit consists of
Option A:	one comparator
Option B:	three adders
Option C:	two inverters
Option D:	one amplifier
9.	A 'n-stage' Johnson counter will circulate a single data bit giving sequence of _____ number of states.
Option A:	2n
Option B:	n
Option C:	n+1
Option D:	$n^2$
10.	A decade counter can be implemented with how many number of flip flops?
Option A:	10
Option B:	5
Option C:	4
Option D:	8
11.	MSI counter IC74163 is
Option A:	4 bit up counter with synchronous preset and clear
Option B:	ripple counter
Option C:	decade counter
Option D:	4 bit up counter with asynchronous preset and clear
12.	In a sequential circuit designed as a moore machine, the output depends on
Option A:	present state
Option B:	past state
Option C:	next state
Option D:	external inputs
13.	IC 7490 is a
Option A:	Group A Asynchronous counter IC
Option B:	Group B Asynchronous counter IC
Option C:	Group C Asynchronous counter IC
Option D:	synchronous counter
14.	The internal structure of MSI counter IC 7493 consist of

Option A:	Mod 2 and Mod 6 counter
Option B:	Mod 2 and Mod 8 counter
Option C:	Mod 5 and Mod 8 counter
Option D:	Mod 2 and Mod 5 counter
15.	An AND gate with 8 input has a fan-out of
Option A:	8
Option B:	4
Option C:	2
Option D:	1
16.	What does FPGA stand for
Option A:	Field Programming Gate Array
Option B:	Field Programmable Gate Array
Option C:	First Program Gate Array
Option D:	First Programmable Gate Array
17.	Programmable Array Logic has
Option A:	a programmable AND and fixed OR array
Option B:	a programmable AND and a programmable OR array
Option C:	only a programmable AND array
Option D:	only a programmable OR array
18.	In verilog HDL the operator <= is used for
Option A:	Blocking assignment
Option B:	Non-Blocking assignment
Option C:	Single line comment
Option D:	Logical left shift
19.	Which type of modeling style is not used in verilog hardware description language
Option A:	Structural
Option B:	Datatype
Option C:	Behavioral
Option D:	Data Flow
20.	The Verilog expression for Boolean equation $Y=AB+C$ will be
Option A:	assign $Y= (A*B)+C$
Option B:	assign $Y= (A.B)+C$
Option C:	assign $Y= (A^B) C$
Option D:	assign $Y= (A\&B) C$

<b>Q2.</b> <b>(20 Marks Each)</b>	
A	<b>Solve any Two 5 marks each</b>
i.	Design and implement a half adder using gates.
ii.	State and prove De-Morgan's theorem.
iii.	Compare mealy and moore machines.
B	<b>Solve any One 10 marks each</b>
i.	Design a Mod-10 asynchronous counter using J-K Flip-Flops.
ii.	Write a program using Verilog HDL to implement a 8:1 multiplexer.

<b>Q3.</b> <b>(20 Marks Each)</b>	
A	<b>Solve any Two 5 marks each</b>
i.	Write a short note on Complex Programmable Logic Devices.
ii.	Convert a JK Flip-Flop to T Flip-Flop.
iii.	Write a program for a D flip-flop with asynchronous reset using Verilog HDL.
B	<b>Solve any One 10 marks each</b>
i.	Design and implement full subtractor circuit using a 3:8 decoder IC 74138.
ii.	Analyze the given state machine and draw the state diagram.

 

**University of Mumbai**  
**Examination 2020 under Cluster 06**  
**(Lead College: Vidyavardhini's College of Engg Tech)**  
**Examination Commencing from 7<sup>th</sup> January 2021 to 20<sup>th</sup> January 2021**  
Program: **Electronics Engineering**  
Curriculum Scheme: Rev 2019  
Examination: SE Semester III  
Course Code: ELC303 and Course Name: Digital Logic Circuits

Time: 2 hour Max. Marks: 80

---

---

**Q1:**

<b>Question Number</b>	<b>Correct Option (Enter either 'A' or 'B' or 'C' or 'D')</b>
Q1.	C
Q2.	D
Q3.	A
Q4	A
Q5	D
Q6	C
Q7	A
Q8.	C
Q9.	A
Q10.	C
Q11.	A
Q12.	A
Q13.	A
Q14.	B
Q15.	D
Q16.	B
Q17.	A
Q18.	B
Q19.	B
Q20.	D

**Important steps and final answer for the questions involving numerical example**

Q2(A) i: Step 1: Truth Table of Half Adder


Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Step 2:

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = A.B$$

Step 3:

 


Q2 (B) i

Step 1: Truth table of Mod 10 counter

Clock Count	Output bit Pattern				Decimal Value
	QD	QC	QB	QA	
1	0	0	0	0	0
2	0	0	0	1	1
3	0	0	1	0	2
4	0	0	1	1	3
5	0	1	0	0	4
6	0	1	0	1	5
7	0	1	1	0	6
8	0	1	1	1	7
9	1	0	0	0	8
10	1	0	0	1	9
11	Counter Resets its Outputs back to Zero				


Step 2:

Circuit Diagram

 

Step 3:

Timing Diagram

 

Q2 (B)(ii)

```

module Multiplexer(d0,d1,d2,d3,d4,d5,d6,d7,sel,out);
input d0,d1,d2,d3,d4,d5,d6,d7;
input [2:0] sel;
output reg out;
always@(sel)
begin
    case(sel)
        3'b000:out=d0;
        3'b001:out=d1;
        3'b010:out=d2;
        3'b011:out=d3;
        3'b100:out=d4;
        3'b101:out=d5;
        3'b110:out=d6;
        3'b111:out=d7;
    endcase
end
endmodule
    
```

Q3 A(ii)

Truth Table of D Flip-flop

Input D	Outputs	
	Present State Q <sub>n</sub>	Next State Q <sub>n+1</sub>
0	0	0
0	1	0
1	0	1
1	1	1

### Excitation Table of JK Flip-flop

Outputs		Inputs	
Present State	Next State	J	K
$Q_n$	$Q_{n+1}$		
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

```

begin
if(reset==1'b1)
Q <= 1'b0;
else
Q <= D;
end
endmodule

```


### J-K to D conversion Table

D Input	Outputs		JK Inputs	
	Present State	Next State	J	K
D	$Q_n$	$Q_{n+1}$		
0	0	0	0	X
0	1	0	X	1
1	0	1	1	X
1	1	1	X	0

### Q3 B(i) Truth Table of Full Subtractor


A	B	$B_{in}$	D	$B_{out}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

### K-Map

 


$$D = \sum m(1, 2, 4, 7)$$

### Circuit Diagram:

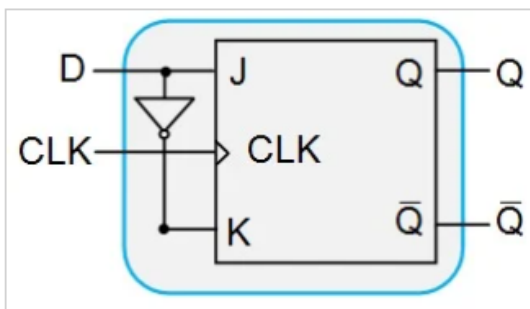

$$B = \sum m(1, 2, 3, 7)$$

### Circuit Diagram:

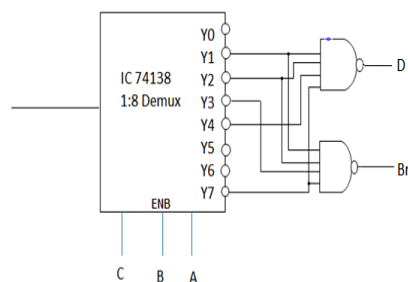

### Q3A(iii)

```

module DFlipFlop (D, clk, reset, Q);
input D; // Data input
input clk; // clock input
input reset; // asynchronous reset
output reg Q; // output Q
always @(posedge clk or posedge reset)

```

### Q3 B(ii)

### Flip-Flop Equations:

$$\begin{aligned}
J_A &= B & K_A &= B x' \\
J_B &= x' & K_B &= A \oplus x
\end{aligned}$$

Next State Equations:

$$A(t+1) = J_A Q'_A + K'_A Q_A$$

$$= A'B + AB' + Ax$$

$$B(t+1) = J_B Q'_B + K'_B Q_B$$

$$= B'x' + ABx + A'Bx'$$

State Table:

Present State			I/P	Next State		Flip-Flop Inputs			
A	B	x		A	B	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>
0	0	0	0	1	0	0	1	0	
0	0	1	0	0	0	0	0	1	
0	1	0	1	1	1	1	1	0	
0	1	1	1	0	1	0	0	1	
1	0	0	1	1	0	0	1	1	
1	0	1	1	0	0	0	0	0	
1	1	0	0	0	1	1	1	1	
1	1	1	1	1	1	0	0	0	

Transition Diagram

